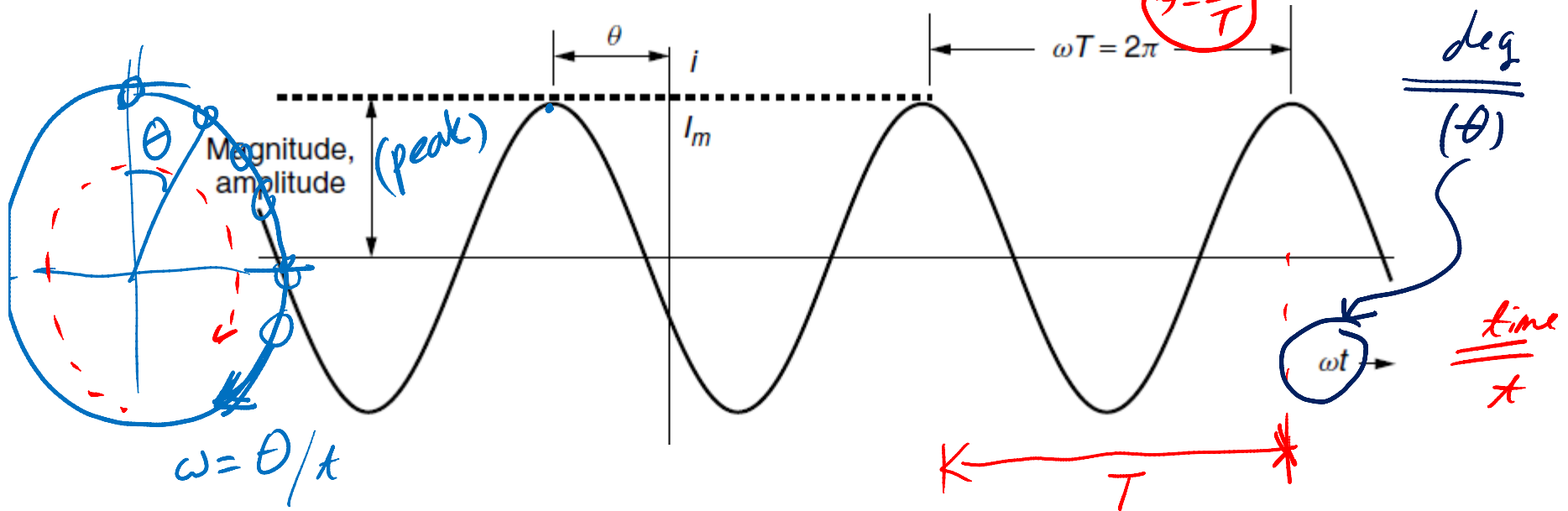


Chapter2: Electric Power

⌘ Sinusoidal Source $i = I_m \cos(\omega t + \theta) = I_m \cos(2\pi f t + \theta) = I_m \cos\left(\frac{2\pi}{T} t + \theta\right)$



⌘ Instantaneous Power $p = i^2 R$


⌘ Average Power (by effective current) $P_{\text{avg}} = (i^2)_{\text{avg}} R = I_{\text{eff}}^2 R$

⌘ RMS current = Effective current $I_{\text{eff}} = \sqrt{(i^2)_{\text{avg}}} = I_{\text{rms}}$


$$I_{\text{rms}} = \sqrt{(i^2)_{\text{avg}}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

RMS value

⌘ RMS value of a square wave

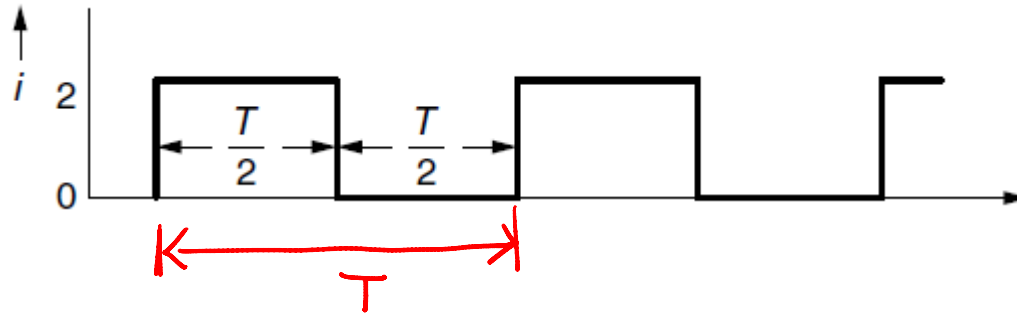

⌘ ANSWER

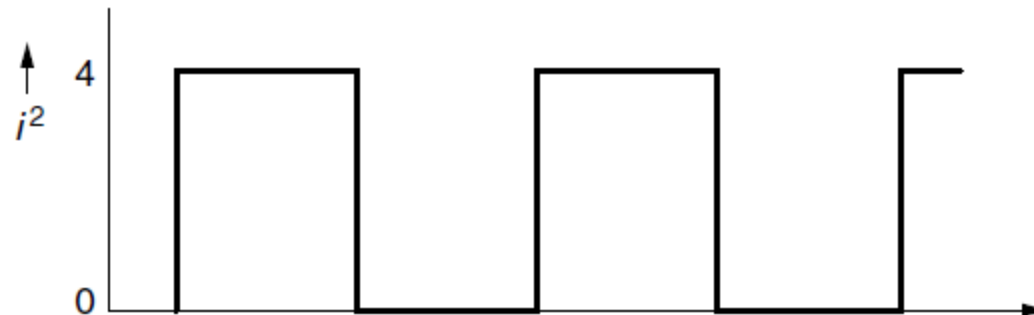


$$\begin{aligned} & \sqrt{\frac{1}{T} \int_0^{T/2} i^2 dt} \\ &= \sqrt{\frac{1}{T} [4t]_0^{T/2}} \\ &= \sqrt{\frac{2T}{T}} \\ &= \sqrt{2} \end{aligned}$$


$$I_{\text{rms}} = \sqrt{(i^2)_{\text{avg}}} = \sqrt{2}A$$

RMS value

RMS value of a sinusoidal voltage

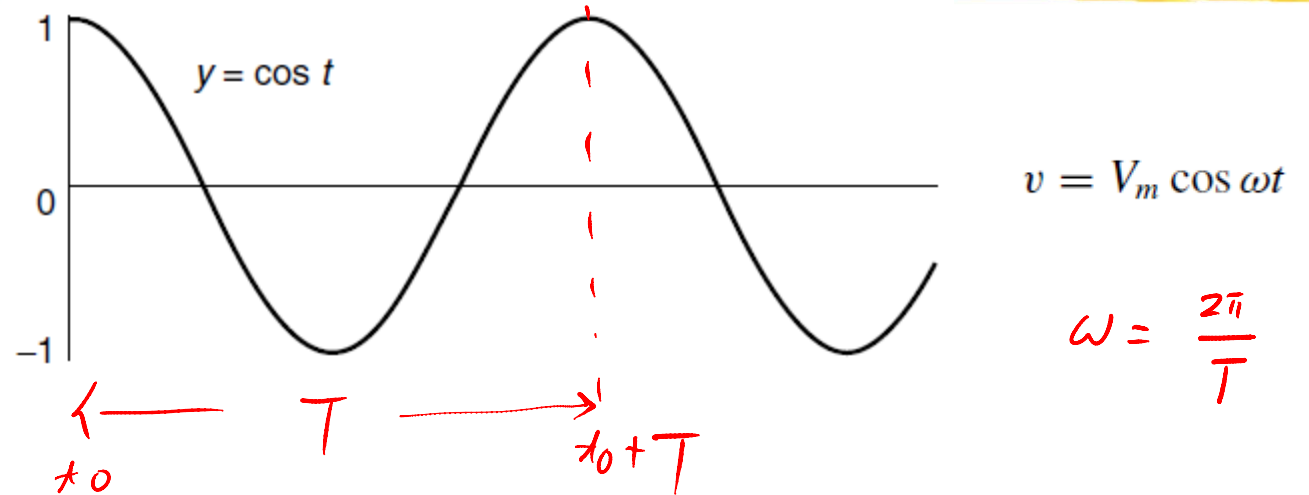


ANSWER

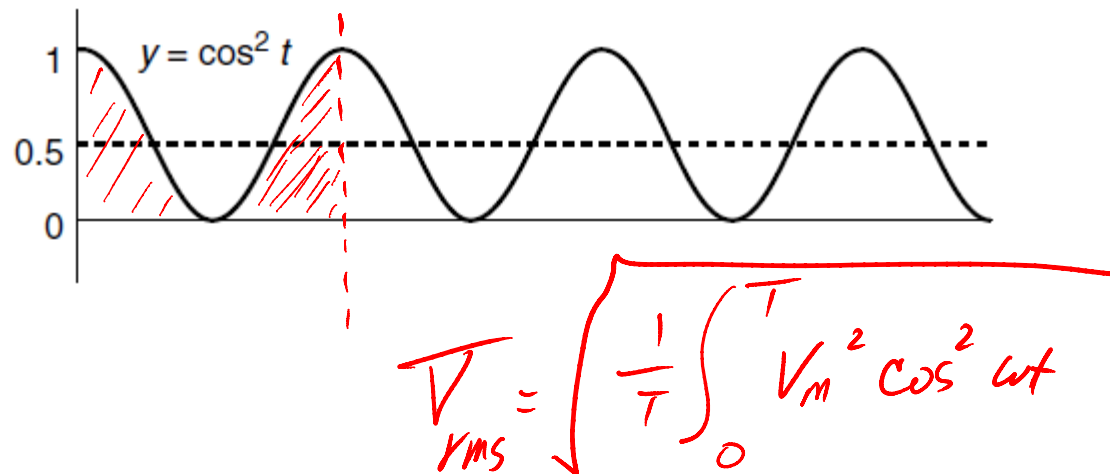

RMS value

⌘ RMS value of a sinusoidal voltage

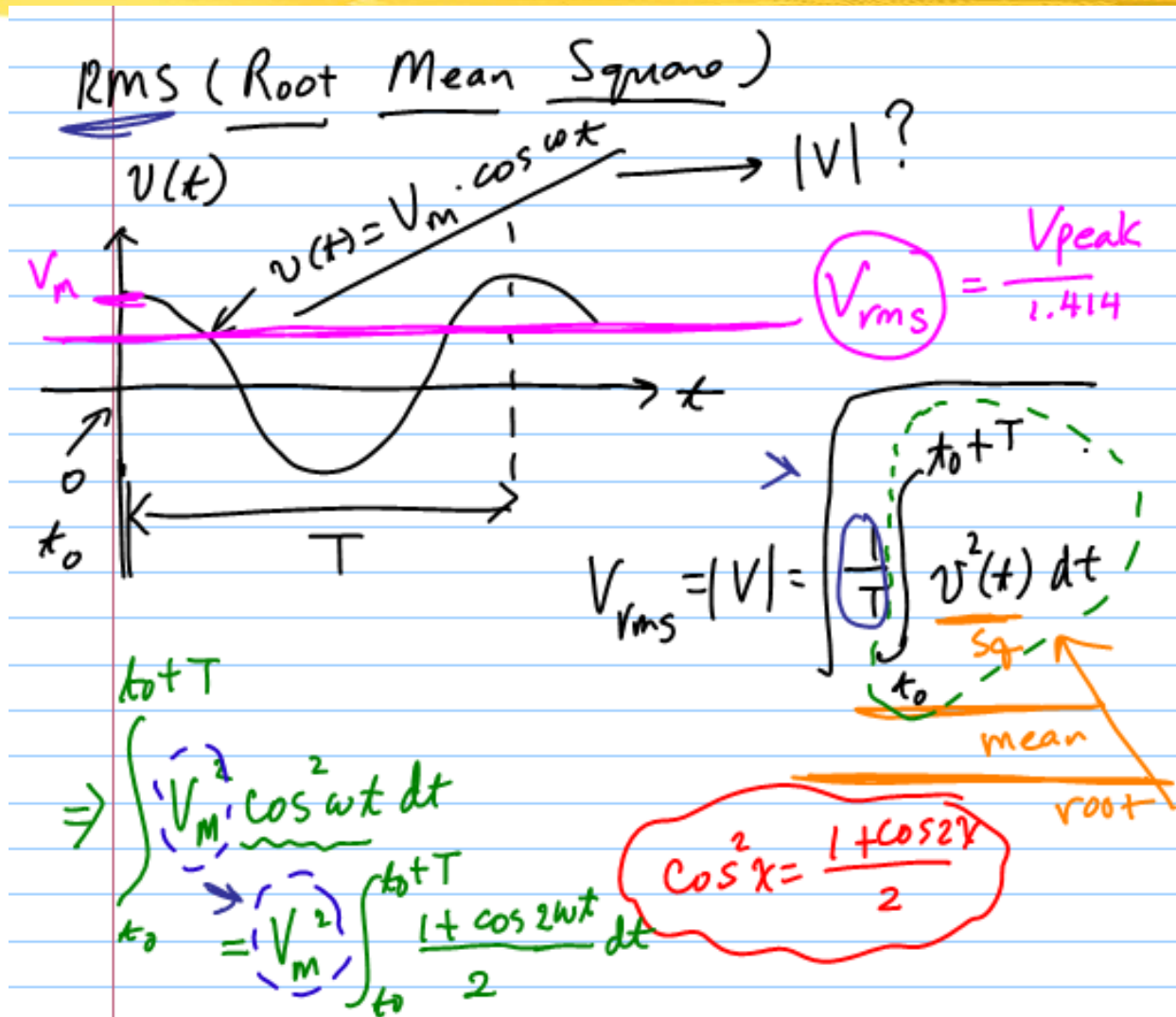

RMS value

⌘ RMS value of a sinusoidal voltage

$$\cos(x+y) = \cos x \cdot \cos y - \sin x \cdot \sin y$$

$$\cos(x-y) = \cos x \cdot \cos y + \sin x \cdot \sin y$$

$$\sin(x+y) = \sin x \cdot \cos y + \cos x \cdot \sin y$$

$$\sin(x-y) = \sin x \cdot \cos y - \cos x \cdot \sin y$$

$$\sin^2 x \rightarrow$$

$$\begin{aligned} \cos(x+x) &= \cos x \cdot \cos x - \sin x \cdot \sin x \\ &= \cos^2 x - \sin^2 x \\ &= \underbrace{\cos^2 x + \sin^2 x}_{=1} - 2 \cdot \sin^2 x \end{aligned}$$

$$\cos 2x = 1 - 2 \cdot \sin^2 x$$
$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

$$\cos^2 x = \frac{1 + \cos 2x}{2}$$

RMS value

⌘ RMS value of a sinusoid

$$\Rightarrow \int_{t_0}^{t_0+T} V_m^2 \cos^2 \omega t \, dt$$

$$= V_m^2 \int_{t_0}^{t_0+T} \frac{1 + \cos 2\omega t}{2} \, dt$$

$$= \int_{t_0}^{t_0+T} \frac{1}{2} \, dt + \int_{t_0}^{t_0+T} \frac{\cos 2\omega t}{2} \, dt$$

$$= \frac{1}{2} t \Big|_{t_0}^{t_0+T} + \frac{1}{4\omega} \left[\sin 2\omega t \right]_{t_0}^{t_0+T}$$

$$= \frac{T}{2} + \frac{1}{4\omega} \left[\sin \left[2\omega t_0 + 2\omega T \right] - \sin 2\omega t_0 \right]$$

$$= \frac{T}{2}$$

$$\underbrace{\sin 2\omega t_0}_{\sin 2\omega t_0} \quad \underbrace{2 \cdot 2\pi f \cdot T}_{= 4\pi} \quad f = \frac{1}{T}$$


$$\sin(x + 4\pi) = \sin x$$

$$V_{rms} = \sqrt{\frac{1}{T} V_m^2 \cdot \frac{T}{2}} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = \frac{\text{Peak Value}}{\sqrt{2}}$$

$$V_{rms} = V_m \sqrt{\frac{1}{2}} = \frac{V_m}{\sqrt{2}}$$

RMS value of a half-wave

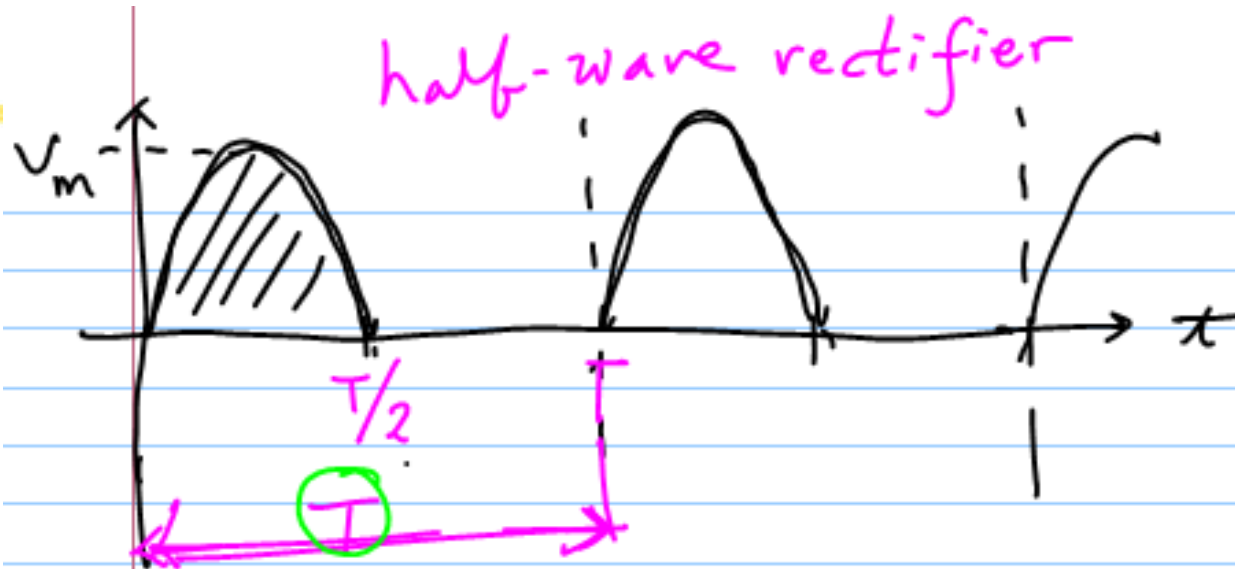

$$v = V_m \cdot \sin \frac{2\pi}{T} t, \quad 0 \leq t \leq T/2$$

RMS value of the above wave form?

cf. $\sin^2 x = \frac{1 - \cos 2x}{2}$

RMS & Magnitude

⌘ Magnitude is usually an RMS value as in

“We have 120 V 60-Hz available in the outlets”

120 → RMS → V_{rms}

⌘ Then, what is the instantaneous voltage equation? $v(t)$

$$v = V_m \cos \omega t$$

peak →

$$V_m = \sqrt{2} V_{\text{rms}} = 120\sqrt{2} = 169.7 \text{ V}$$


$$\omega = 2\pi f = 2\pi 60 = 377 \text{ rad/s}$$

$$v = 169.7 \cos 377t$$

Phasor



Phasor

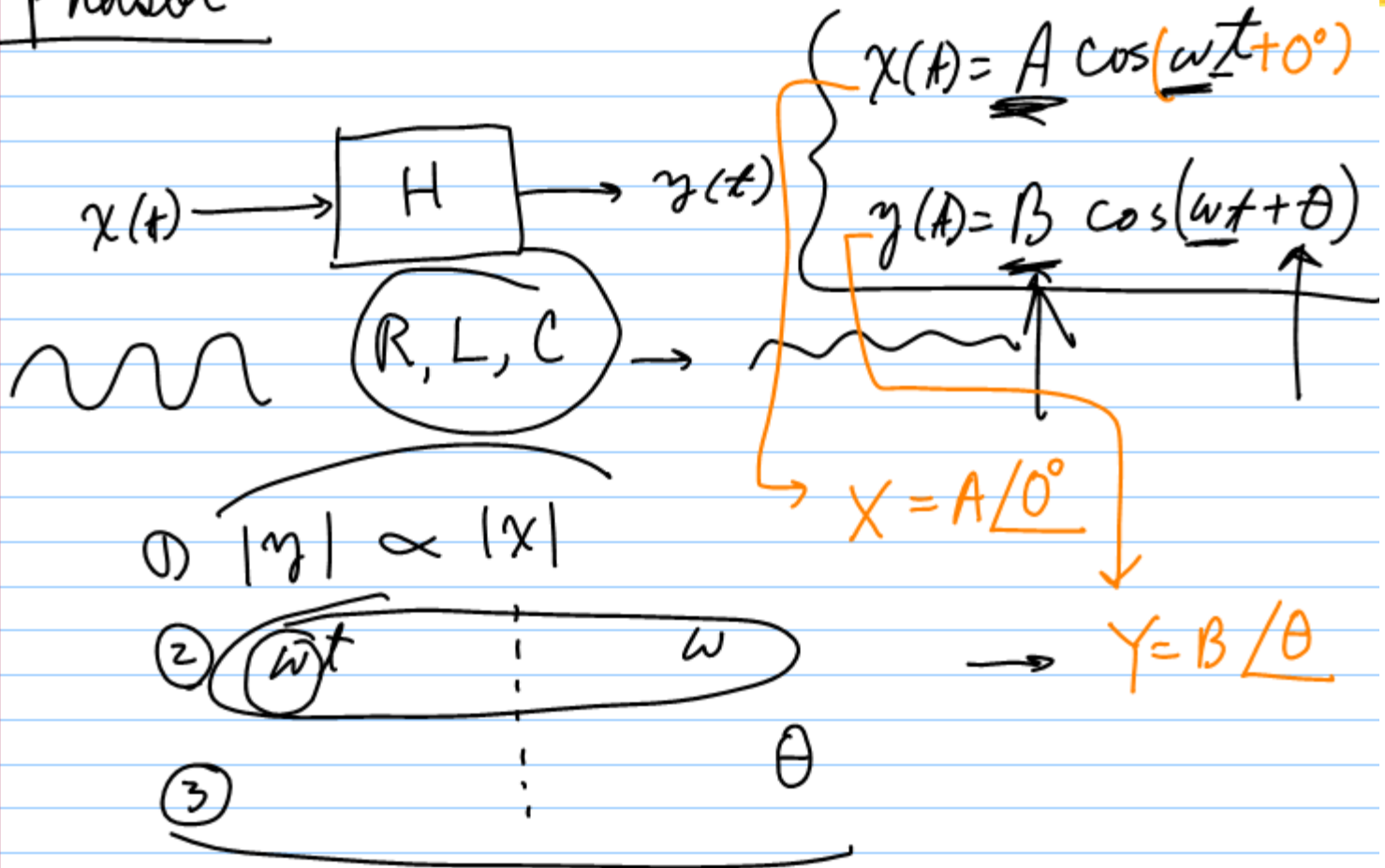

Phasor

$$v(t) = V_{\max} \cos(\omega t + \phi)$$

$$i(t) = I_{\max} \cos \omega t$$

lower case ; instantaneous value

lower case ; instantaneous value

$$V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}}$$

\bar{V} magnitude, Amplitude $|V|$ $|I|$

\bar{I}

\bar{V} complex phasor or $\bar{V} = 2 + j2$ rms

$\bar{V} = 2\sqrt{2} \angle 45^\circ$

$$\text{phasor} = \text{rms} \angle \theta$$

$$v = 141.4 \cos(\omega t + 30^\circ)$$

$$i = 7.07 \cos(\omega t + 0^\circ)$$

$$\bar{V} = \frac{141.4}{\sqrt{2}} \angle 30^\circ = 100 \angle 30^\circ \rightarrow \phi_v$$


$$\bar{I} = \frac{7.07}{\sqrt{2}} \angle 0^\circ = 5 \angle 0^\circ \leftarrow V_{\text{rms}} \phi_i$$

$$\phi = \phi_v - \phi_i = 30 - 0 = 30^\circ$$

$$\bar{V} = 100 \angle 30^\circ = 100 (\cos 30^\circ + j \sin 30^\circ)$$

$$= 100 \frac{\sqrt{3}}{2} + j 100 \cdot \frac{1}{2} = 86.6 + j 50$$
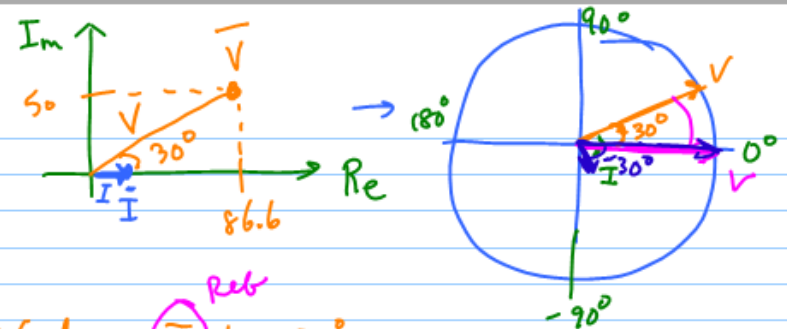
$$\bar{I} = 5 \angle 0^\circ = 5 (\cos 0^\circ + j \sin 0^\circ) = 5 + j 0$$




V leads I by 30°

I lags V by 30° \leftarrow Convention

Phasor

Complex Numbers

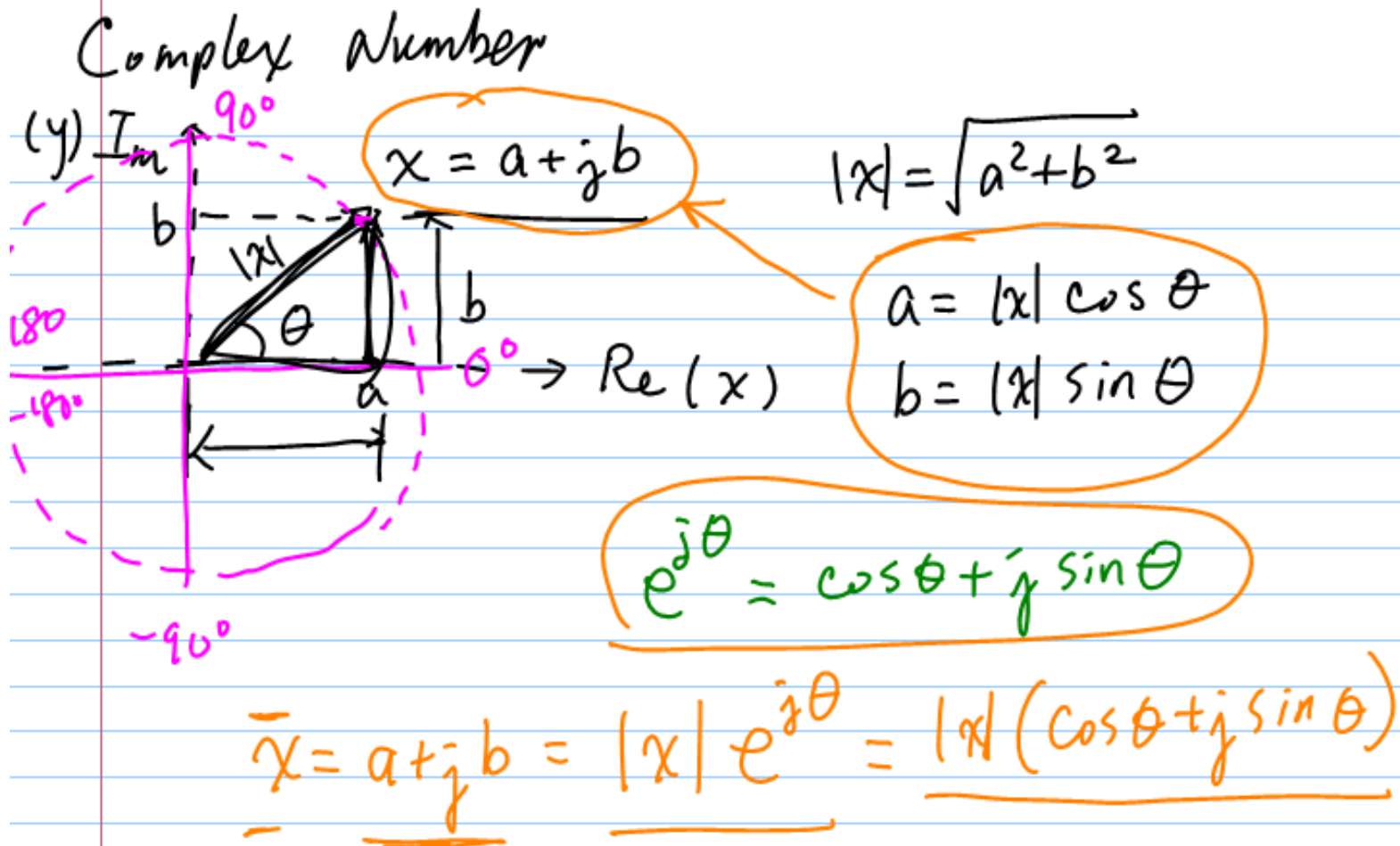

Phasor



$$\begin{aligned}\bar{x} &= 8 + j10 & \bar{x} + \bar{y} &= 13 + j6 \\ \bar{y} &= 5 - j4 & \bar{x} \cdot \bar{y} &= (8 + j10)(5 - j4) \\ & & &= 8 \cdot 5 + 8(-j4) + 5(j10) - j^2 40 \\ & & &= 40 - j32 + j50 + 40 = 80 + j16 = \square \angle \theta\end{aligned}$$

$$x = a \angle \theta_1 \quad y = b \angle \theta_2$$

$$xy = ab \angle \theta_1 + \theta_2$$

$$\frac{x}{y} = \frac{a \angle \theta_1}{b \angle \theta_2} = \frac{a}{b} \angle \theta_1 - \theta_2$$

$$\sqrt{80^2 + 16^2} \angle \tan^{-1} \frac{16}{80}$$

$$82 \angle 12.68^\circ$$

Instantaneous Power $p(t)$

Power in single-phase (1ϕ) circuit

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos(\omega t - \theta)$$


$$p(t) = v(t) i(t) = V_m I_m \cos \omega t \cdot \cos(\omega t - \theta)$$

$$\cos \alpha \cdot \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

$$= \frac{V_m I_m}{2} \{ \cos \theta + \cos(2\omega t - \theta) \}$$


$$\cos(\alpha - \beta) = \cos \alpha \cdot \cos \beta + \sin \alpha \cdot \sin \beta$$
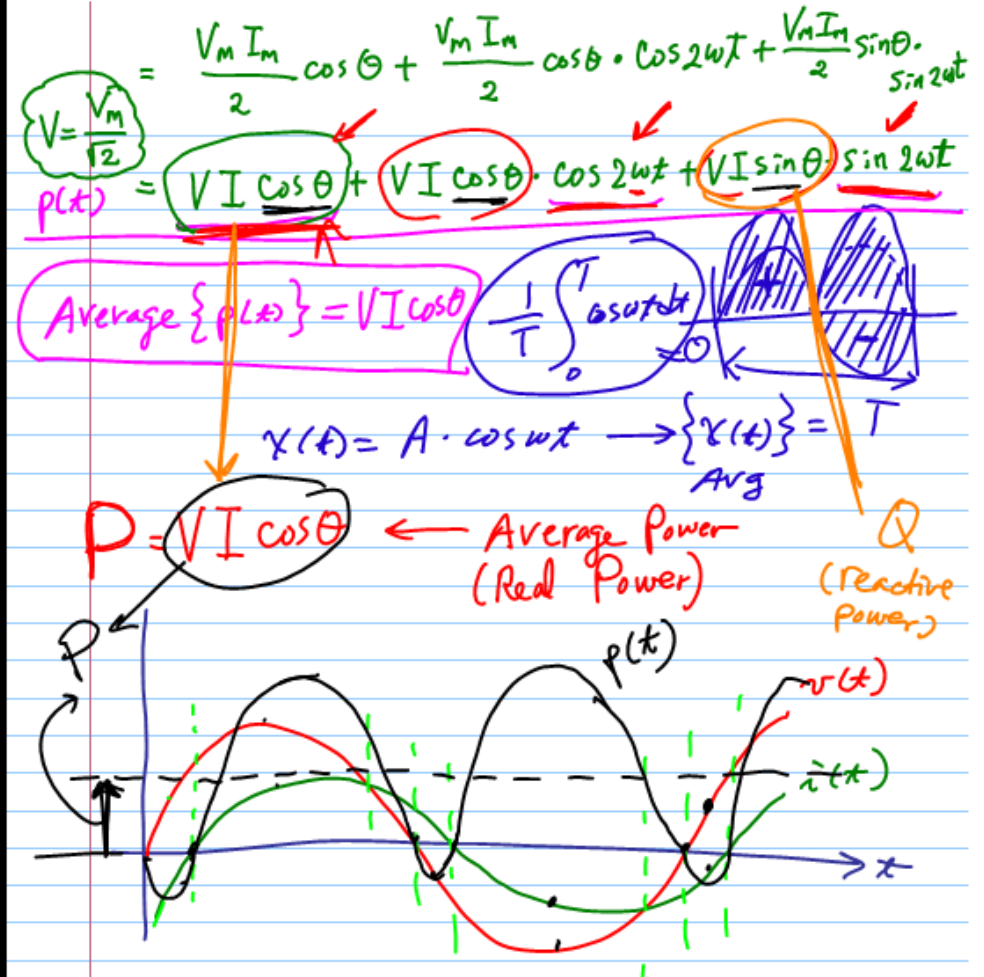
$$= \frac{V_m I_m}{2} \{ \cos \theta + \cos 2\omega t \cdot \cos \theta + \sin 2\omega t \cdot \sin \theta \}$$




$p(t)$ and S {Complex Power in Phasor}

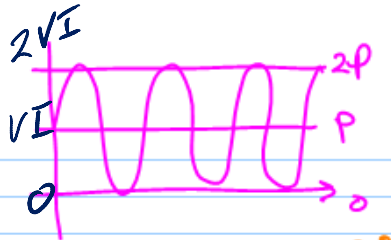
$\theta = 0^\circ, \cos\theta = 1, \sin\theta = 0$
 $p(t) = VI + VI \cos 2\omega t$
 $= VI(1 + \cos 2\omega t)$



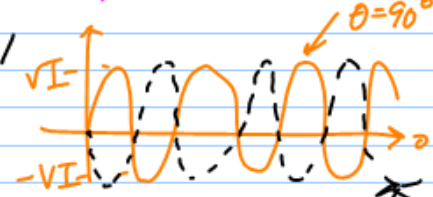
$\theta = 90^\circ, \cos\theta = 0, \sin\theta = 1$
 $p(t) = VI(\sin 2\omega t)$



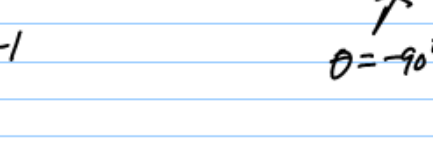$\theta = -90^\circ, \cos\theta = 0, \sin\theta = -1$
 $p(t) = -VI \sin 2\omega t$



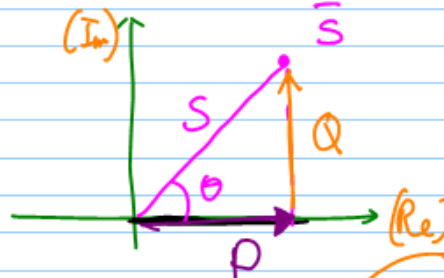$P = VI \cos\theta$ [W] $Q = VI \sin\theta$ [Var]
 $P + jQ = VI \{\cos\theta + j \sin\theta\} = VI \angle \theta = \bar{S}$
 Complex power



S : Apparent power

$S = \sqrt{P^2 + Q^2} = VI$
 $(VI)^2 \cos^2\theta + (VI)^2 \sin^2\theta = (VI)^2$

$P = VI \cos\theta, Q = VI \sin\theta$

P real power

$$p(t) = VI \cos\theta + VI \cos\theta \cdot \cos 2\omega t + VI \sin\theta \cdot \sin 2\omega t$$

Q reactive power

Circuit Elements in Phasor


$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

$v(t)$	\xrightarrow{P}	V	
$i(t)$	\xrightarrow{P}	I	\sim
✓ R	\xrightarrow{P}	R	$V = I(R)$
✓ L	\xrightarrow{P}	$j\omega L = \omega L \angle 90^\circ$	$\downarrow L$ $s f(s) - f(0)$
✓ C	\xrightarrow{P}	$\frac{1}{j\omega C} = -j \frac{1}{\omega C}$	\downarrow $s \leftarrow j\omega$

$$v = i(R)$$

$$v = L \left(\frac{di}{dt} \right)$$

$$v = L \frac{di}{dt}$$

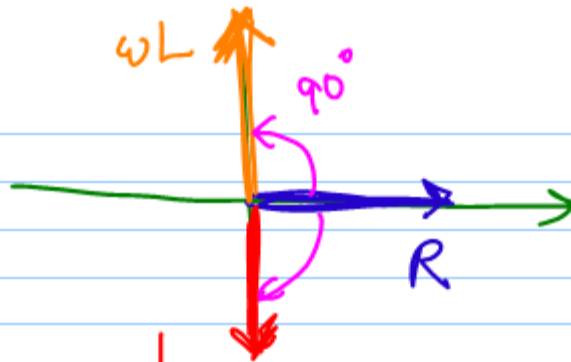




$$\cos \rightarrow \frac{di}{dt} = \sin$$

$$V(s) = L(s I(s) - i(0)) \rightarrow sL \rightarrow j\omega L$$

Phasor and Power Factor (pf)

$$\cos \theta = \frac{P}{\sqrt{P^2 + Q^2}} = \frac{P}{VI} \leftarrow \text{power factor}$$

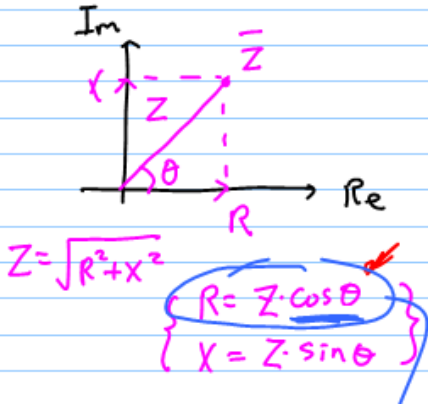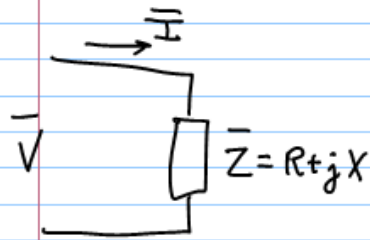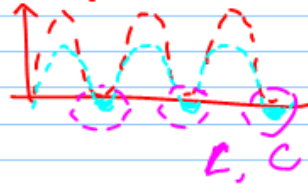$\text{pf} = \cos \theta = 1$
 $\cos \theta > .95$



$$P = VI \cos \theta$$

$$\bar{V} = \bar{I} \bar{Z} \quad \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{V \angle 0^\circ}{Z \angle \theta} = \frac{V}{Z} \angle -\theta$$

$$P = VI \cos \theta = I^2 Z \cos \theta = I^2 R$$


$$Q = VI \sin \theta = I^2 Z \sin \theta = I^2 X$$

$$\cos \theta = \frac{R}{Z} \leftarrow \text{power factor}$$

$$\text{pf} = \cos \theta$$


	P.F	Z
$\text{pf} = 1$	$\cos \theta = 1, \sin \theta = 0$	R only
$\text{pf} > 0$	$\cos \theta > 0, \sin \theta > 0$	$R \& L$
$\text{pf} < 0$	$\cos \theta > 0, \sin \theta < 0$	$R \& C$

Phasor

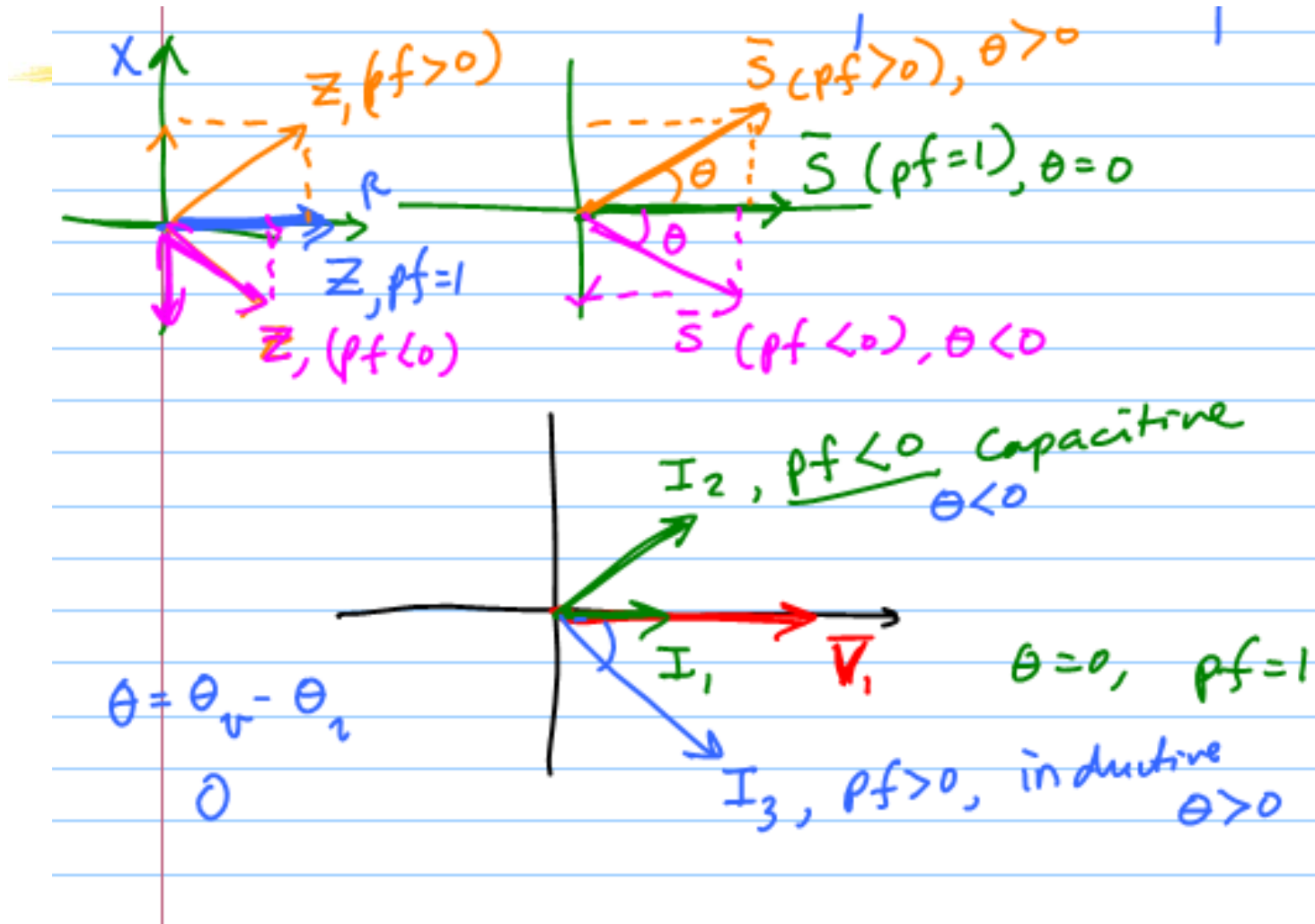


3-wire single-phase residential wiring

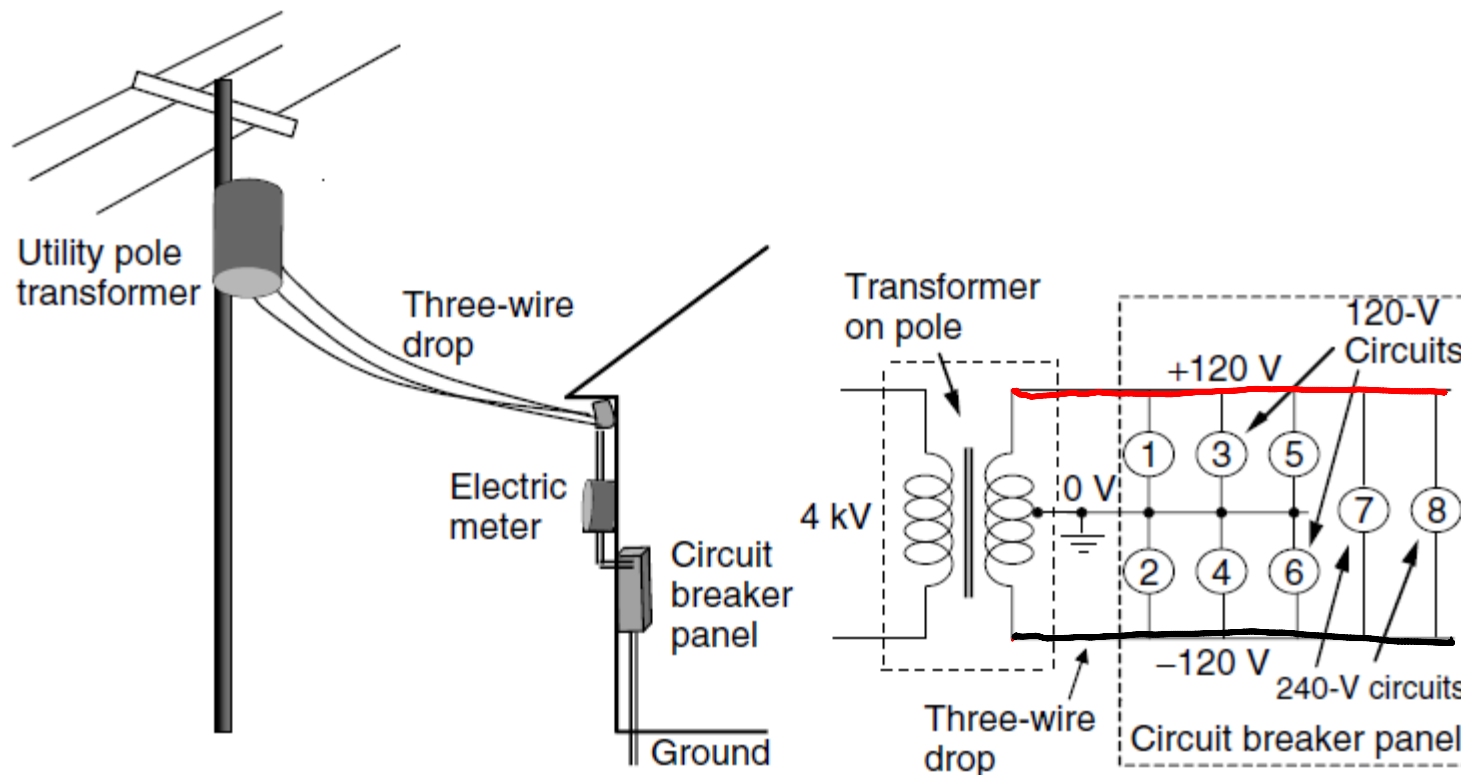- ⌘ Two "hot" sides (red and black)
- ⌘ Center-tapped ground (Neutral, white)



3-wire single-phase residential wiring

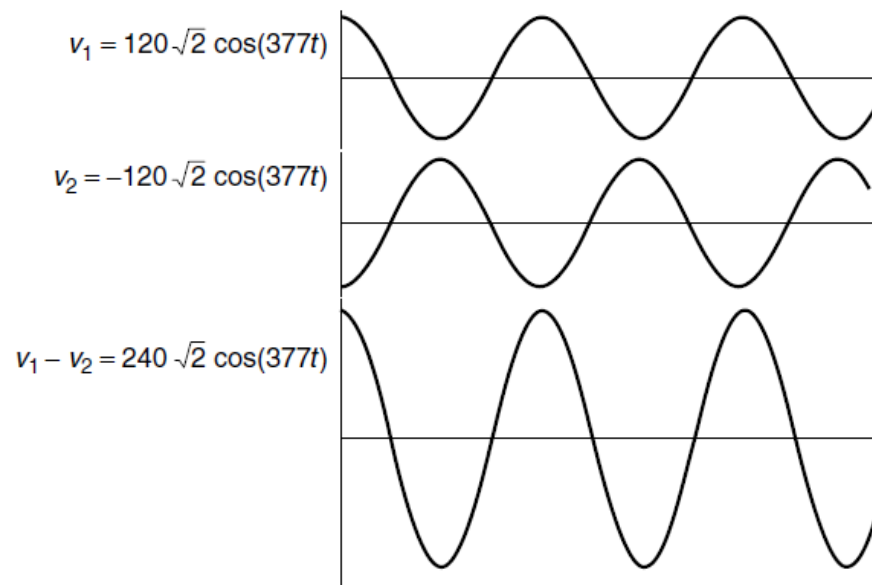- ⌘ Two "hot" sides (red and black)
- ⌘ Center-tapped ground (Neutral, white)



$$v_1 = 120\sqrt{2} \cos(2\pi \cdot 60t) = 120\sqrt{2} \cos 377t$$


$$v_2 = 120\sqrt{2} \cos(377t + \pi) = -120\sqrt{2} \cos 377t$$

$$v_1 - v_2 = 240\sqrt{2} \cos 377t$$

3-wire single-phase residential wiring - Example


⌘ Find the current in each of the three legs?

(RMS)

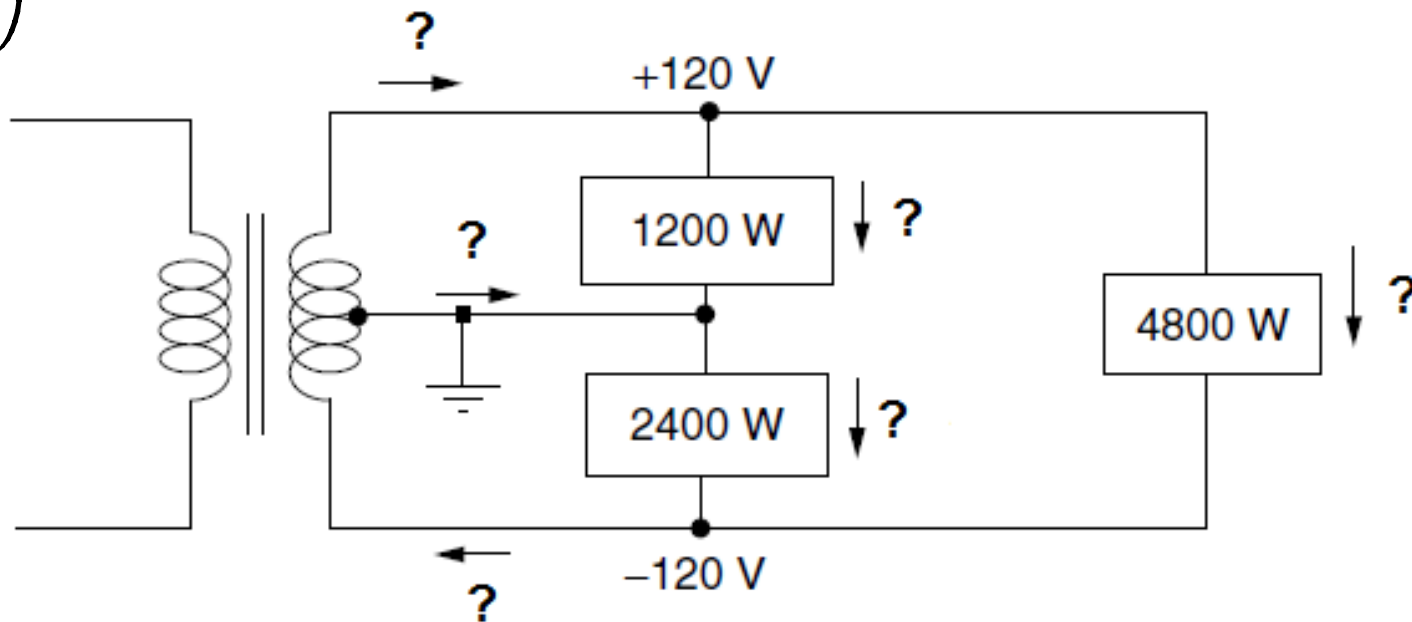


3-phase power systems


⌘ 3-phase power system

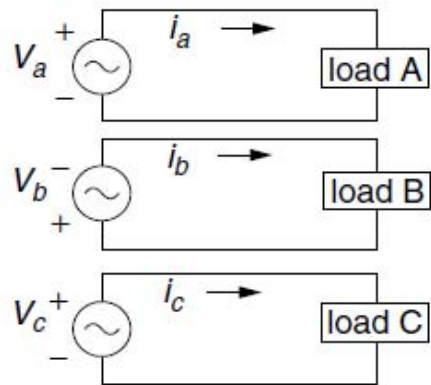

(a) Three separate circuits

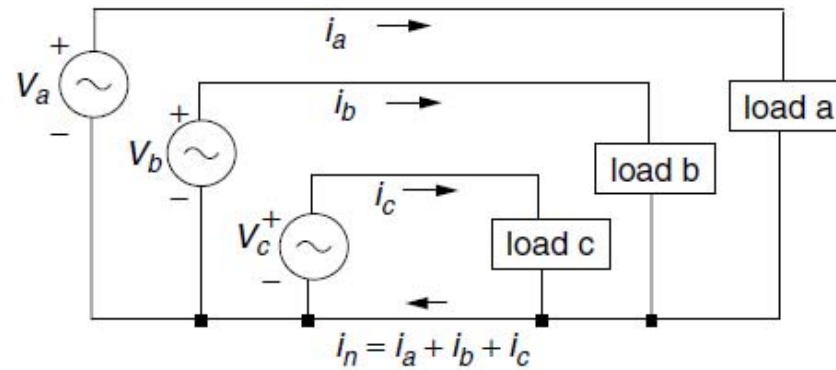

(b) Combined use of the neutral line

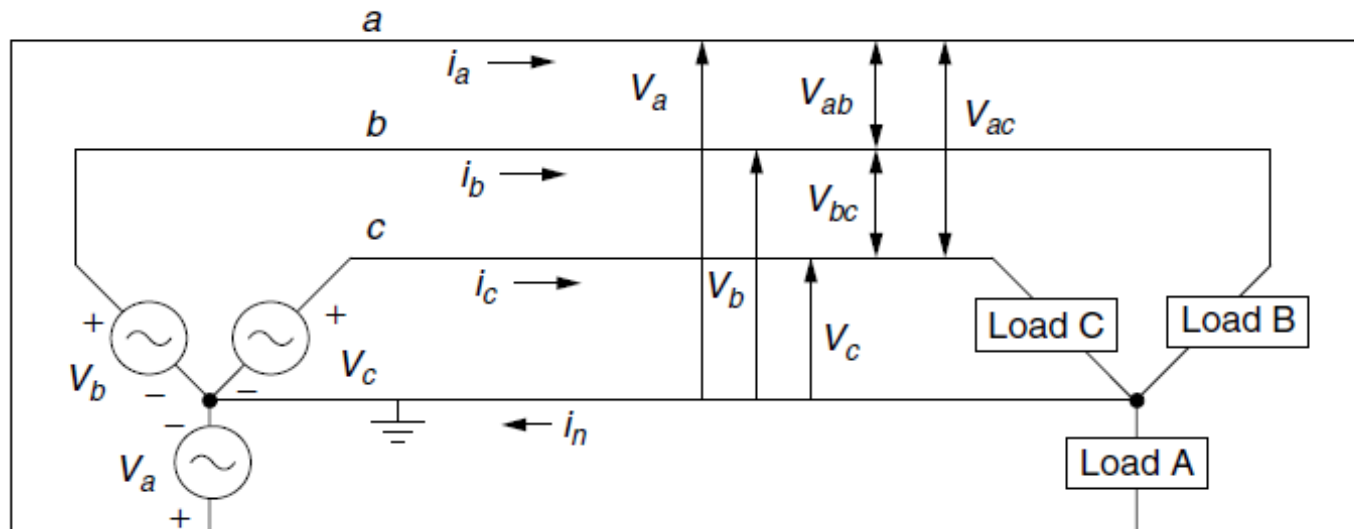


3-phase power systems

"Balanced 3- ϕ system"



: 3 ϕ generator

: 3 identical loads

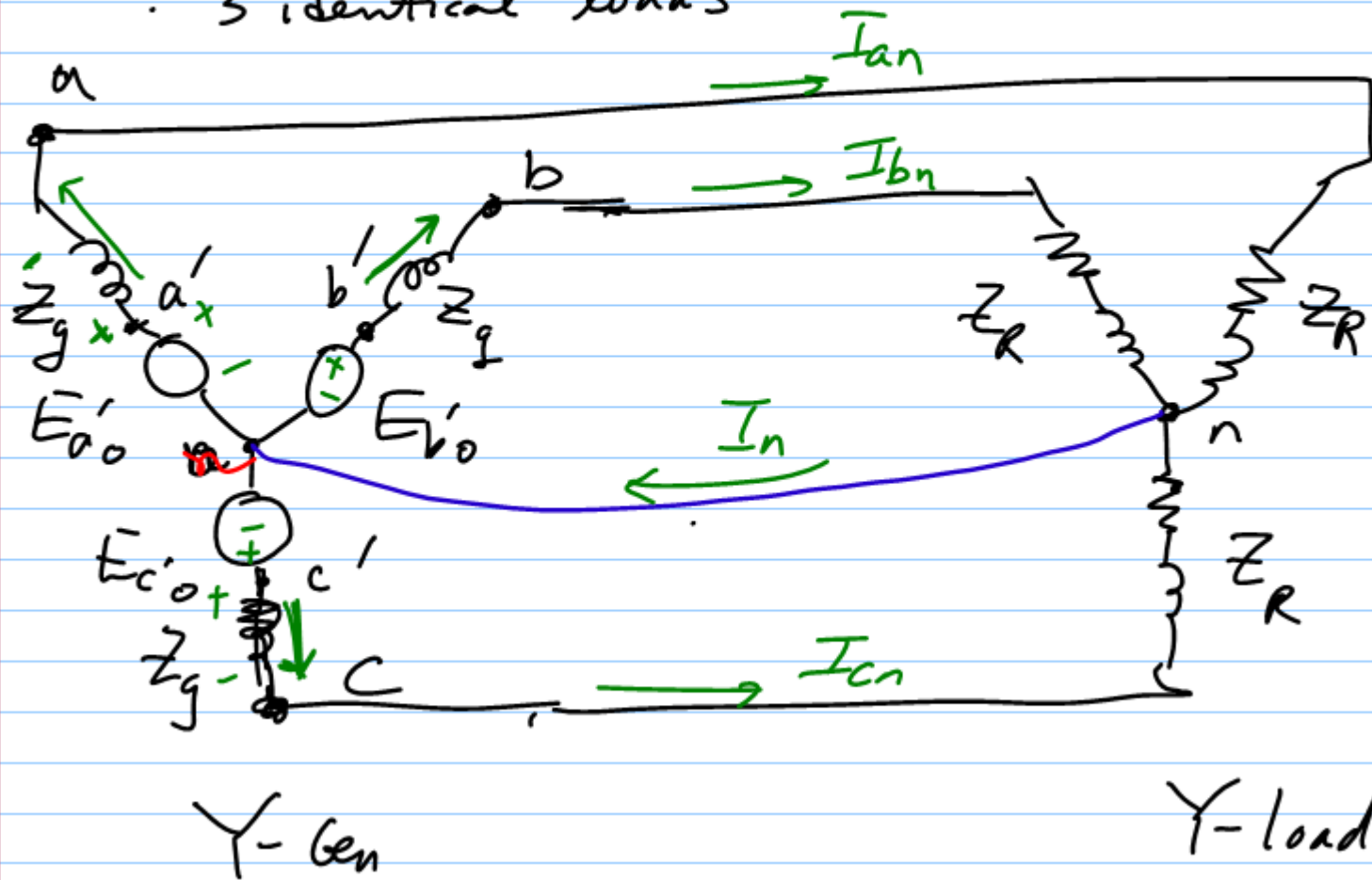

$$E_{a'_{R}} = E \angle 0^{\circ} \quad E_{b'_{R}} = E \angle -120^{\circ} \quad E_{c'_{R}} = E \angle 120^{\circ}$$

$$(\quad = E \angle 240^{\circ} \quad)$$

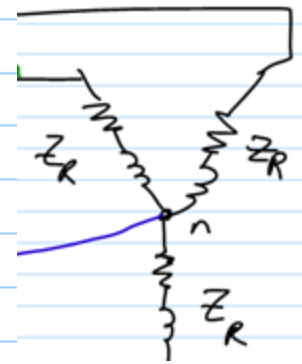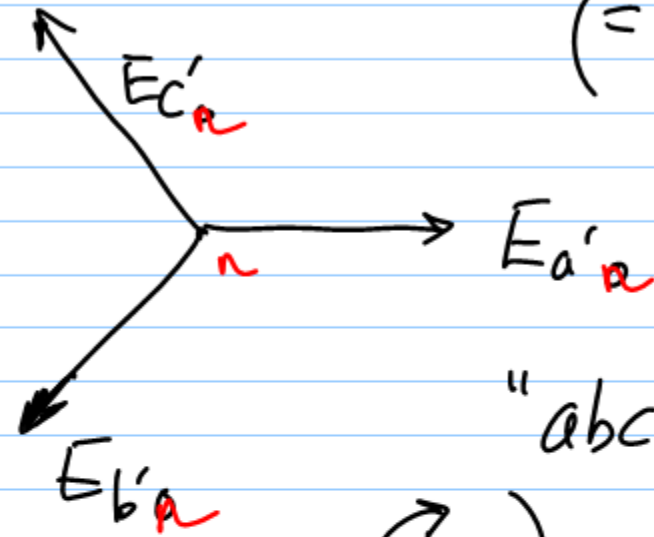

"abc-sequence"

V_{an}

(Gen)

(Load)

$$V_{aR} = E_{a'a} - I_{aR} Z_g$$

$$V_{an} = I_a Z_R \rightarrow I_{aR} = \frac{V_{an}}{Z_R}$$

$$V_{bR} = E_{b'a} - I_{bR} Z_g$$

$$V_{bn} = I_b Z_R \rightarrow I_{bR} = \frac{V_{bn}}{Z_R}$$

$$V_{cR} = E_{c'a} - I_{cR} Z_g$$

$$V_{cn} = I_c Z_R \rightarrow I_{cR} = \frac{V_{cn}}{Z_R}$$

3-phase power systems


$$E_{a'a} = I_a (Z_g + Z_R) \rightarrow I_a = \frac{E_{a'a}}{Z_g + Z_R} = \frac{V_{an}}{Z_R}$$

$$E_{b'a} = I_b (Z_g + Z_R) \rightarrow I_b = \frac{E_{b'a}}{Z_g + Z_R} = \frac{V_{bn}}{Z_R}$$

$$E_{c'a} = I_c (Z_g + Z_R) \rightarrow I_c = \frac{E_{c'a}}{Z_g + Z_R} = \frac{V_{cn}}{Z_R}$$

Since $E_{a'a}$, $E_{b'a}$, and $E_{c'a}$ are balanced,

I_a , I_b , & I_c are also balanced.

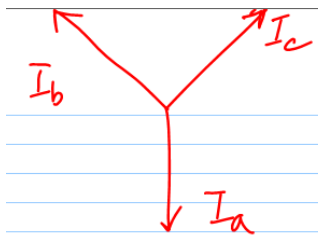


$$\text{and } \underline{I_a + I_b + I_c = 0}$$

$\rightarrow \underline{I_n = 0}$ No current
flow back to
generator.

3-phase power systems

Line-to-Line Voltage
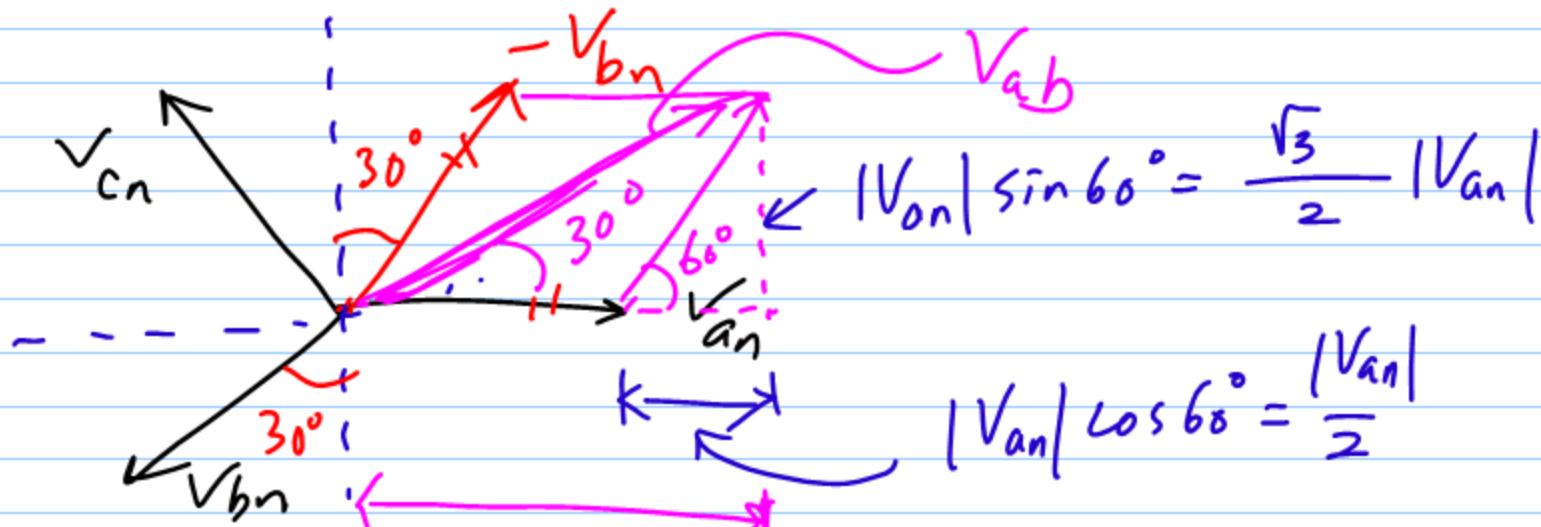
$$\vec{V}_{ab} = \vec{V}_{an} + \vec{V}_{nb} = \vec{V}_{an} - \vec{V}_{bn}$$




$$|V_{ab}| = \sqrt{\left(\frac{\sqrt{3}}{2} |V_{an}|\right)^2 + \left(\frac{3}{2} |V_{an}|\right)^2} = \sqrt{\frac{12}{4} |V_{an}|^2} = \sqrt{3} |V_{an}|$$



$$\Rightarrow \vec{V}_{ab} = \sqrt{3} \vec{V}_{an} \angle 30^\circ$$

$$\Rightarrow \vec{V}_{bc} = \sqrt{3} \vec{V}_{bn} \angle 30^\circ$$
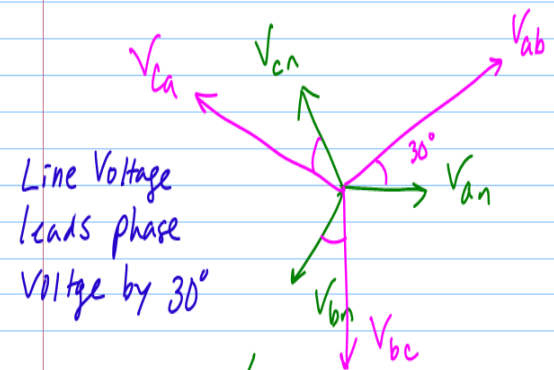
$$\Rightarrow \vec{V}_{ca} = \sqrt{3} \vec{V}_{cn} \angle 30^\circ$$



3-phase power systems

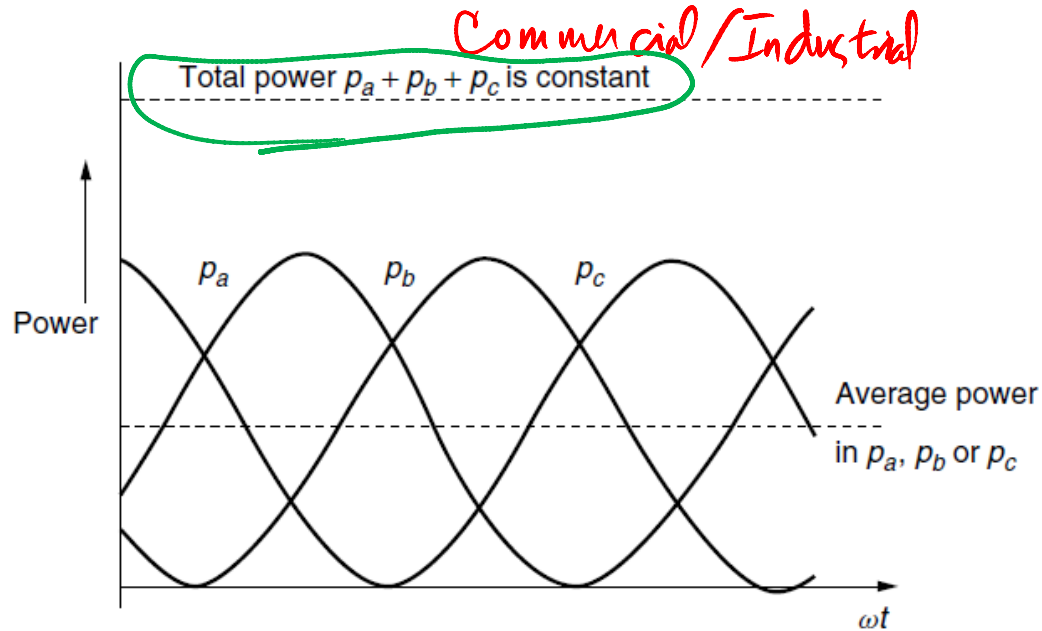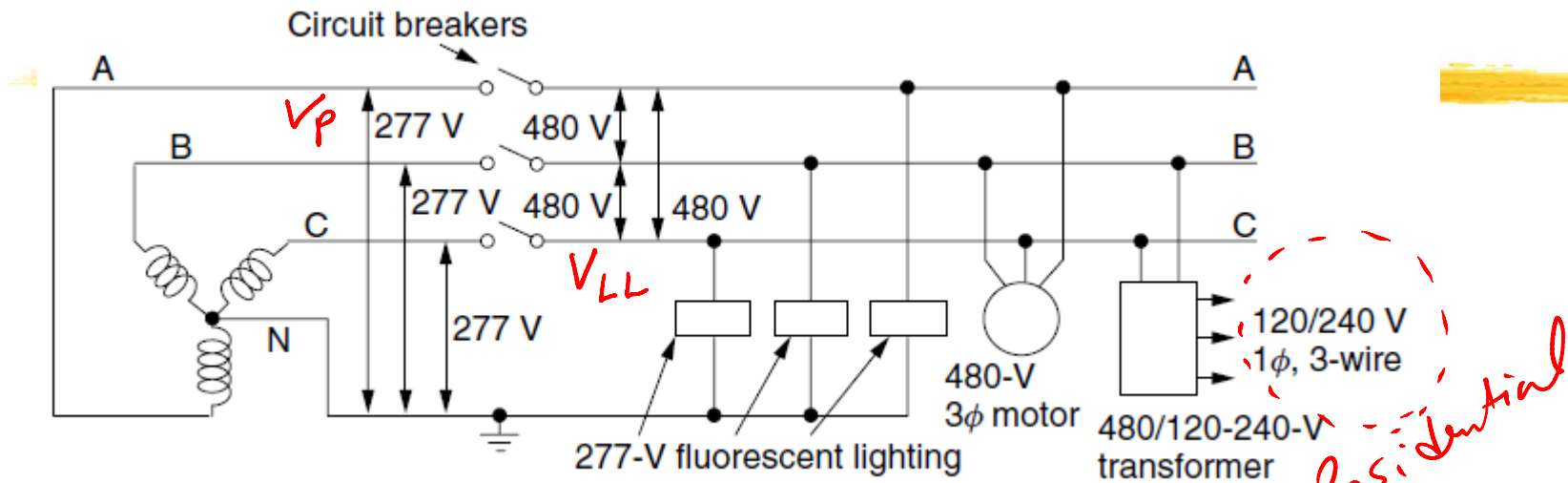

3-phase power systems

3 ϕ instantaneous power $P_3(t)$

$$v_a = V_m \cos \omega t$$

$$v_b = V_m \cos(\omega t - 120^\circ)$$

$$v_c = V_m \cos(\omega t + 120^\circ)$$

$$i_a = I_m \cos(\omega t - \theta)$$

$$i_b = I_m \cos(\omega t - \theta - 120^\circ)$$

$$i_c = I_m \cos(\omega t - \theta + 120^\circ)$$

$$P_{3\phi} = P_a(t) + P_b(t) + P_c(t)$$

$$= V_m I_m \cos \omega t \cdot \cos(\omega t - \theta)$$

$$+ V_m I_m \cos(\omega t - 120^\circ) \cdot \cos(\omega t - 120^\circ - \theta)$$

$$+ V_m I_m \cos(\omega t + 120^\circ) \cdot \cos(\omega t + 120^\circ - \theta)$$

3-phase power systems

From, 1 ϕ instantaneous power $P(t)$

Phase a:

$$P_a(t) = \frac{V_m I_m}{2} \cos \theta + \frac{V_m I_m}{2} \cos \theta \cdot \cos 2\omega t + \frac{V_m I_m}{2} \sin \theta \cdot \sin 2\omega t$$

Phase b:

$$P_b(t) = \frac{V_m I_m}{2} \cos \theta + \frac{V_m I_m}{2} \cos \theta \cdot \cos(2\omega t - 240^\circ)$$

$$\frac{V_m I_m}{2} \sin \theta \cdot \sin(2\omega t - 240^\circ)$$

3 phase power systems

Phase C:

$$P_c(t) = \frac{V_m I_m}{2} \cos \theta + \frac{V_m I_m}{2} \cos \theta \cdot \cos(2\omega t + 240^\circ)$$

$$\frac{V_m I_m}{2} \sin \theta \cdot \sin(2\omega t + 240^\circ)$$

$$P_3(t) = P_a(t) + P_b(t) + P_c(t)$$

$$= 3 \left(\frac{V_m I_m}{2} \cos \theta \right) + \frac{V_m I_m}{2} \cos \theta \left\{ \cancel{\cos 2\omega t} + \cos(2\omega t - 240^\circ) + \cos(2\omega t + 240^\circ) \right\}$$

$$+ \frac{V_m I_m}{2} \sin \theta \left\{ \cancel{\sin 2\omega t} + \sin(2\omega t - 240^\circ) + \sin(2\omega t + 240^\circ) \right\}$$


3-phase power systems

$$= 3 \frac{V_m I_m}{2} \cos \theta$$

$$= 3 |V| |I| \cos \theta$$

Constant !!
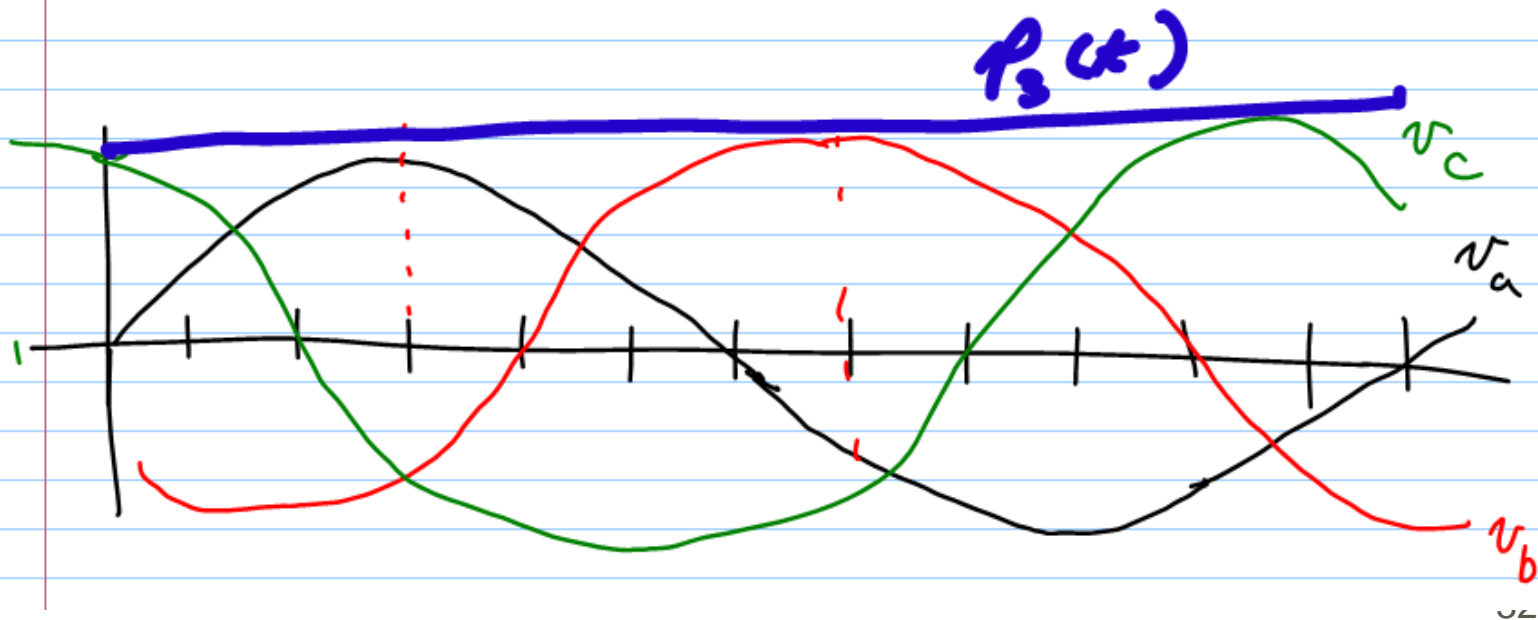
$$\underline{\underline{P_3(t) = \text{Constant}}}$$



Power in Balanced 3- ϕ Circuits

$$P_{3\phi} = P_a + P_b + P_c$$

$$= 3 \cdot P_a \quad (\text{in Balanced System})$$

V_p : phase voltage magnitude to neutral

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

I_p : phase current magnitude for Y-Load

$$I_p = |I_{an}| = |I_{bn}| = |I_{cn}|$$

θ_p : phase angle between \vec{V}_p & \vec{I}_p
: angle to the impedance $\longrightarrow \theta_Z$

3-phase power systems

$$\Rightarrow P_{3\phi} = 3 V_p I_p \cos \theta_p$$

V_L : Line-to-Line Voltage Magnitude or 1 ϕ eqn

$$V_p = \frac{V_L}{\sqrt{3}} \quad \text{and} \quad I_p = I_L \quad (\text{Y-load case})$$

current over
a line

$$I_L = I_p \sqrt{3}$$

Δ Load case

$$\Rightarrow P_{3\phi} = 3 V_p I_p \cos \theta_p$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$$

$$\& Q_{3\phi} = 3 V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$$



3-phase power systems

Further,

$$S_{3\phi} = P_{3\phi} + j Q_{3\phi}$$

$$\begin{aligned} |S_{3\phi}| &= \sqrt{P_{3\phi}^2 + Q_{3\phi}^2} = \sqrt{3} V_L I_L \\ &= 3 V_p I_p \end{aligned}$$

LAB

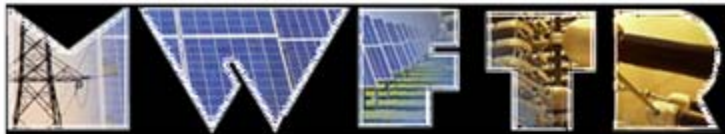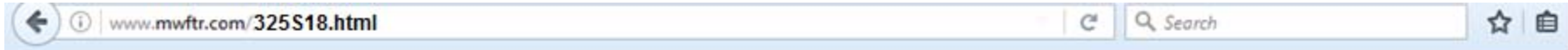

Lab Manual/Handout:

1. Check the web for Lab manual
2. Printout and Read before coming to the lab
3. Report --- Write on the Lab manual & Submit
1 week after

EECE325 Fundamentals of Energy Systems + Lab (EECE326)

[Course Introduction](#) (for 325 and 326)

EECE325 - Lecture	EECE326 - Lab
Syllabus	Syllabus
Subject 1: Background	Lab 1 -- Safety and Power Supply
Chapter 2	Lab 2 -- Phase Sequence
	Lab 3 -- Real and Reactive Power
Subject 2: Power Industry and Distributed Generation	Lab 4 -- Power Flow
Chapter 3	Lab 5 -- Phase Angle and Voltage Drop
Chapter 4	Lab 6 -- Synchronous Machine
Subject 3: Wind Electricity Generation	Lab 7 -- Wind Power Generation
Chapter 6	Lab 8 -- Power Inverter
Subject 4: Photovoltaic Electricity Generation	
Chapter 7	Lab 9 -- PV Systems
Chapter 8	Lab 10 -- Battery Systems
Chapter 9	Lab 11 -- Additional Lab

LAB1



326Lab1_Safety and Power Su...

