

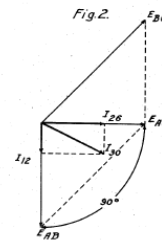


Lab 3 – Real Power & Reactive Power

- ⌘ Real Power (P) [Watt] [W] $V|I| \cos \theta$
- ⌘ Reactive Power (Q) [Var] $V|I| \sin \theta$
- ⌘ Complex Power (S) = P + jQ
- ⌘ Apparent Power (|S|) = $\sqrt{P^2 + Q^2}$

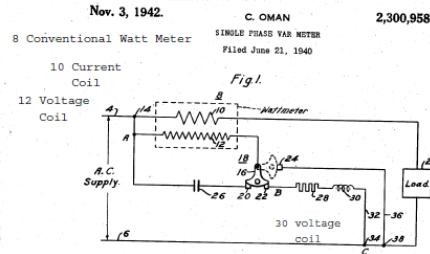

3-phase power: P and Q

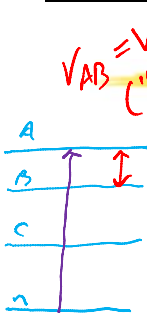

$V_{An} \rightarrow V_p$
 "phase voltage"
 $V_{AB} \rightarrow V_L$
 "line-to-neutral voltage"

$V_{AB} = V_L$ ("Line voltage")
 $\Rightarrow P_{3\phi} = 3 V_p I_p \cos \theta_p$

V_L : Line-to-Line Voltage magnitude

$V_p = \frac{V_L}{\sqrt{3}}$ and $I_p = I_L$ (Y-load case)

$I_L = I_p \sqrt{3}$ (Delta load case)

$\Rightarrow P_{3\phi} = 3 V_p I_p \cos \theta_p$
 $= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$


$\& Q_{3\phi} = 3 V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$

P and Q & R and X

$\cos\theta = \frac{P}{\sqrt{P^2+Q^2}} = \frac{P}{VI}$ ← power factor
 $\text{pf} = \cos\theta = 1$ (circled)
 $\cos\theta > .95$ (circled)

$Z = R + jX$
 $Z = \sqrt{R^2 + X^2}$
 $R = Z \cos\theta$
 $X = Z \sin\theta$

$P = VI \cos\theta$

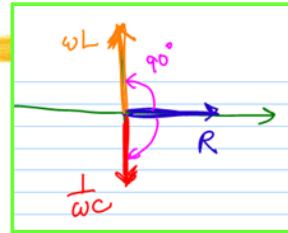

$$Z = R + jX = R + j(X_L - X_C)$$

$$X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$


$\vec{V} = \vec{I} \vec{Z} \quad \vec{I} = \frac{\vec{V}}{\vec{Z}} = \frac{V \angle 0^\circ}{Z \angle \theta} = \frac{V}{Z} \angle -\theta$
 $P = VI \cos\theta = I^2 Z \cos\theta = I^2 R$
 $Q = VI \sin\theta = I^2 Z \sin\theta = I^2 X$
 $\cos\theta = \frac{R}{Z}$ ← power factor

3



P and Q with Z

$P = VI \cos\theta$



$Q = VI \sin\theta$

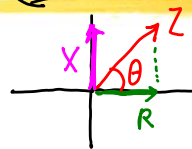

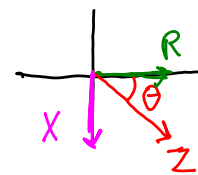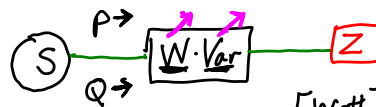
$R = 5 \quad X = 5 \quad \theta = 45^\circ$
 $P > 0 \quad Q > 0$



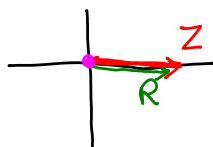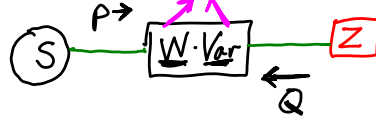$R = 5 \quad X = -5 \quad \theta = -45^\circ$
 $P > 0 \quad Q < 0$




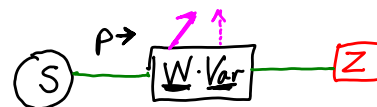$R = 5 \quad X = 0 \quad \theta = 0$
 $P > 0 \quad Q = 0$



4

Example LAB 3 -- EXAMPLE CALCULATION

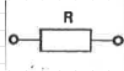

$$P_{3\phi} = 3V_p I_p \cos \theta_p$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$$

$$Q_{3\phi} = 3V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$$

VP=120

VL=VP*sqrt(3)=207.846097

R=300

Z=R |Z|=300

theta=arg(Z)=0

IL=VP/Z=0.4 We measure this in the lab

|IL|=0.4

P=3*|VP|*|IL|*cos(theta)=144

P=sqrt(3)*|VL|*|IL|*cos(theta)=144 W

Q=sqrt(3)*|VL|*|IL|*sin(theta)=0 Var

→
P
Q=0

Example



$$P_{3\phi} = 3V_p I_p \cos \theta_p$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$$

$$Q_{3\phi} = 3V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$$

VP=120

VL=VP*sqrt(3)=207.846097

R=0 XL=300

Z=R+i*XL |Z|=300

theta=arg(Z)=1.570796

theta deg = theta * 180 / pi = 90

IL=VP/Z=-0.4*i We measure this in the lab


|IL|=0.4

P=sqrt(3)*|VL|*|IL|*cos(theta)=-5.027736*10^-13 W

Q=sqrt(3)*|VL|*|IL|*sin(theta)=144 Var

0
P=0
Q →

Example

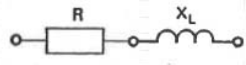

$$P_{3\phi} = 3V_p I_p \cos \theta_p$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$$

$$Q_{3\phi} = 3V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$$

$$V_P = 120$$

$$V_L = V_P \cdot \sqrt{3} = 207.846097$$

$$R = 300$$

$$X_L = 300$$

$$Z = R + i \cdot X_L$$

$$|Z| = 424.264069$$

$$\theta = \arg(Z) = 0.785398$$

$$\theta_{deg} = \theta \cdot \frac{180}{\pi} = 45$$

$$I_L = \frac{V_P}{Z} = 0.2 - 0.2 \cdot i$$

We measure this in the lab

$$|I_L| = 0.282843$$

$$P = \sqrt{3} |V_L| |I_L| \cos(\theta) = 72 \quad \text{W}$$


$$Q = \sqrt{3} |V_L| |I_L| \sin(\theta) = 72 \quad \text{Var}$$

$P \rightarrow$

$Q \rightarrow$

7

Example

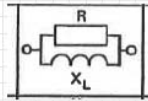

$$P_{3\phi} = 3V_p I_p \cos \theta_p$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$$

$$Q_{3\phi} = 3V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$$

$$V_P = 120$$

$$V_L = V_P \cdot \sqrt{3} = 207.846097$$

$$R = 300$$

$$X_L = 300$$

$$X = i \cdot X_L$$

$$Z = \frac{R \cdot X}{R + X} = 150 + 150 \cdot i$$

$$|Z| = 212.132034$$

$$\theta = \arg(Z) = 0.785398$$

$$I_L = \frac{V_P}{Z} = 0.4 - 0.4 \cdot i$$

$$\theta_{deg} = \theta \cdot \frac{180}{\pi} = 45$$

We measure this in the lab

$$|I_L| = 0.565685$$

$$P = 3 |V_P| |I_L| \cos(\theta) = 144$$

$$P = \sqrt{3} |V_L| |I_L| \cos(\theta) = 144 \quad \text{W}$$

$$Q = \sqrt{3} |V_L| |I_L| \sin(\theta) = 144$$

Var

$P \rightarrow$

$Q \rightarrow$