

- 1 SENDER AND RECEIVER VOLTAGES UNEQUAL BUT IN PHASE
- 2 SENDER AND RECEIVER VOLTAGES EQUAL BUT OUT OF PHASE
- 3 SENDER AND RECEIVER VOLTAGES UNEQUAL AND OUT OF PHASE

$V_{mS} := 30000$ $\theta_S := 10 \text{ deg}$ $\theta_R := 0$ $Z_t := 0 + i \cdot 100$ Line Impedance

$V_{mR} := 25000$

try to change

$V_S := V_{mS} \cdot e^{i \cdot \theta_S \cdot \frac{\pi}{180}} = 29544.2326 + 5209.4453 \cdot i$ $|V_S| = 30000$ $\arg(V_S) \cdot \frac{180}{\pi} = 10 \text{ deg}$

$V_R := V_{mR} \cdot e^{i \cdot \theta_R \cdot \frac{\pi}{180}} = 25000$ $|V_R| = 25000$ $\arg(V_R) \cdot \frac{180}{\pi} = 0 \text{ deg}$

$V_t := V_S - V_R = 4544.2326 + 5209.4453 \cdot i$ $|V_t| = 6912.9133$ $\arg(V_t) \cdot \frac{180}{\pi} = 48.9016$

$I := \frac{V_S - V_R}{Z_t} = 52.0945 - 45.4423 \cdot i$ $|I| = 69.1291$ $\arg(I) \cdot \frac{180}{\pi} = -41.0984$

$$SS := VS \cdot (\operatorname{Re}(I) - i \cdot \operatorname{Im}(I)) = 1.3024 \cdot 10^6 + 1.6139 \cdot 10^6 \cdot i$$

Complex Power at Sender

$$SR := VR \cdot (\operatorname{Re}(I) - i \cdot \operatorname{Im}(I)) = 1.3024 \cdot 10^6 + 1.1361 \cdot 10^6 \cdot i$$

Complex Power at Receiver

$$St := (VS - VR) \cdot (\operatorname{Re}(I) - i \cdot \operatorname{Im}(I)) = 4.7788 \cdot 10^5 \cdot i$$

Complex Power in the Line

$$pSS := \operatorname{Re}(SS) = 1.302361 \cdot 10^6$$

$$pSt := \operatorname{Re}(St) = 0$$

$$pSR := \operatorname{Re}(SR) = 1.302361 \cdot 10^6$$

$$qSS := \operatorname{Im}(SS) = 1.613942 \cdot 10^6$$


$$qSt := \operatorname{Im}(St) = 4.778837 \cdot 10^5$$

$$qSR := \operatorname{Im}(SR) = 1.136058 \cdot 10^6$$

$$S := \begin{bmatrix} 0 & 0 \\ \frac{pSS}{10^6} & \frac{qSS}{10^6} \end{bmatrix}$$

$$R := \begin{bmatrix} 0 & 0 \\ \frac{pSR}{10^6} & \frac{qSR}{10^6} \end{bmatrix}$$
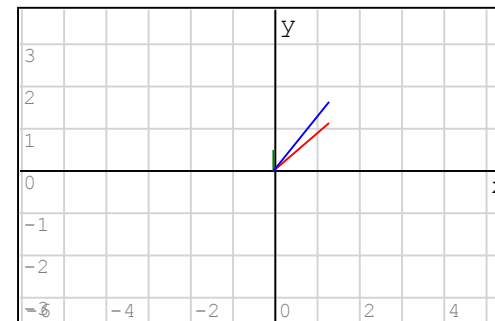
$$t := \begin{bmatrix} 0 & 0 \\ \frac{pSt}{10^6} & \frac{qSt}{10^6} \end{bmatrix}$$



$$\left. \begin{array}{l} S \\ R \\ t \end{array} \right\}$$