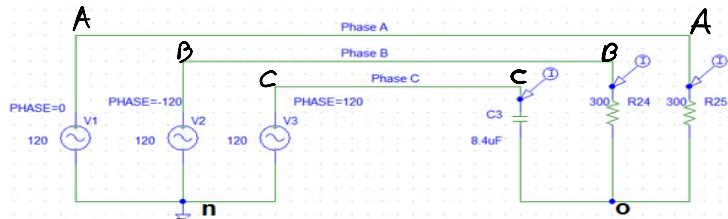


Lab 2 – Phase sequence determination


- ⌘ How to find a sequence of Phase (ABC, ACB) when there is no marking
- ⌘ Use unbalanced load situation



Balanced Source

V_{an}, V_{bn}, V_{cn}

$$V_{an} + V_{bn} + V_{cn} = 0$$

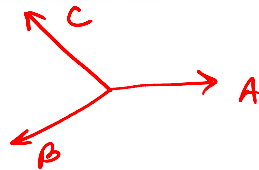

Unbalanced Load

Balanced Line-to-Line Voltage

V_{ab}, V_{bc}, V_{ca}

Unbalanced Line-to-point voltage

V_{ao}, V_{bo}, V_{co}


$$V_{ao} + V_{bo} + V_{co} \neq 0$$

$$I_a + I_b + I_c = 0$$

So there is voltage developed between n and o

1

Lab 2 – Phase sequence determination

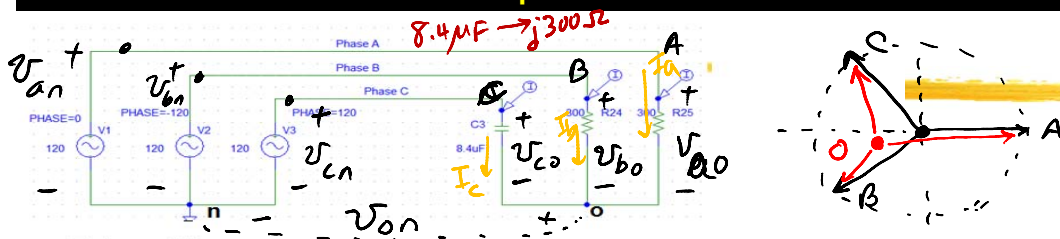

$$V_{ao} = V_{an} - V_{on}$$

$$V_{bo} = V_{bn} - V_{on}$$

$$V_{co} = V_{cn} - V_{on}$$

$$V_{ao} = I_a \cdot R$$

$$V_{bo} = I_b \cdot R$$

$$V_{co} = I_c \cdot (-jR)$$

$$I_a \cdot R = V_{an} - V_{on}$$


$$I_b \cdot R = V_{bn} - V_{on}$$

$$I_c \cdot (-jR) = V_{cn} - V_{on}$$

$$C \rightarrow \frac{1}{j\omega C} = -j\left(\frac{1}{\omega C}\right) \quad \text{Cap. reactance}$$


2

Lab 2 – Phase sequence determination

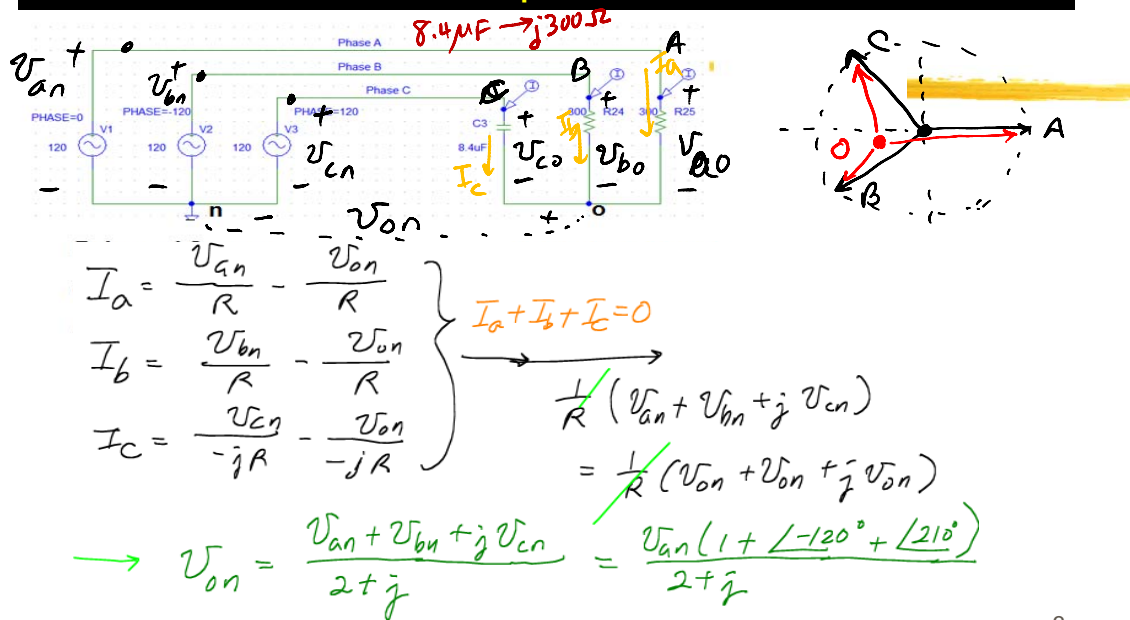

3


Lab 2 – Phase sequence determination

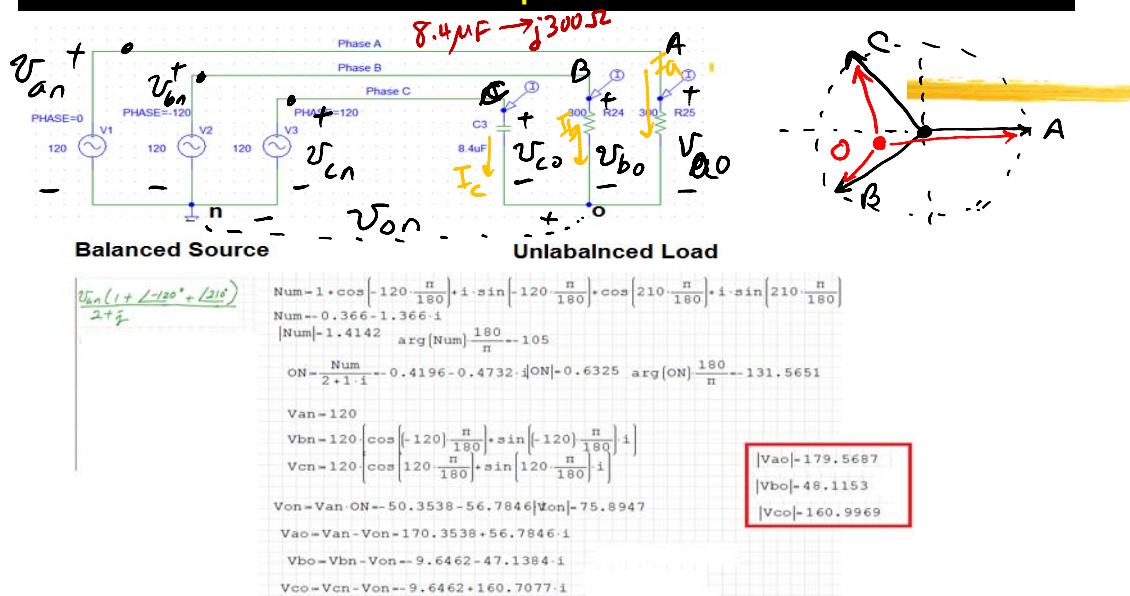

4

Lab 2 – Phase sequence determination


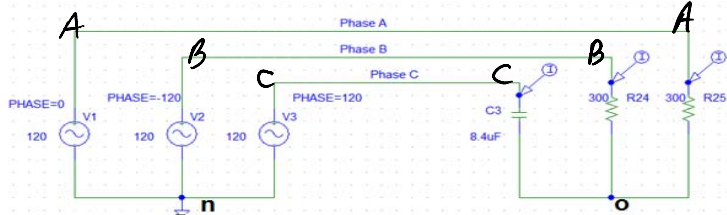
- How to find a sequence of Phase (ABC, ACB) when there is no marking
- Use unbalanced load situation



Phase sequence Rule

High - Low - C



(A) (B) (C)

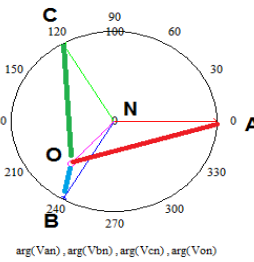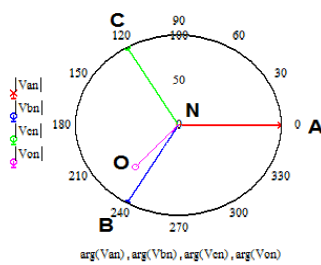

AO > BO


5

Lab 2 – Phase Sequence Determination

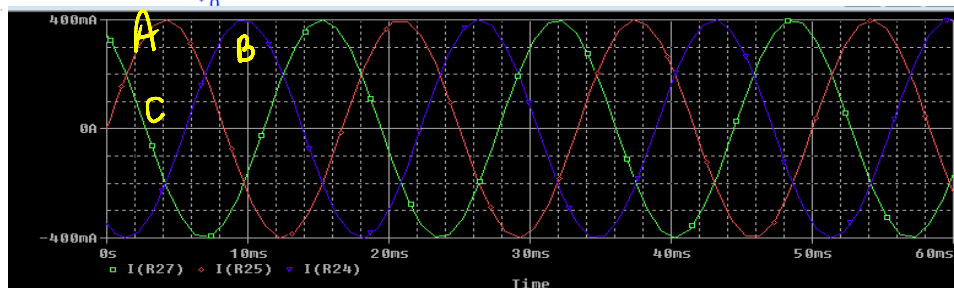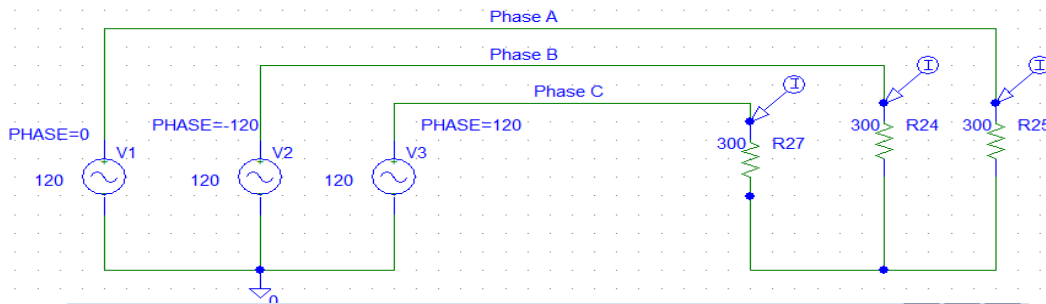


6

Lab 2 – Phase Sequence Determination

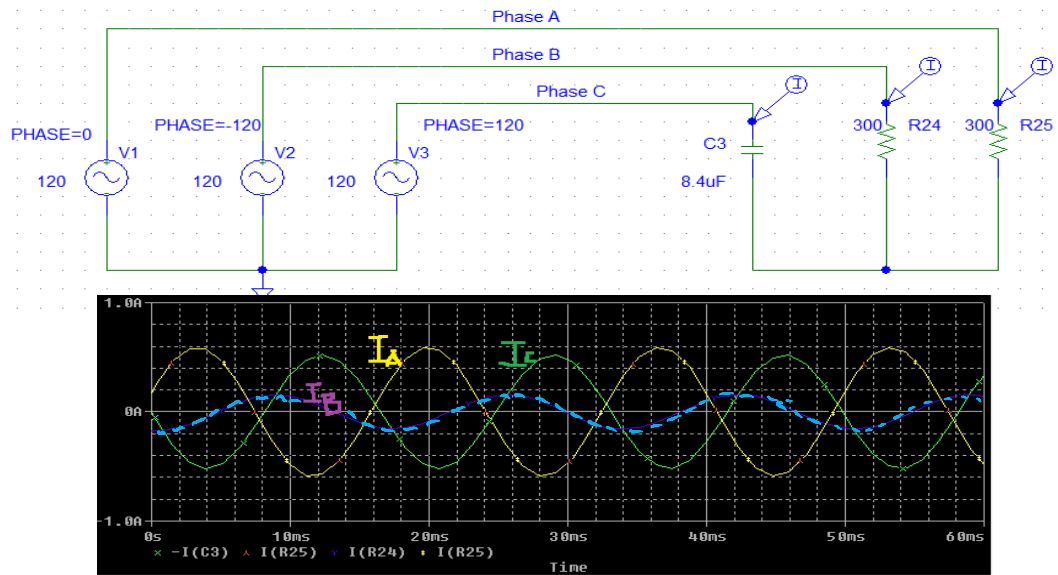

7

Lab 2 – Exp Part

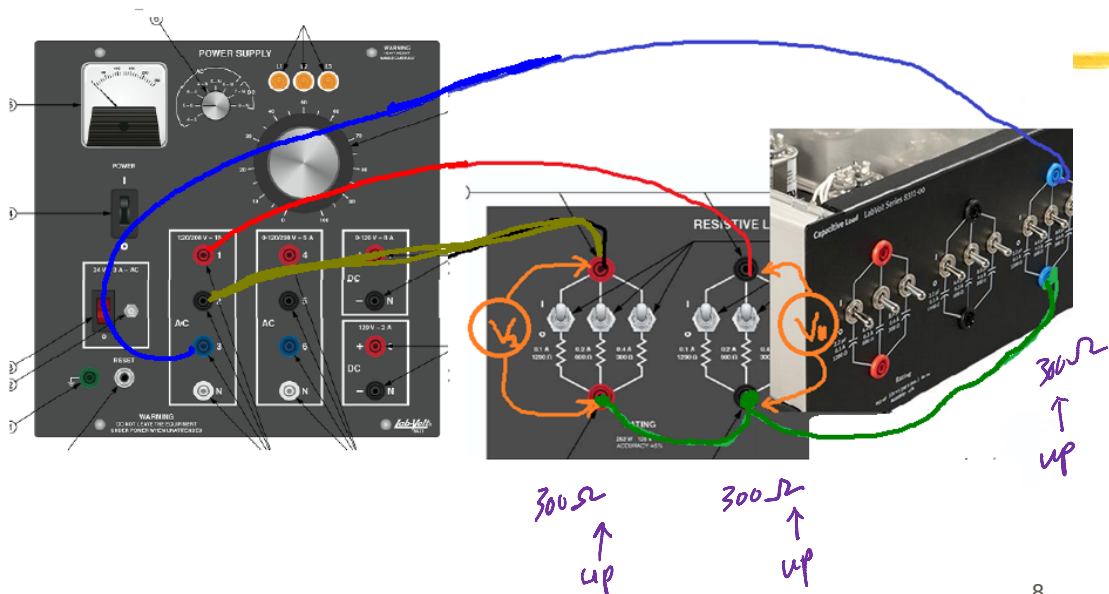

8

Lab 2 – Exp Part 2

⌘ For light bulbs, for the best result and observation, use a capacitor of 2.2 μF (1200 ohm)

