

Pre-Lab 3 Three-Phase System Real and Reactive Power

1. A 3-phase load with identical impedance of $300 + j300$ at each phase is supplied by a balanced 3-phase source whose line-to-line voltage is 120 V. Find (a) 3-phase real power of the load (P_1), (b) 3-phase reactive power of the load (Q_1), and (c) power factor of the load.
2. A 3-phase load with identical impedance made of $R=300$ and $X_L=300$ in parallel at each phase is supplied by a balanced 3-phase source whose line-to-line voltage is 120 V. Find (a) 3-phase real power of the load (P_2), (b) 3-phase reactive power of the load (Q_2), and (c) power factor of the load.
3. A 3-phase load with identical impedance made of $R=300$ and $X_L=200$ and $X_C=250$ in parallel at each phase is supplied by a balanced 3-phase source whose line-to-line voltage is 120 V. Find (a) 3-phase real power of the load (P_3), (b) 3-phase reactive power of the load (Q_3), and (c) power factor of the load.
4. Draw a phase diagram for complex powers of $\mathbf{S}_1=P_1+jQ_1$, $\mathbf{S}_2=P_2+jQ_2$, and $\mathbf{S}_3=P_3+jQ_3$.