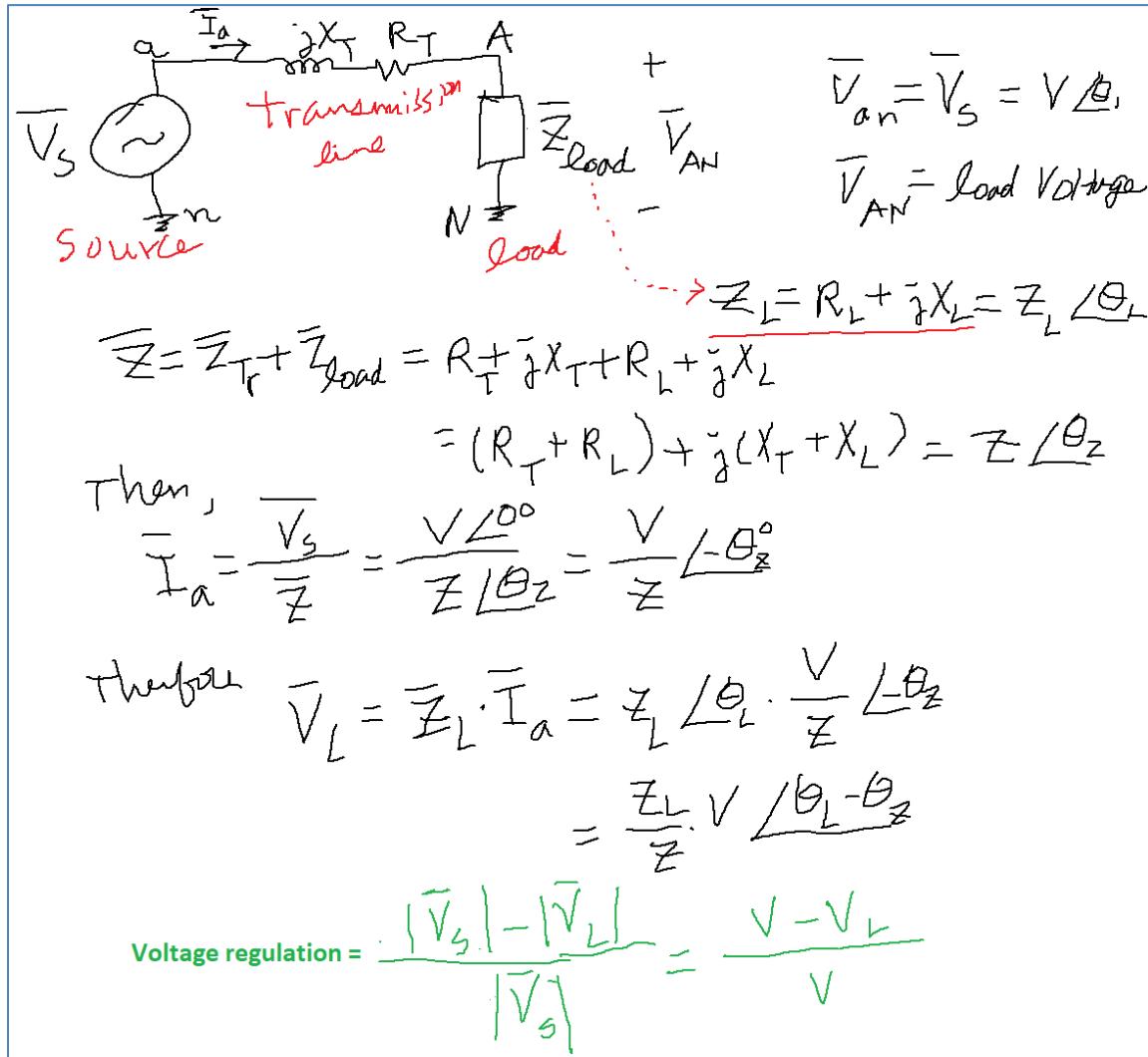


Pre-Lab 4 Power Flow and Voltage Regulation of a Simple Transmission Line

Power from a source to a load can be described by the following diagram and equations thereof:



1. When transmission impedance $\mathbf{Z}_T=R_T+jX_T$ ($R_T=10$, $X_T=100$), $\mathbf{V}_s=10000+j0$, the load $\mathbf{Z}_L=R_L+jX_L$ ($R_L=100$, $X_L=100$), calculate (a) the load voltage \mathbf{V}_{AN} and (b) voltage regulation.

2. When transmission impedance $\mathbf{Z}_T=R_T+jX_T$ ($R_T=0$, $X_T=100$), $\mathbf{V}_s=10000+j0$, the load $\mathbf{Z}_L=R_L+jX_L$ ($R_L=100$, $X_L=100$), calculate (a) the load voltage \mathbf{V}_{AN} and (b) voltage regulation.

3. When transmission impedance $\mathbf{Z}_T=R_T+jX_T$ ($R_T=10$, $X_T=100$), $\mathbf{V}_s=10000+j0$, the load $\mathbf{Z}_L=R_L+jX_L$ ($R_L=100$, $X_L=-50$), calculate (a) the load voltage \mathbf{V}_{AN} and (b) voltage regulation.

4. When transmission impedance $\mathbf{Z}_T=R_T+jX_T$ ($R_T=0$, $X_T=100$), $\mathbf{V}_s=10000+j0$, the load $\mathbf{Z}_L=R_L+jX_L$ ($R_L=100$, $X_L=-50$), calculate (a) the load voltage \mathbf{V}_{AN} and (b) voltage regulation.