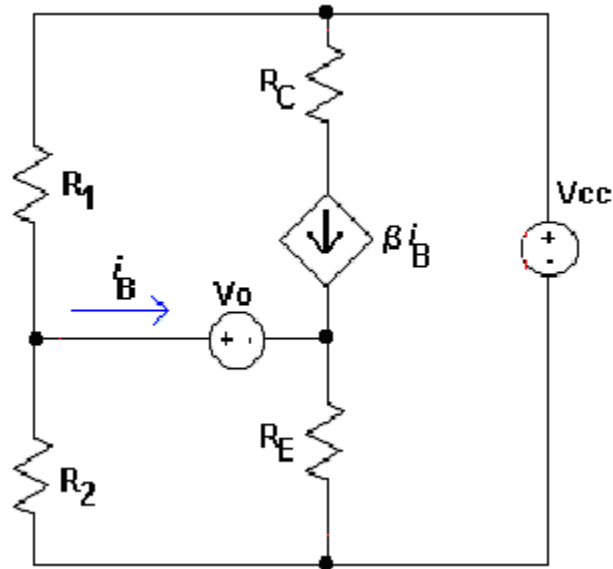


*Solution***Problem 2:**


In a given circuit below, all the resistances and sources are known.

In other words, the known are: V_{cc} , V_o , R_1 , R_2 , R_E , and R_C .

And the question is: **Find equation for i_B in terms of all the known values.**

**Solution:**

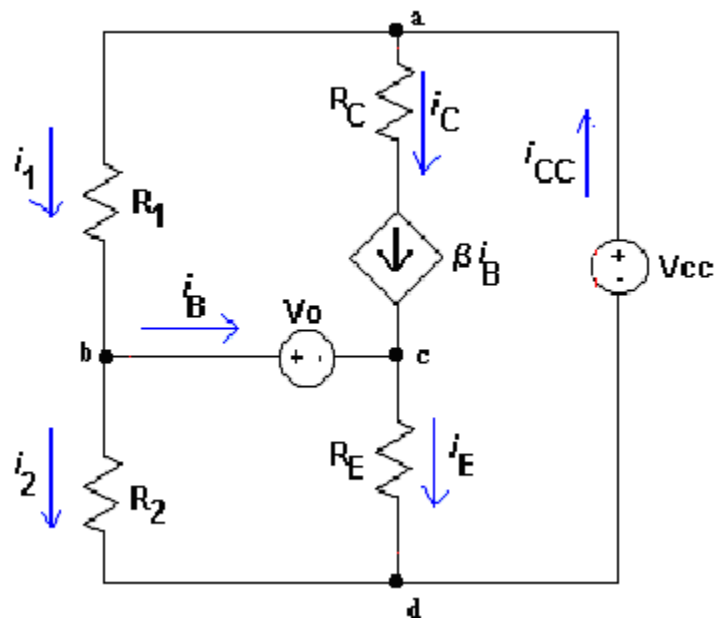1. The first thing we do is to mark nodes (a, b, c, and d) and flow indication of the currents (i_1 , i_2 , i_B , i_E , i_C , and i_{CC})



2. Since the current i_B is our target, it must be centered in any equation derivation.


3. At node c, we have a relationship for the current:

KCL @c: $i_B + i_C = i_E$, since $i_C = \beta i_B$ the final equation is: $i_B(1 + \beta) = i_E$ (1)

4. Now, we have to find equation of i_E

KVL @ Loop2 or KVL @d-b-c-d: $-i_2 R_2 + V_o + i_E R_E = 0$ (2)

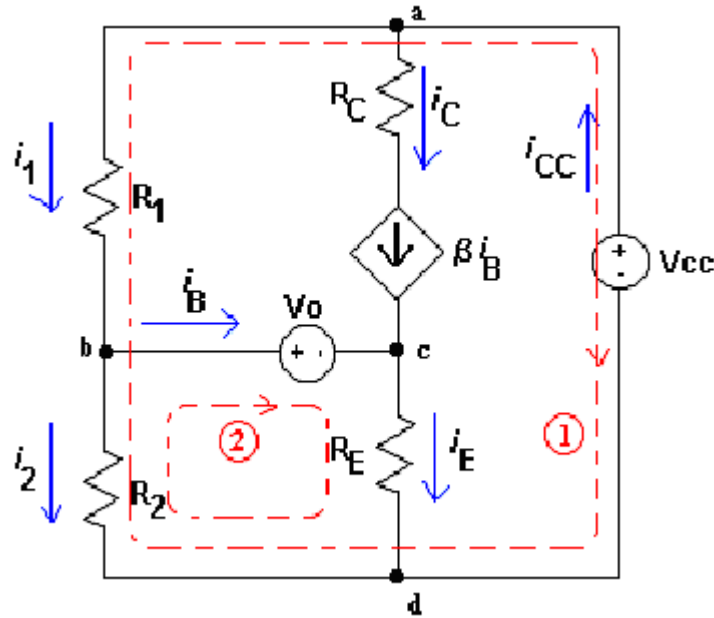5. Since we have one more variable, i_2 , we need another equation which includes i_2



KVL@ Loop1 or KVL @d-b-a-d: $-i_1 R_1 - i_2 R_2 + V_{cc} = 0$ (3)

6. Wait a minute! We now realize that, to solve one equation, we introduce new variables.

So far we have the following 4 unknown variables in 3 equations: i_1 , i_2 , i_B , and i_E

In other words, we need one more equation. Then we may be in a good shape.

7. At node b, we can have an equation which relates currents i_1 and i_2 in terms of i_B

KCL @b: $i_2 = i_1 - i_B$ (4)

8. Now we have 4 unknowns and 4 equations, so the only thing left is how to manipulate to eliminate some.

Let's have a substitution of (4) to (2):

(4) --> (2): $-(i_1 - i_B)R_2 + V_o + i_E R_E = -i_1 R_2 + i_B R_2 + V_o + i_E R_E = 0$ (2)'

Also, let's have another substitution of (4):

(4) --> (3): $-i_1 R_1 - (i_1 - i_B)R_2 + V_{cc} = -i_1 (R_1 + R_2) + i_B R_2 + V_{cc} = 0$ (3)'

9. From (3)', we could get a nice equation of i_1 in terms of i_B and other known values.

$$(3)' \rightarrow: i_1 = \frac{V_{cc} + i_B R_2}{R_1 + R_2} \quad (3)''$$

10. Now, if you plug equation (3)'' to equation (2)', we have an equation with i_E and i_B only.

$$(3)'' \rightarrow (2)': -\frac{V_{cc} R_2 + i_B R_2^2}{R_1 + R_2} + i_B R_2 + V_o + i_E R_E = 0 \quad (2)''$$

11. We now see that with two variables (i_E and i_B), we have two equations (i.e., (1) and (2)''). Let's plug (1) to (2)''

$$(1) \rightarrow (2)'': -\frac{V_{cc} R_2 + i_B R_2^2}{R_1 + R_2} + i_B R_2 + V_o + (1 + \beta) i_B R_E = 0 \quad (2)'''$$

12. I will leave the final simplification of (2)''' to you.

$$i_B [R_2 + (1 + \beta) i_B - \frac{R_2^2}{R_1 + R_2}] + V_o - \frac{V_{cc} R_2}{R_1 + R_2} = 0$$

$$i_B [(1 + \beta) i_B - \frac{R_1 R_2 + R_2^2 - R_2^2}{R_1 + R_2}] + V_o - \frac{V_{cc} R_2}{R_1 + R_2} = 0$$

13. Here is the final solution. Check with yours.

$$i_B = \frac{\frac{V_{cc} R_2}{R_1 + R_2} - V_o}{(1 + \beta) R_E + \frac{R_1 R_2}{R_1 + R_2}}$$

Now we use Smath Studio to find the the value:

The screenshot shows the following steps in Smath Studio:

- Given values: $V_{cc} = 15$, $V_o = 200 \cdot 10^{-3}$, $R_1 = 20 \cdot 10^3$, $R_C = 500$, $\beta = 39$, $R_2 = 80 \cdot 10^3$, $R_E = 100$.
- Calculation of i_B :

$$i_B = \frac{\frac{V_{cc} \cdot R_2}{R_1 + R_2} - V_o}{(1 + \beta) \cdot R_E + \frac{R_1 \cdot R_2}{R_1 + R_2}} = 0.00059$$
 (labeled [A] and "From (3)'")
- Calculation of i_1 :

$$i_1 = \frac{V_{cc} + i_B \cdot R_2}{R_1 + R_2} = 0.000622$$
- Calculation of i_C :

$$i_C = \beta \cdot i_B = 0.02301$$
- Calculation of i_{CC} using KCL at node a:

$$i_{CC} = i_C + i_1 = 0.023632$$