

Dependent Source Problem

EECE499-Spring 2022 HW1

In a given circuit below, all the resistances and sources are known.
In other words, the known are: V_{cc} , V_o , R_1 , R_2 , R_E , and R_C .
And the question is: **Find equation for i_B in terms of all the known values.**

