

499 HW5 SP22 Define Euler identify

$$\text{Euler}(\theta) = \exp(j\theta) = \cos\theta + j\sin\theta = 1 \angle \theta$$


Test

$$\text{Euler}\left(\text{deg} \cdot \frac{\pi}{180} \cdot i\right) := e$$

$$\text{Euler}(0) = 1 \quad \text{Euler}(90) = -3 \cdot 10^{-15} + i$$

$$\text{Euler}(180) = -1 - 6 \cdot 10^{-15} \cdot i$$

1

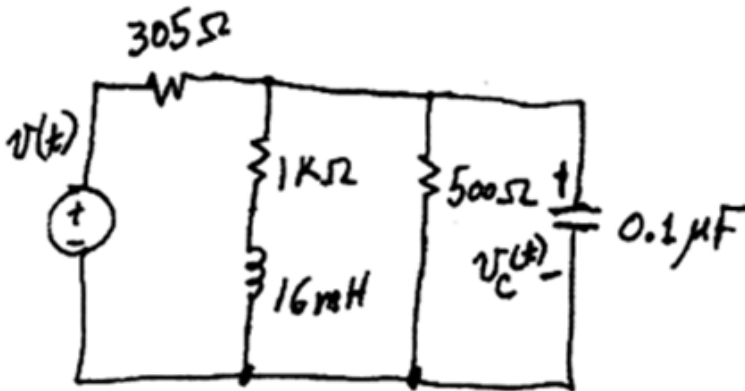1. Find the voltage $v_c(t)$ by steady-state analysis, where $v(t) = \cos(2\pi ft + 45^\circ)$ [V] with $f = 10^4$ [Hz].

$$f := 10^4 \quad \omega := 2 \cdot \pi \cdot f = 62831.8530718$$

$$L := 16 \cdot 10^{-3}$$

$$C := 0.1 \cdot 10^{-6}$$

$$R1 := 305$$

$$R2 := 1000$$

$$R3 := 500$$

Phasor Circuit


$$V := \frac{1}{\sqrt{2}} \cdot \text{Euler}(45) = 0.5 + 0.5 \cdot i$$

$$|V| = 0.7071068$$

$$\arg(V) \cdot \frac{180}{\pi} = 45$$

Equivalent

impedance of the

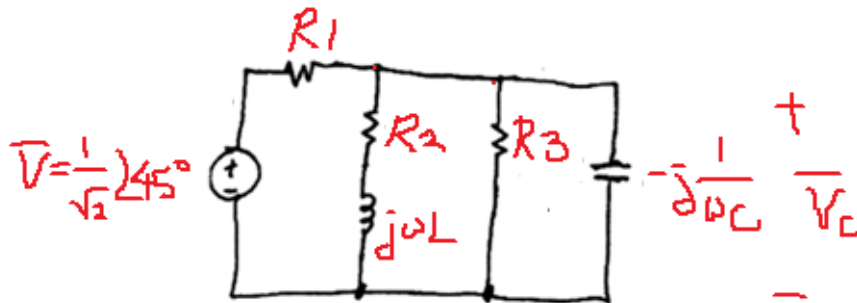3 parallel branches: Z_p 

$$\frac{1}{\omega \cdot C} = 159.154943$$

$$Z_p := \frac{1}{\frac{1}{R2 + \omega \cdot L \cdot i} + \frac{1}{R3} + \frac{1}{-\frac{1}{\omega \cdot C} \cdot i}} = 62.9340027 - 145.7381291 \cdot i$$

$$\omega \cdot L = 1005.309649$$

 V_c can be found by voltage division

$$V_c := V \cdot \frac{Z_p}{Z_p + R1} = 0.2836423 - 0.0001755 \cdot i$$

$$|V_c| = 0.2836423 \quad \arg(V_c) \cdot \frac{180}{\pi} = -0.0354483$$

$$|V_c| \cdot \sqrt{2} = 0.4011308$$

$$v_c(t) = 0.4 \cdot \cos(\omega t - 0.035)$$

2. In a computer center, there are three single-phase computer devices (description listed below) installed in parallel. The magnitude of the voltage of each device is 208 [V].

Disk: 6.157 kVA at $\text{pf} = 0.79$ lag

Drum: 16.93 kW at $\text{pf} = 0.96$ lag

CPU: 22.694 kW while the current through the CPU = 127 [A]

Find the power factor of the combined computer device (i.e., pf of the computer center).

$$V_{\text{mag}} := 208 \quad I_{\text{cpumag}} := 127$$

$$\theta_{\text{disk}} := \arccos(0.79) = 0.6599873$$

$$S_{\text{disk}} := 6157 \cdot \text{Euler}\left(\theta_{\text{disk}} \cdot \frac{180}{\pi}\right) = 4864.03 + 3774.8988277 \cdot i$$

$$\theta_{\text{drum}} := \arccos(0.96) = 0.2837941$$

$$S_{\text{drum}} := 16930 + 16930 \cdot \tan(\theta_{\text{drum}}) \cdot i = 16930 + 4937.9166667 \cdot i$$

$$\text{from } P_{\text{cpu}} = V_{\text{mag}} \cdot I_{\text{cpumag}} \cdot \cos(\theta_{\text{cpu}})$$

$$P_{\text{cpu}} := 22694$$

$$\theta_{\text{cpu}} := \arccos\left(\frac{P_{\text{cpu}}}{V_{\text{mag}} \cdot I_{\text{cpumag}}}\right) = 0.5372867$$

$$\theta_{\text{cpu}} \cdot \frac{180}{\pi} = 30.7842583$$

$$Q_{\text{cpu}} := V_{\text{mag}} \cdot I_{\text{cpumag}} \cdot \sin(\theta_{\text{cpu}}) = 13519.8897925$$

$$S_{\text{cpu}} := P_{\text{cpu}} + Q_{\text{cpu}} \cdot i = 22694 + 13519.8897925 \cdot i$$

Combined complex power of the computer devices:

$$S := S_{\text{disk}} + S_{\text{drum}} + S_{\text{cpu}} = 44488.03 + 22232.7052868 \cdot i$$

$$|S| = 49734.0728038$$


$$\theta_S := \arg(S)$$

$$\theta_S \cdot \frac{180}{\pi} = 26.5533974$$

$$\text{pf}_S := \cos(\theta_S) = 0.8945181$$


lagging
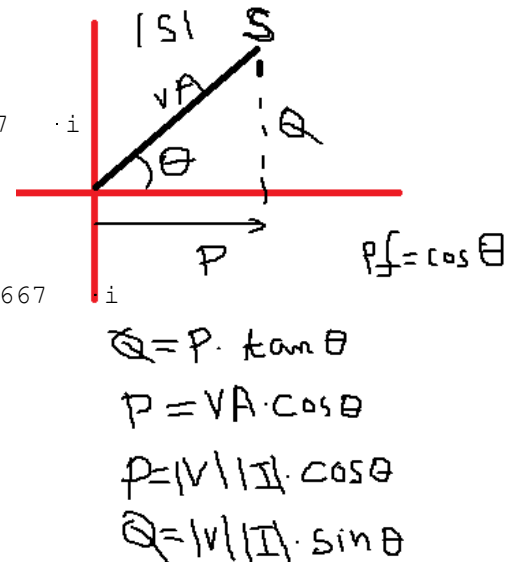
$$\arccos(0.79) \cdot \frac{180}{\pi} = 37.814489$$



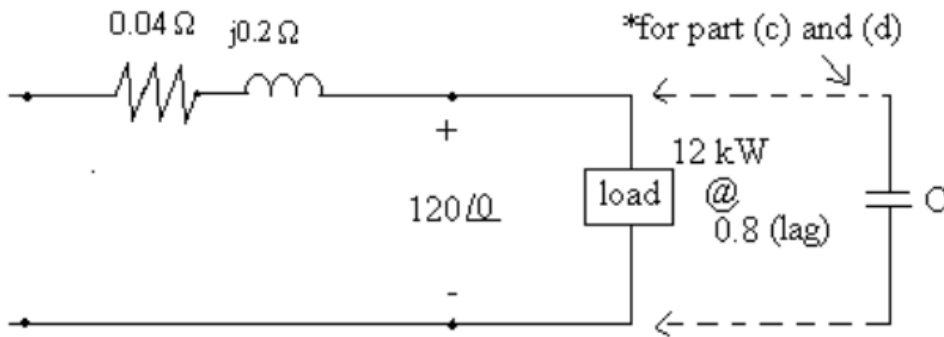3. A load on a 60-Hz system requires 12kW at 0.8 pf lagging when operated at 120V. The impedance of the feeder supplying the load is $0.04 + j0.2 \Omega$. (See circuit below)

- What is the magnitude of the voltage at the source?
- What is the power loss in the feeder line?
- To improve the pf of the load to 0.96 (lagging), what size capacitor (in microfarads) at the load end is needed?
- After the capacitor is installed, what is the magnitude of the voltage at the source, if the load voltage is maintained at 120 V?



```

P1 := 12000      pf1 := 0.8      V := 120 * Euler( 0 ) = 120      f := 60
θ1 := acos( pf1 )      ω := 2 * π * f = 376.9911184
Q1 := P1 * tan( θ1 ) = 9000      Zt := 0.04 + 0.2 * i = 0.04 + 0.2 * i

S1 := P1 + Q1 * i = 12000 + 9000 * i
From S = V I*      I = (S/V)*

I1 := Re( S1 / V ) - Im( S1 / V ) * i = 100 - 75 * i
|I1| = 125      arg( I1 ) * (180 / π) = -36.8698976

Source voltage = I * Zt + V

Vs := I1 * Zt + V = 139 + 17 * i
|Vs| = 140.0357097      arg( Vs ) * (180 / π) = 6.9727693

Power loss in the line Pline = |I|^2 * Rline

Ploss := |I1|^2 * 0.04 = 625 W

```

Now load 2 (with Capacitor only) is added to make the total load has pf of 0.96

Since $P_2=0$, therefore the combine complex power S has the same real power (of load 1).

```

P := P1 = 12000      pf := 0.96      P2 := 0
θ := acos( pf ) = 0.2837941      tan( θ ) = 0.2916667

```

Then $Q := P \cdot \tan(\theta) = 3500$

$$S := P + Q \cdot i = 12000 + 3500 \cdot i$$

Since $Q = Q_1 + Q_2$, $Q_2 = Q - Q_1$ This is required Q from Load 2

$$Q_2 := Q - Q_1 = -5500$$

$$S_2 := P_2 + Q_2 \cdot i = -5500 \cdot i$$

$$\omega = 376.9911184$$

Now current through Load 2 is: From $S = VI^*$ --> $I = (S/V)^*$

$$I_2 := \operatorname{Re}\left(\frac{S_2}{V}\right) - \operatorname{Im}\left(\frac{S_2}{V}\right) \cdot i = 45.8333333 \cdot i$$

Then the impedance of load 2

$$Z_2 := \frac{V}{I_2} = -2.6181818 \cdot i$$

Since $Z_2 = -j(1/\omega C)$

$$C := \frac{1}{\omega \cdot |Z_2|} = 0.0010131 \text{ F}$$

$$C \cdot 10^6 = 1013.1391053 \text{ uF}$$

Now the total current is $I_1 + I_2$

$$I := I_1 + I_2 = 100 - 29.1666667 \cdot i$$

$$V_s := V + I \cdot Z_t = 129.8333333 + 18.8333333 \cdot i$$

$$|V_s| = 131.192183$$

$$\arg(V_s) \cdot \frac{180}{\pi} = 8.2536288$$

$$P_{\text{loss2}} := |I|^2 \cdot 0.04 = 434.0277778 \text{ W}$$

4. A three-phase line has an impedance of $0.8 + j2.4 \Omega$ each phase. The line feeds two balanced three-phase loads that are connected in parallel. The first load is absorbing a total of 144 kW and 108kVar. The second load is Δ -connected and has an impedance of $144 - j42 \Omega$ each phase. The line-to-neutral voltage at the load end of the line is 2400 V. What is the magnitude of the line voltage at the source end of the line?

3 phase load 1

$$S_{31} := 144000 + 108000 \cdot i$$

Load 2

$$Z_{\Delta} := 144 - 42 \cdot i$$

Load Line voltage

$$V_{AN} := 2400$$

per -phase analysis

Line impedance


$$Z_{line} := 0.8 + 2.4 \cdot i$$

single phase power of Load 1

$$S_1 := \frac{S_{31}}{3} = 48000 + 36000 \cdot i$$

 Δ to Y conversion

$$Z_Y := \frac{Z_{\Delta}}{3} = 48 - 14 \cdot i$$

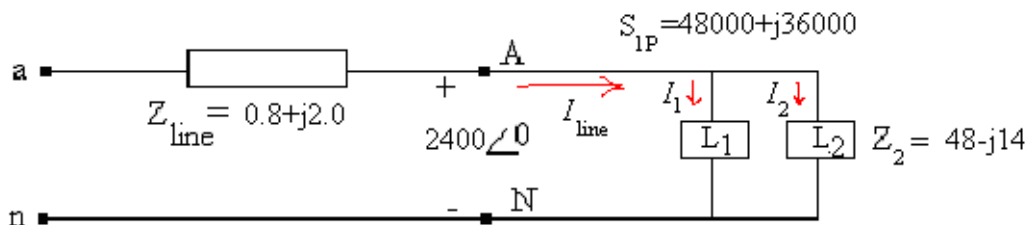From $S = VI^*$ --> $I = (S/V)^*$

$$I_1 := \operatorname{Re}\left(\frac{S_1}{V_{AN}}\right) - \operatorname{Im}\left(\frac{S_1}{V_{AN}}\right) \cdot i = 20 - 15 \cdot i$$

$$I_2 := \frac{V_{AN}}{Z_Y} = 46.08 + 13.44 \cdot i$$

$$I_{line} := I_1 + I_2 = 66.08 - 1.56 \cdot i$$

$$V_{an} := V_{AN} + I_{line} \cdot Z_{line} = 2456.608 + 157.344 \cdot i$$

$$|V_{an}| = 2461.6417286$$

$$\arg(V_{an}) \cdot \frac{180}{\pi} = 3.6647482$$

Since Line voltage is $\sqrt{3}$ bigger and 30 deg angle shift

$$V_{ab} := \sqrt{3} \cdot V_{an} \cdot \operatorname{Euler}(30) = 3548.6480989 + 2363.5009351 \cdot i$$

$$|V_{ab}| = 4263.688544$$

$$\arg(V_{ab}) \cdot \frac{180}{\pi} = 33.6647482$$