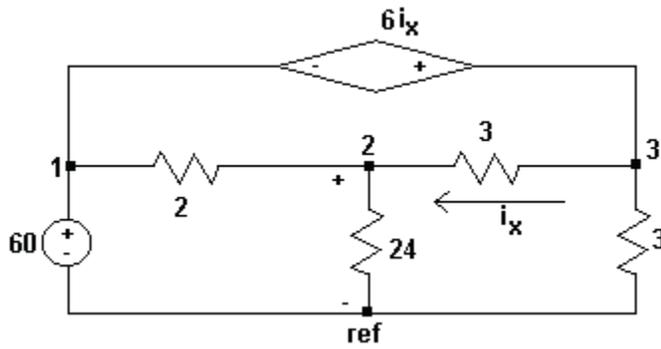


1. Find the voltage at node 2, V_2 .



2. Using the node-voltage method, find the current i_{10} .

