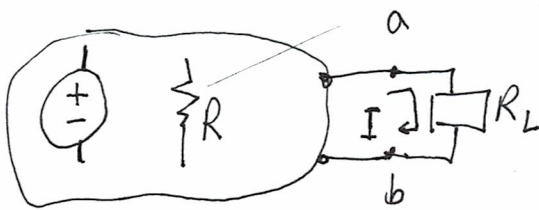



Thevenin Theorem (Principle) ← by Superposition



① Connect a Load

② Then current flows I

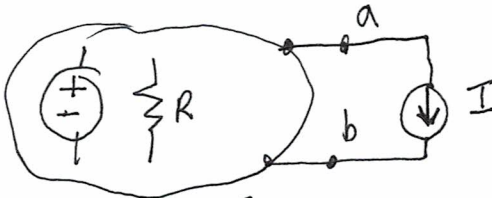③ We replace the Load as a current source with I



④ Apply Superposition,

(i) Voltage source only;

then $\downarrow \Rightarrow 0 \Rightarrow$ open circuit.

$$\rightarrow V_{OC} = V_1$$

(ii) current source only
Voltage source shorted,


So,

$$V_2 = -I \cdot R$$

⑤ Total Voltage

$$V_{ab} = V_1 + V_2$$

$$= V_{OC} - I \cdot R$$

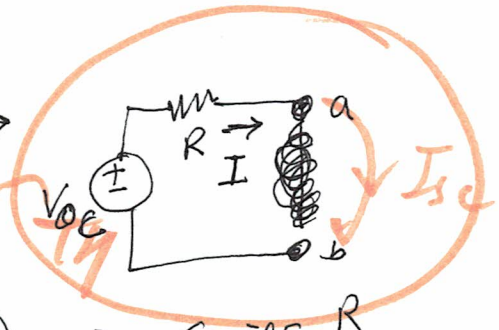

$$V_{OC} = V_{Th} \text{ with series } R$$



R : Equivalent Resistance
after deactivation of
All internal sources

$$V_{Th} = V_{OC}$$

$$R_{Th} = \frac{V_{OC}}{I_{sc}}$$

(2) R_{TH} - conti

(3)

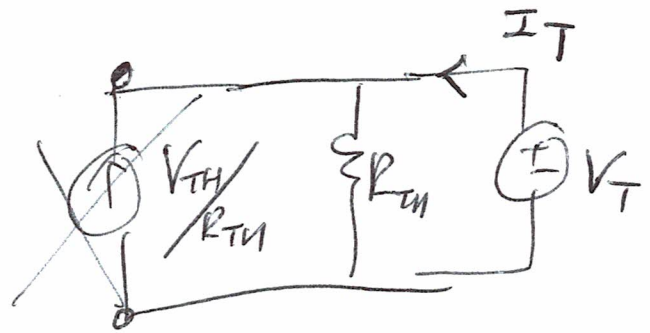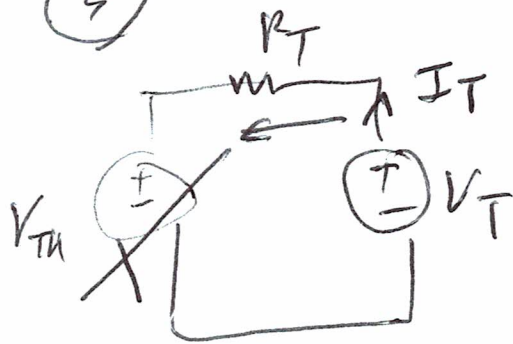

"Test voltage method"


$$R_{TH} = \frac{V_T}{I_T}$$

$$R_{TH} = \frac{V_T}{I_T}$$

"works for all cases source types"




	Applicable Circuits	src deactivated?	$R_{TH}?$
Input Resistance	1) Independent src only	yes	$R_{TH} = R_{ab}$
Short circuit	1) <u>Indep src</u> 2) <u>Indep + dep src</u>	NO	$R_{TH} = \frac{V_{TH}}{I_{SC}}$
Test voltage	1) <u>Indep sr</u> 2) <u>Indep + dep</u> 3) <u>dep src only</u>	yes	$R_{TH} = \frac{V_T}{I_T}$

Thevenin Circuit Exercise problems

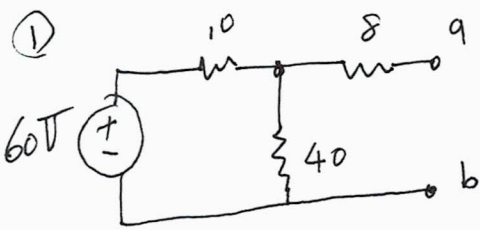

$$V_{oc} = 60 \cdot \frac{40}{10+40} = \frac{60 \cdot 40}{50} = 48V$$
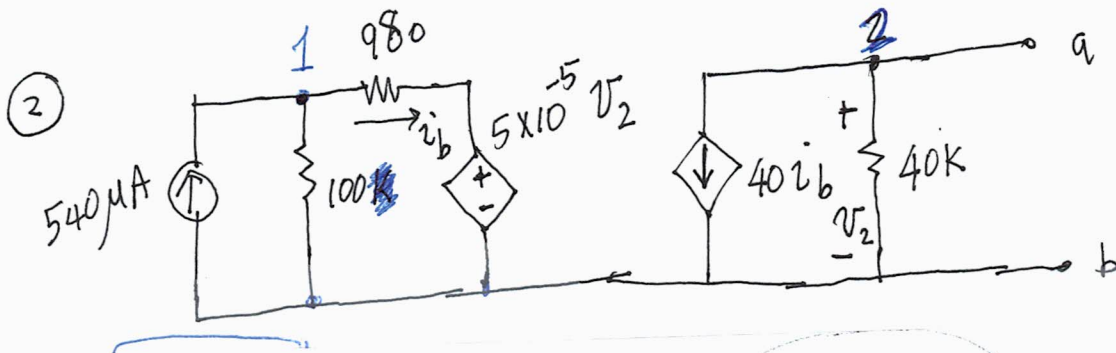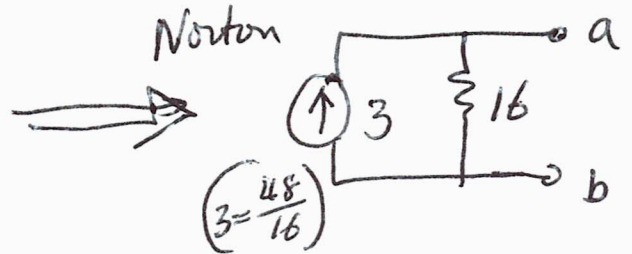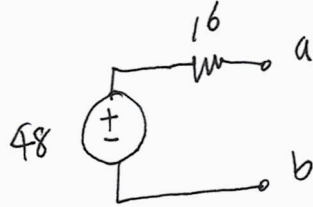
$$R_{th} = 8 + 10 // 40 = 8 + \frac{10 \cdot 40}{50} = 16$$



②; $V_2 = -40 \cdot i_b \cdot 40 \cdot 10^3 = -16 \times 10^5 \cdot i_b$ ①

$V_{oc} = V_2$

①) $-540 \times 10^{-6} + \frac{V_1}{100} + \frac{V_1 - 5 \times 10^{-5} V_2}{980} = 0$ ②

$i_b = \frac{V_1 - 5 \times 10^{-5} V_2}{980}$

$= \frac{V_1 - 5 \times 10^{-5} (-16 \times 10^5) i_b}{980} = \frac{V_1 + 80 \cdot i_b}{980}$

$980 i_b = V_1 + 80 i_b \rightarrow V_1 = 900 i_b$ ③


③ $\rightarrow$ ②: $-540 \times 10^{-6} + \frac{900 i_b}{100} + i_b = 0 \rightarrow -540 \times 10^{-6} + 10 \cdot i_b = 0$

$i_b = 54 \times 10^{-6}$

② $\rightarrow V_{oc} = V_2 = -16 \times 10^5 \cdot i_b = -16 \times 10^5 \cdot (54) \times 10^{-6}$
 $= -86.4 \rightarrow V_{TH}$

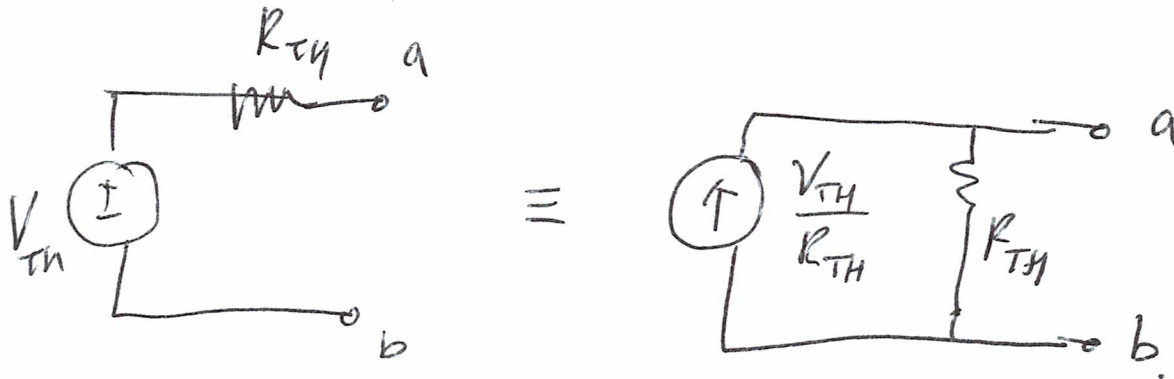(F) 2/18/22

Start from Thevenin circuit / or Norton Cir




$$(1) V_{TH} = \underline{V_{ab}(\text{open})} = \underline{V_{OC}} \quad \Rightarrow \quad V_{TH} = \frac{V_{TH}}{R_{TH}} \cdot R_{TH} = V_{TH} = V_{ab}(\text{open}) = \underline{V_{OC}}$$

(2) R_{TH}

① R_{ab} w/ V_{TH} deactivated $\equiv$ R_{ab} w/ $\frac{V_{TH}}{R_{TH}}$ deactivates
 (Short) (open)
"Input Resistance" $\rightarrow$ Indep source only

②

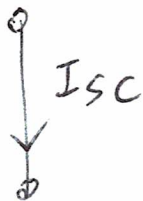


$$R_{TH} = \frac{V_{TH}}{V_{TH}/R_{TH}} = R_{TH}$$

$$R_{TH} = \frac{V_{TH}}{I_{SC}} \text{ with } \underline{ab \text{ shor}}$$

"Short Circuit Method" $\rightarrow$ Indep + dep
Not for Dep only
 "No source"
 deactivation

② Conti-


Short circuit

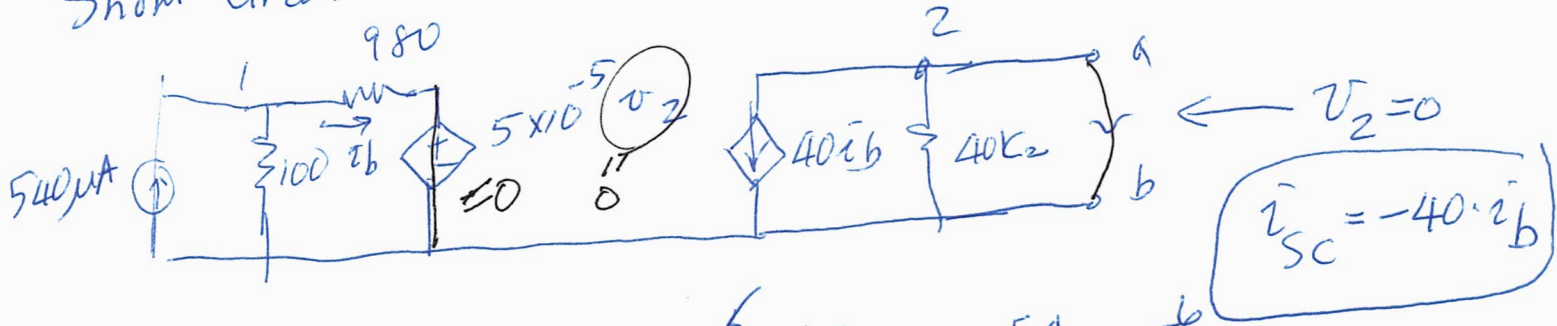

$$i_{b_{sc}} = \frac{540 \times 10^{-6}}{100 + 980} \cdot \frac{100}{100 + 980} = \frac{54}{1.08} \times 10^{-6} = 50 \mu A$$


$$R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{-86.4}{-40 \cdot 50 \mu A} = \frac{-86.4}{(-2000 \cdot 10^{-6})}$$
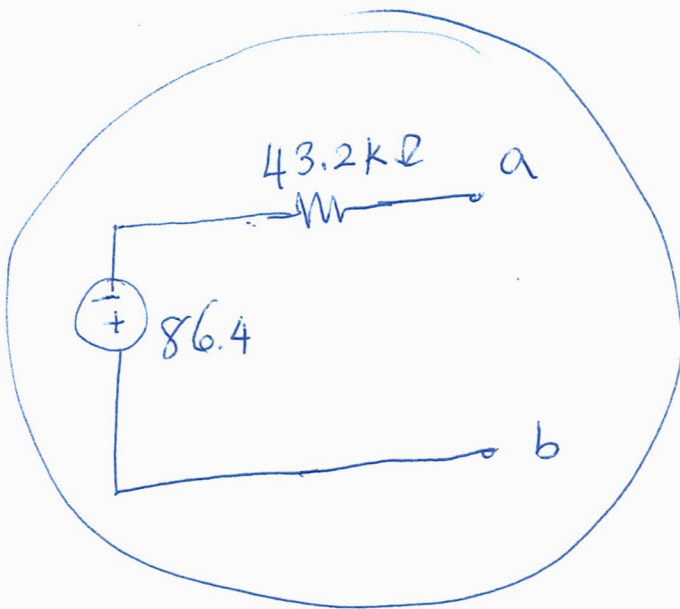
$$= \left(\frac{-86.4}{-2} \right) \cdot 10^3 = (43.2) 10^3 = 43.2 k\Omega$$





Thevenin Theorem Exercise Problem (Continue)

③ Thevenin Circuit at Terminals a & b

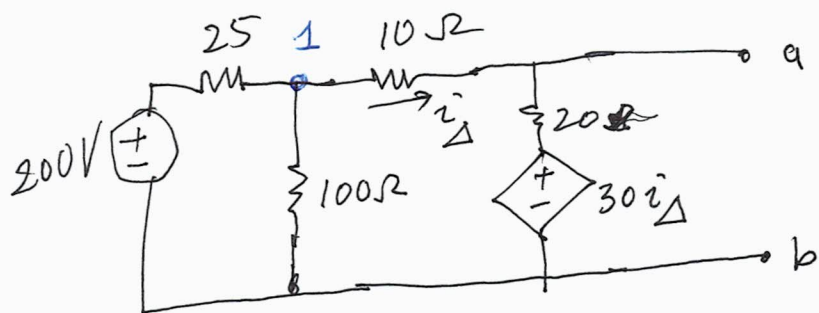

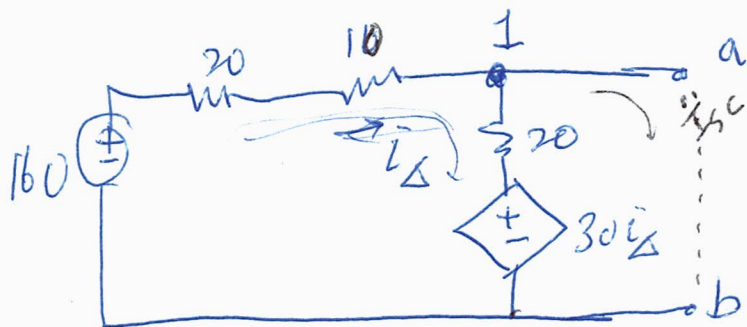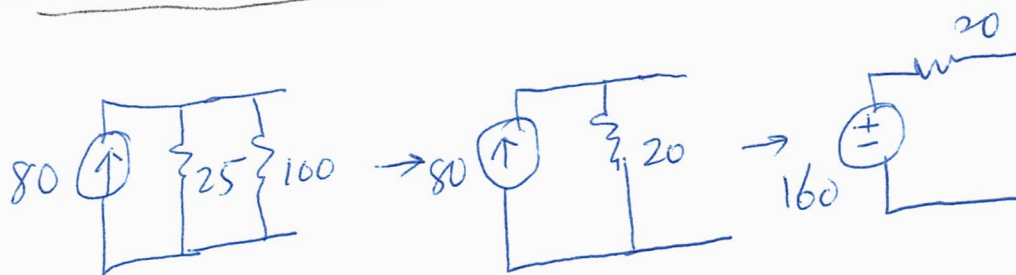Simplify the left side by Source Transformation.



$$V_{oc} = V_1 = (20)i_{\Delta} + 30i_{\Delta}$$

$$V_1 = 50i_{\Delta}$$

@ 1: $\frac{V_1 - 160}{30} + \frac{V_1 - 30i_{\Delta}}{20} = 0$

or $2(50i_{\Delta} - 160) + 3(20i_{\Delta}) = 0 \rightarrow 160i_{\Delta} = 2 \cdot 160$
 $\therefore i_{\Delta} = 2$

$160 = 50i_{\Delta} + 30i_{\Delta}$
 $= 80i_{\Delta}$
 $\therefore i_{\Delta} = 2$


$V_{th} = 100$

$V_1 = 50i_{\Delta} = 50 \cdot 2 = 100 = \underline{V_{oc}} = \underline{V_{th}}$

Now ~~the~~ ~~to~~ practice

Apply Test Voltage Method

Deactivator

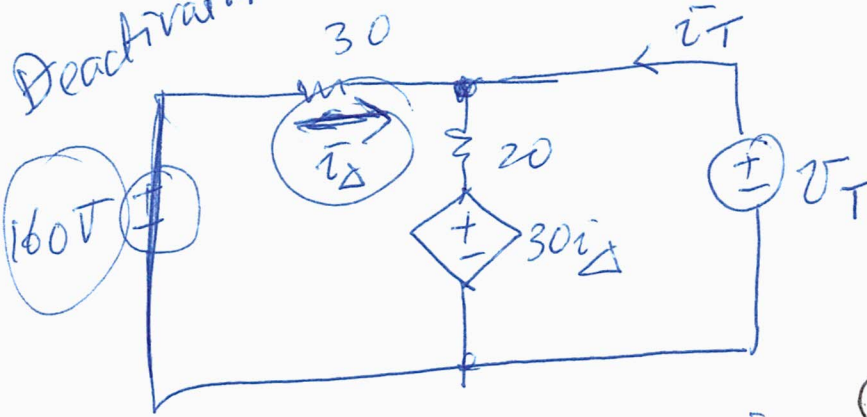


$$\frac{V_T}{30} + \frac{V_T - 30i_{\Delta}}{20} - i_T = 0$$

$$2V_T + 3V_T - 90\left(-\frac{V_T}{30}\right) - 60i_T = 0$$


$$5V_T(2+3+3) = 60i_T$$
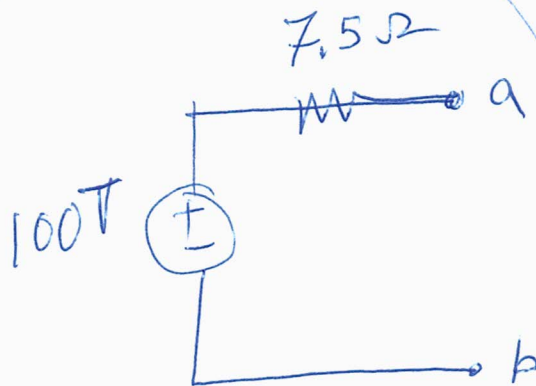
$$\therefore \frac{V_T}{I_T} = \frac{60}{8} = \frac{15}{2} = 7.5 \rightarrow R_{th}$$



$$R = \frac{V_{th}}{I_T}$$

Short circuit case

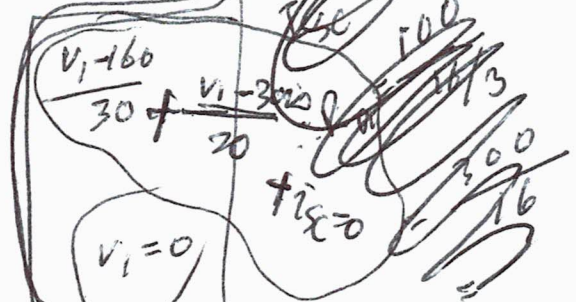

$$\frac{-160}{30} + \frac{-30i_{XC}}{20} + i_{XC} = 0$$

$$i_{XC} = \frac{160}{30}$$

$$\frac{-160}{30} + \frac{-160}{20} + i_{XC} = 0$$

$$-\frac{16}{3} + \frac{16}{2} = i_{XC}$$

$$\frac{-32 + 48}{6} = i_{XC}$$


$$\frac{16}{6} = i_{XC}$$

$$\frac{80}{6} = i_{XC}$$

$$R_{th} = \frac{100}{\frac{80}{6}} = \frac{60}{8} = 7.5$$

Thevenin Theorem Practice Prob (Conti-)

4

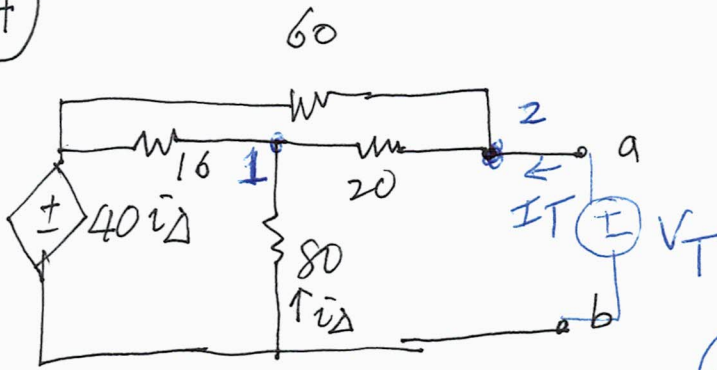

② $V_{th} = 0$, there is no independent source

$$V_2 = V_T$$

$$i_{\Delta} = -\frac{V_1}{80}$$

② $R_{th} = \frac{V_T}{I_T}$

@ 2 : $-I_T + \frac{V_T - V_1}{20} + \frac{V_T - 40i_{\Delta}}{60} = 0$ (1)

@ 1 : $\frac{V_1 - 40i_{\Delta}}{16} + \frac{V_1}{80} + \frac{V_1 - V_T}{20} = 0$ (2)

(1) $\Rightarrow -I_T + \frac{V_T - V_1}{20} + \frac{V_T - 40(-\frac{V_1}{80})}{60} = 0$

$$4V_T - 2.5V_1 = 60I_T \quad (1)'$$

(2) $\Rightarrow 5V_1 - 5 \cdot 40(-\frac{V_1}{80}) + V_1 + 4V_1 - 4V_T = 0$

$$5V_1 + 2.5V_1 + V_1 + 4V_1 - 4V_T = 0$$


$$12.5V_1 = 4V_T \Rightarrow V_1 = \frac{4}{12.5} V_T \quad (2)'$$

(2)' $\Rightarrow$ (1)' $4V_T - 2.5 \cdot \frac{4}{12.5} V_T = 60I_T$ $\frac{20-4}{5} V_T = 60I_T$ $\frac{V_T}{I_T}$

$$4V_T - \frac{4}{5}V_T = 60I_T$$


$$\frac{20-4}{5}V_T = 60I_T \rightarrow \frac{16}{5}V_T = 60I_T$$
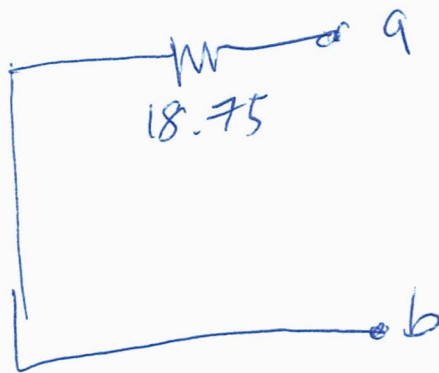
$$\frac{V_T}{I_T} = \frac{60}{16/5} = \frac{60(5)}{16} = 18.75$$



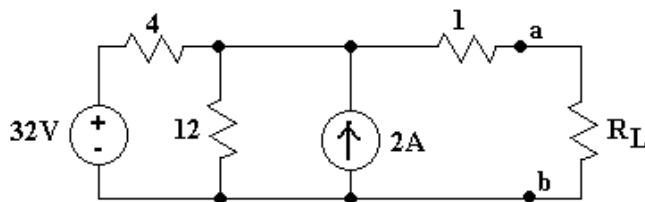
8. An example of **Input Resistance Method**

Find the Thevenin equivalent circuit of the circuit shown below, to the left of the terminals **a** and **b**. Then, find the current through the load resistor $R_L = 6 \Omega$.




Solution:

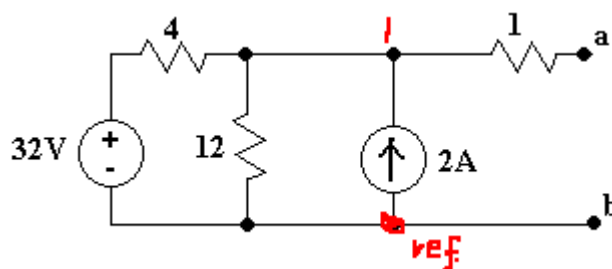(a) Finding V_{th} : Open-circuit voltage. Since two terminals a and b are open, there is no current flowing through 1Ω resistor. If we apply the node-voltage method, the open circuit voltage is the same as the node voltage V_1 .




Therefore, @node 1: $\frac{V_1 - 32}{4} + \frac{V_1}{12} - 2 = 0 \rightarrow V_1 = 30 \text{ V} \rightarrow V_{th} = 30 \text{ V}$

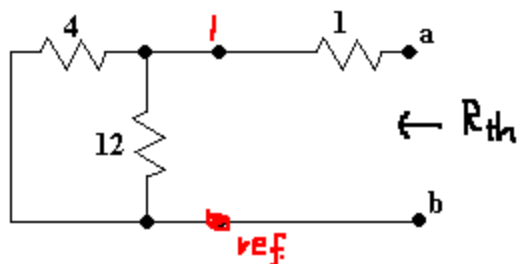(b) Finding R_{th} : After deactivating independent sources, we have,




Therefore, $R_{th} = R_{ab} = 1 + (4//12) = 1 + 3 = 4 \Omega$

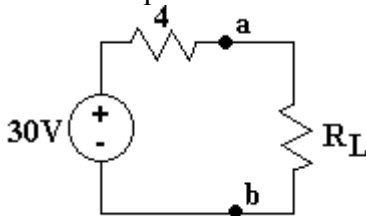(c) Finding the load current: The final equivalent circuit with the load is reduced to:




Therefore, $I_L = \frac{30}{4 + 6} = 3 \text{ [A]}$

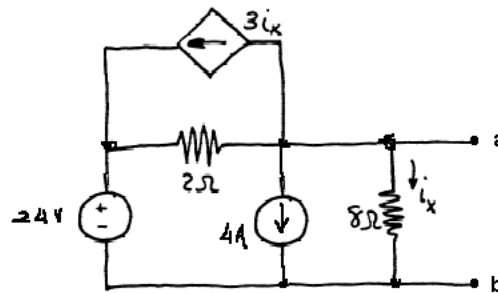9. An example of **Short Current Method** and **Test Voltage Method**
Find the Thevenin equivalent circuit of the following circuit.



Solution:


(a) **Derivation of V_{th} .**

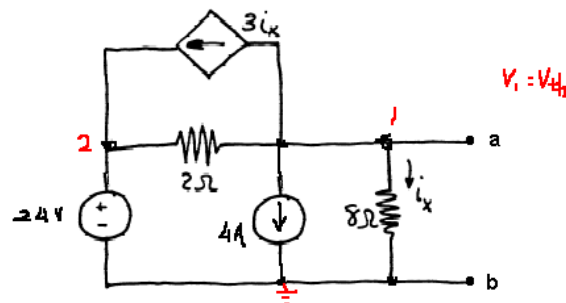


Constraints: $V_2 = 24$; $i_x = \frac{V_1}{8}$

@ node 1: $\frac{V_1 - 24}{2} + 4 + \frac{V_1}{8} + 3 \cdot \frac{V_1}{8} = 0 \rightarrow V_1 = 8 \text{ [V]} = V_{th}$

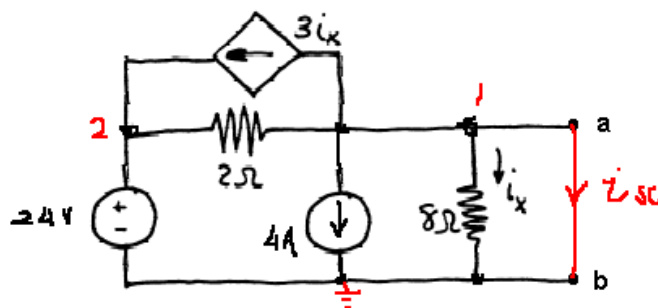(b) **Derivation of R_{th} by Short Current Method:** First, two terminals a and b are shorted to find the short current I_{sc} .



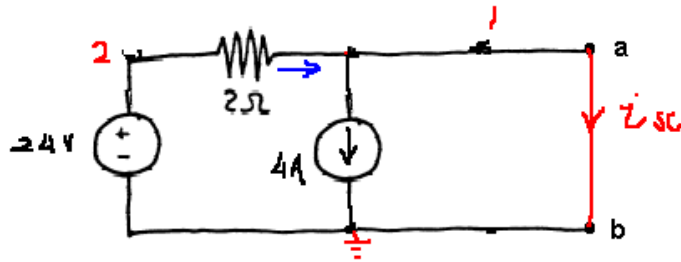When a and b are shorted out, there is no current through 8Ω resistor, therefore, $i_x = 0$. Hence, the dependent source disappears from the circuit. Therefore, the circuit has changed to:




The circuit is very weird, but somehow we may apply node-voltage equation like:


$$\frac{24}{2} = 4 + I_{sc}, \text{ so } I_{sc}=8.$$

Therefore $R_{th}=8/8=1 [\Omega]$

So, the Thevenin equivalent circuit is:

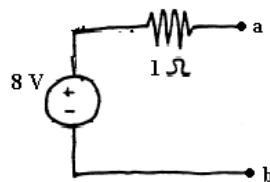

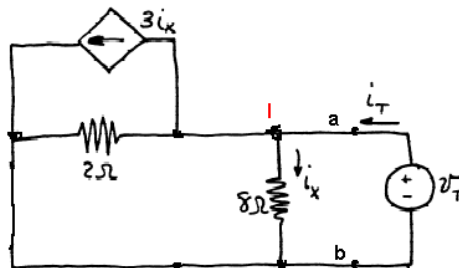(c) **Derivation of R_{th} by Test Voltage Method:** After deactivation of the independent sources, we have the following circuit.




Constraint: $i_x = \frac{V_1}{8}$, $V_1=V_T$.


Applying KCL at node 1: $I_T = i_x + \frac{V_T}{2} + 3i_x = \frac{8V_T}{8} = V_T$

Therefore, $R_{th} = \frac{V_T}{I_T} = 1$

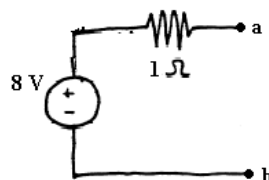
So we have the same Thevenin equivalent circuit, like this.



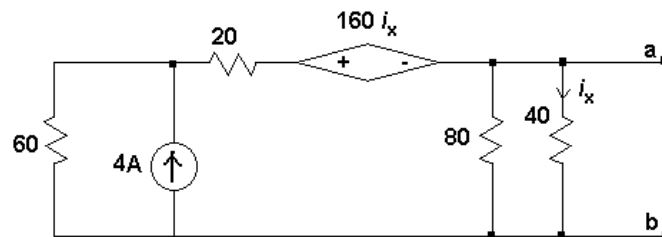10. Another Thevenin equivalent circuit problem.



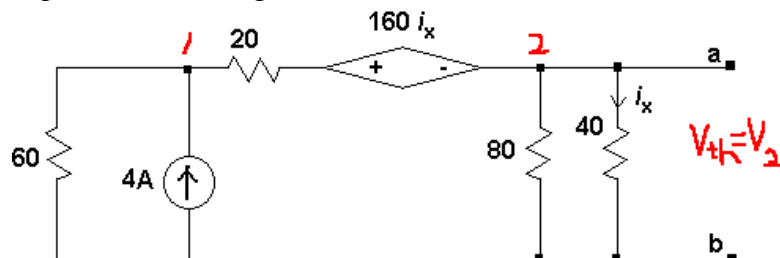(a) V_{th} derivation: Open-circuit voltage




Constraint: $i_x = \frac{V_2}{40}$, therefore $160i_x = 4V_2$

@ node 1: $\frac{V_1}{60} - 4 + \frac{V_1 - V_2 - 4V_2}{20} = 0$ -----(1)

@ node 2: $\frac{V_2}{80} + \frac{V_2}{40} + \frac{V_2 - V_1 + 4V_2}{20} = 0$ -----(2)

From (1) and (2): $V_2 = V_{th} = 30$ [V]

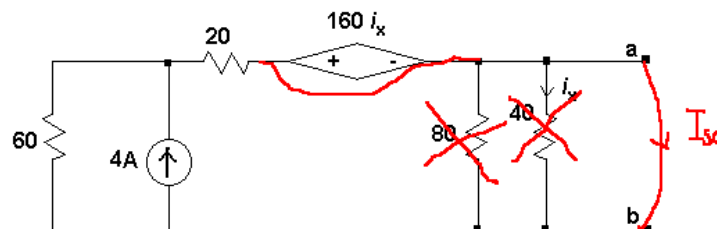
(b) Derivation of R_{th} by Short Current Method: If you short the terminal, then the circuit becomes like below: (Remember $i_x = 0$)



By current-division, we have: $I_{sc} = 4 \cdot \frac{60}{60 + 20} = 3$

Therefore, $R_{th} = 30/3 = 10$ [Ω]

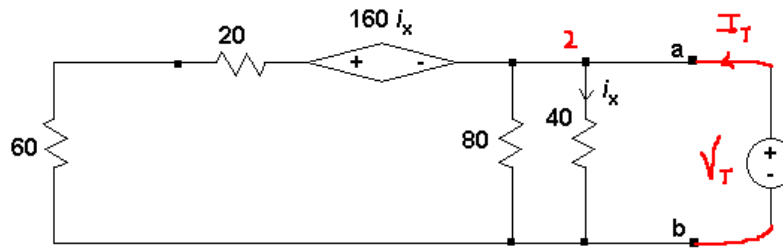(c) Derivation of R_{th} by Test Voltage Method: After deactivation of the independent source and applying a test voltage, we have the following circuit.



Constraint: $i_x = \frac{V_T}{40}$, therefore $160i_x = 4V_T$

Applying KCL @ node 2: $I_T = \frac{V_T}{80} + \frac{V_T}{40} + \frac{V_T + 4V_T}{80}$,

from this $\frac{V_T}{I_T} = 10 = R_{th}$

(d) Final Thevenin equivalent circuit?

