

EECE 417 Computer Systems Architecture

**Department of Electrical and Computer
Engineering
Howard University**

Charles Kim

Spring 2007

Computer Organization and Design (3rd Ed)

-The Hardware/Software Interface

by

David A. Patterson

John L. Hennessy


Chapter 4 - Part B

Transition to Chapter 5

Review on ALU

Lets Build a Processor

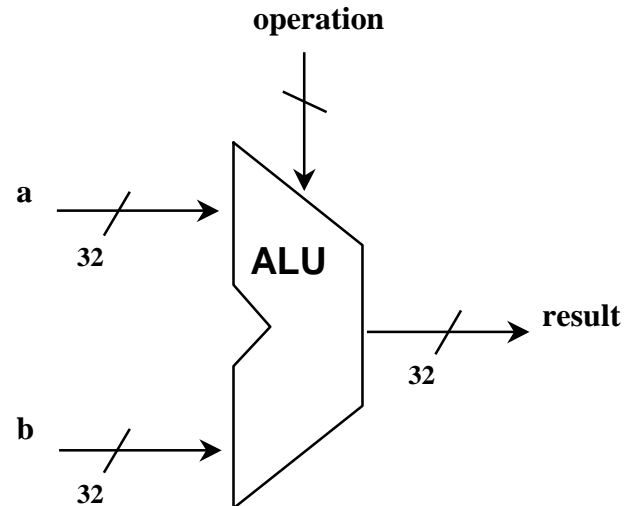- Almost ready to move into chapter 5 and start building a processor
- let's review Boolean Logic and build the ALU we'll need



Review: Boolean Algebra & Gates

- **Problem:** Consider a logic function with three inputs: A, B, and C.

Output D is true if at least one input is true



Output E is true if exactly two inputs are true

Output F is true only if all three inputs are true


- **Show the truth table for these three functions.**
- **Show the Boolean equations for these three functions.**
- **Show an implementation consisting of inverters, AND, and OR gates.**

An ALU (arithmetic logic unit)

  - Let's build an ALU to support the `andi` and `ori` instructions
 - we'll just build a 1 bit ALU, and use 32 of them




 - Possible Implementation (sum-of-products):




Review: The Multiplexor

 - Selects one of the inputs to be the output, based on a control input




- Lets build our 1-bit ALU using a MUX:

 

Different Implementations

 - Not easy to decide the “best” way to build something
 - Don't want too many inputs to a single gate
 - Don't want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit Adder (ALU for addition):




Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$


$$c_{\text{out}} = a b + a c_{\text{in}} + b c_{\text{in}}$$
$$\text{sum} = a \text{ xor } b \text{ xor } c_{\text{in}}$$

- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?

Building a 32 bit ALU

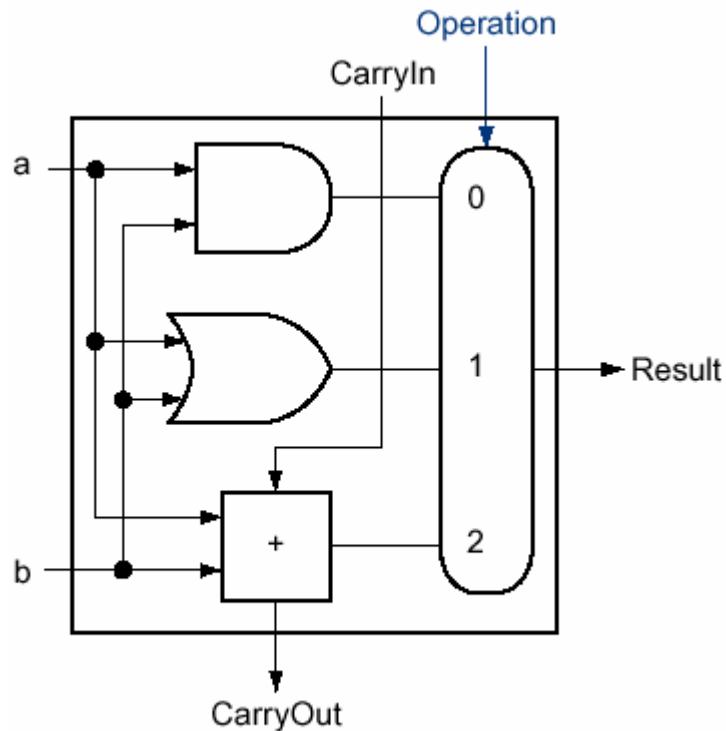

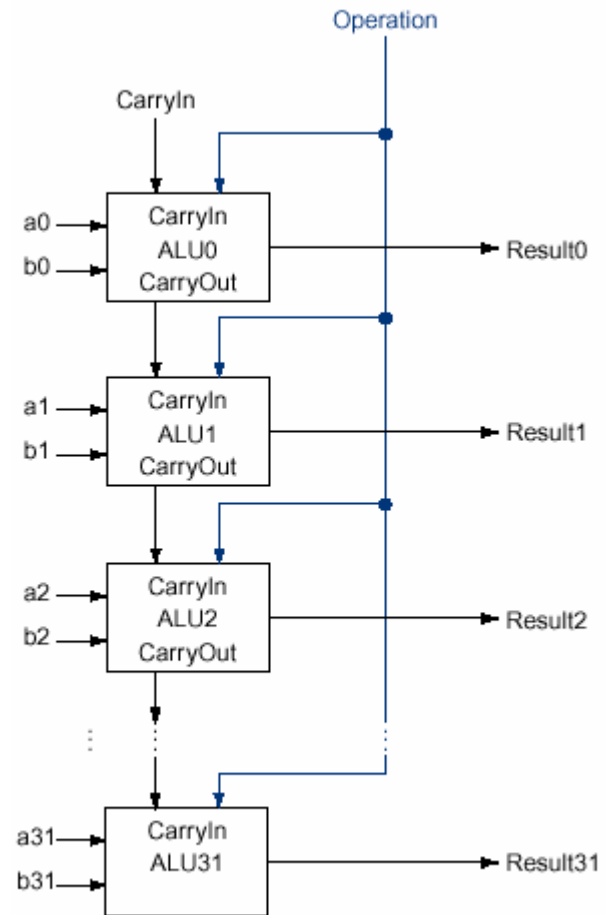A 1-bit ALU that performs AND, OR, and addition




A 32-bit ALU constructed from 32 1-bit ALUs.

What about subtraction ($a - b$) ?

- Two's complement approach: just negate b and add.

- How do we ne


- A very clever solution:

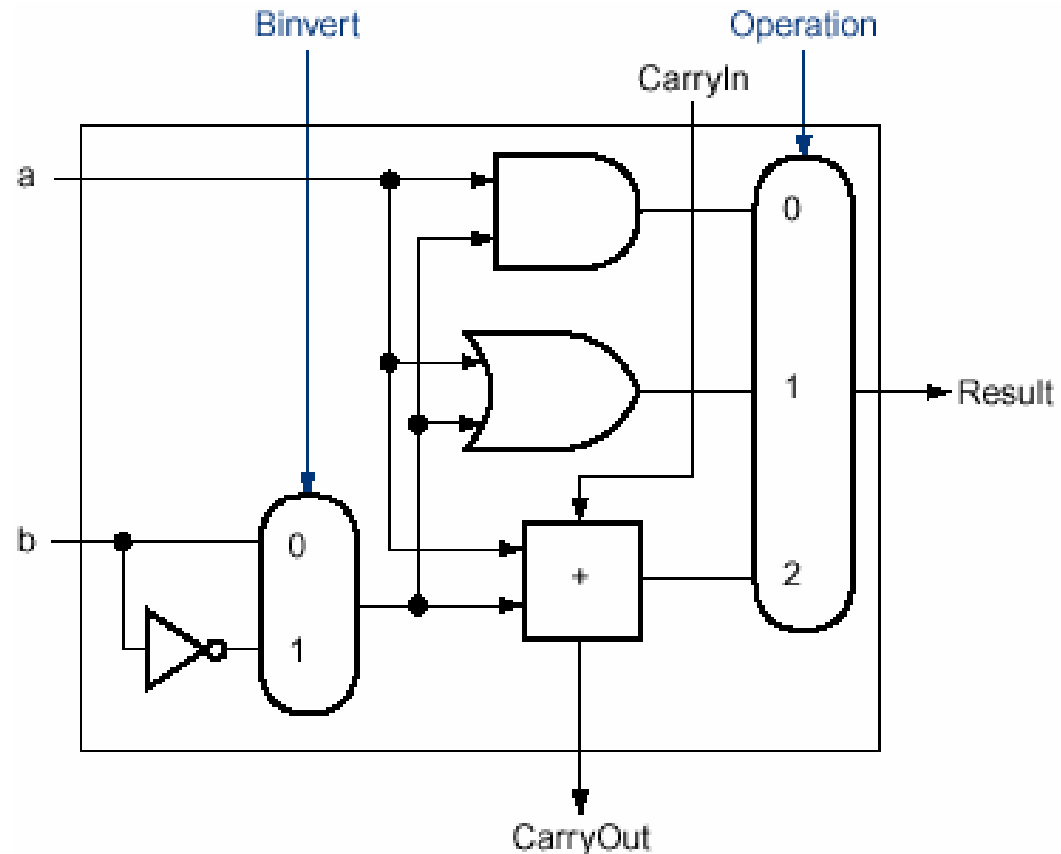

A 1-bit ALU that performs AND, OR, and addition on a and b or a and \bar{b} .


Adding a NOR function

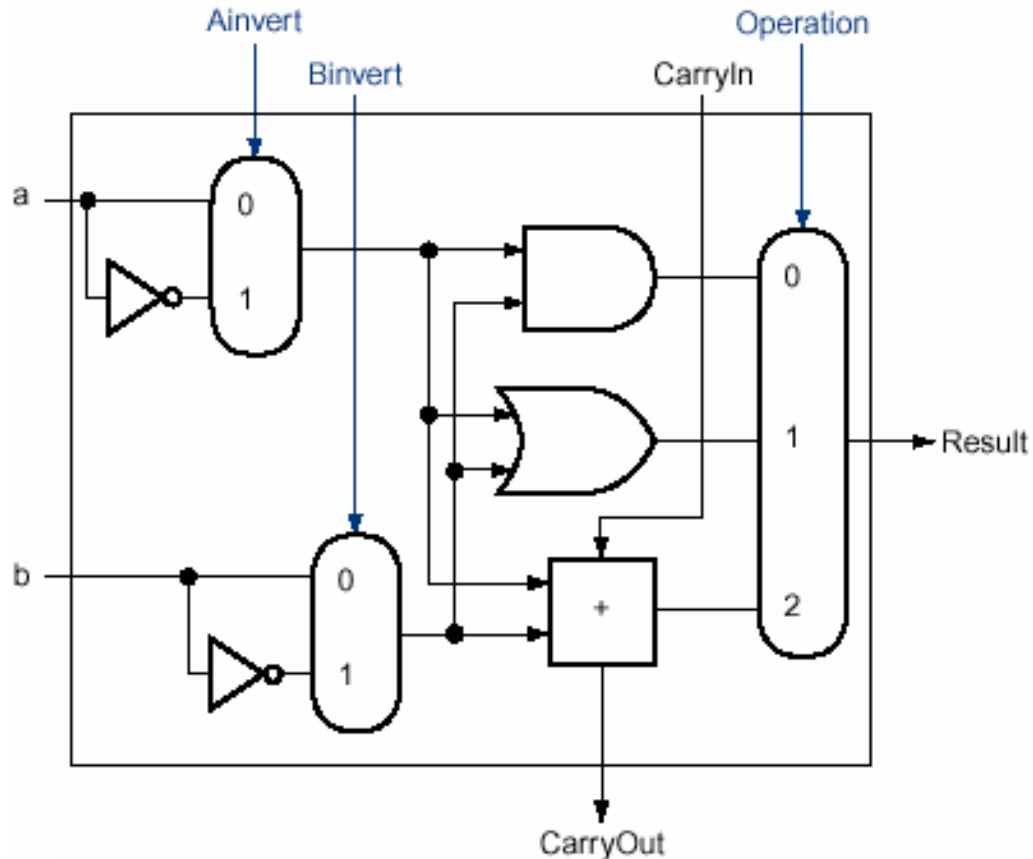- Can also choose to invert a. How do we get “a NOR b” ?




A 1-bit ALU that performs AND, OR, and addition on a and b or \bar{a} and \bar{b} .

Final ALU

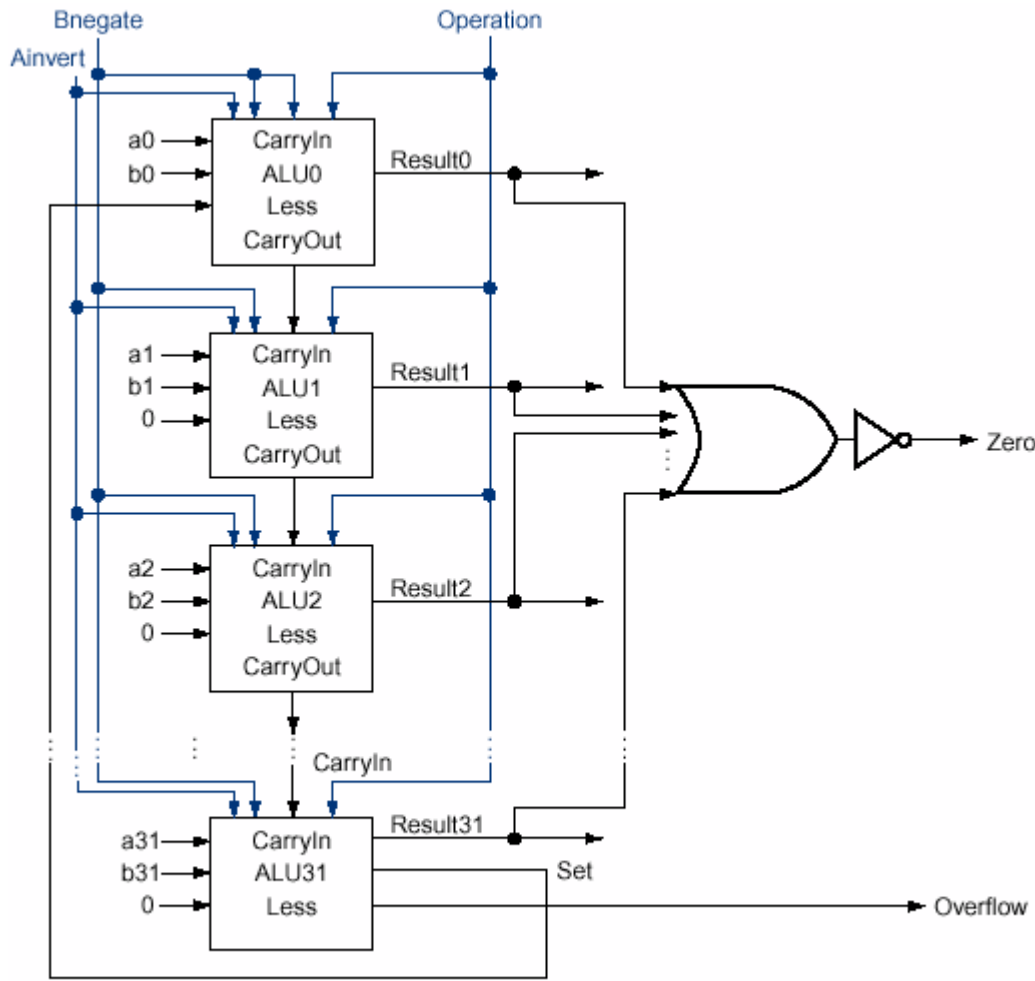

The final 32-bit ALU.

 

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

Conclusion

- **We can build an ALU to support the MIPS instruction set**
 - key idea: use multiplexor to select the output we want
 - we can efficiently perform subtraction using two's complement
 - we can replicate a 1-bit ALU to produce a 32-bit ALU
- **Important points about hardware**
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)