

# EECE 417 Computer Systems Architecture

Department of Electrical and Computer Engineering  
Howard University

Charles Kim

Spring 2007

# **Computer Organization and Design (3<sup>rd</sup> Ed)**

**-The Hardware/Software Interface**

**by**

**David A. Patterson**


**John L. Hennessy**

# **Chapter Five**

## **The Processor: Datapath and Control**

### **Part A**

# Five Classic Components of a Computer

 

# Overview


- Performance Key Factors
  - Instruction count
  - Clock cycle time
  - CPI
- What determines the Instruction Count
  - Compiler
  - instruction set
- What determines the Clock Cycle Time and CPI
  - Implementation of the processor
- Focus of the chapter
  - Implementation principle and technique of MIPS
  - Datapath and control

# The Processor: Datapath & Control

- **Implementation of the MIPS - Simplified version**
  - memory-reference instructions: `lw`, `sw`
  - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
  - control flow instructions: `beq`, `j`
- **Generic Implementation (for all three types):**
  - Send PC to Memory that contains the code
  - Fetch the instruction from that memory
  - Read registers using the fields of the instruction
  - Execute the Instruction depending on the instruction class
- **Common Actions (across different instructions)**
  - Step 1:
    - **Use ALU for operation execution after reading registers**
    - **Use ALU for address calculation (for memory-reference instr)**
  - Step 2
    - **Memory access to load or store**
    - **write back to register**

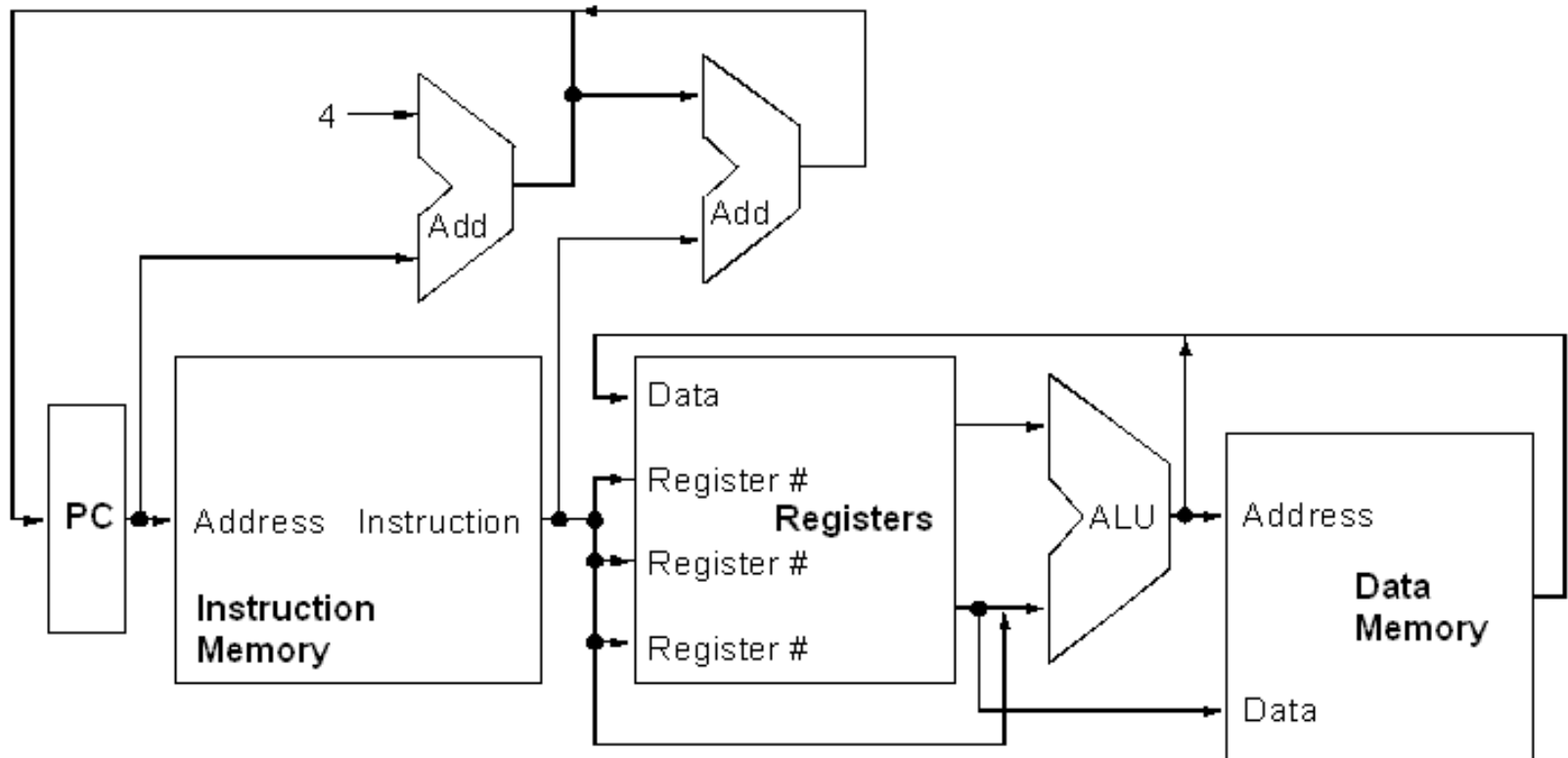
# High Level view of MIPS Implementation

- Abstract / Simplified View:
- Two types of functional units:
  - elements that operate on data values (combinational)
  - elements that contain state (sequential)



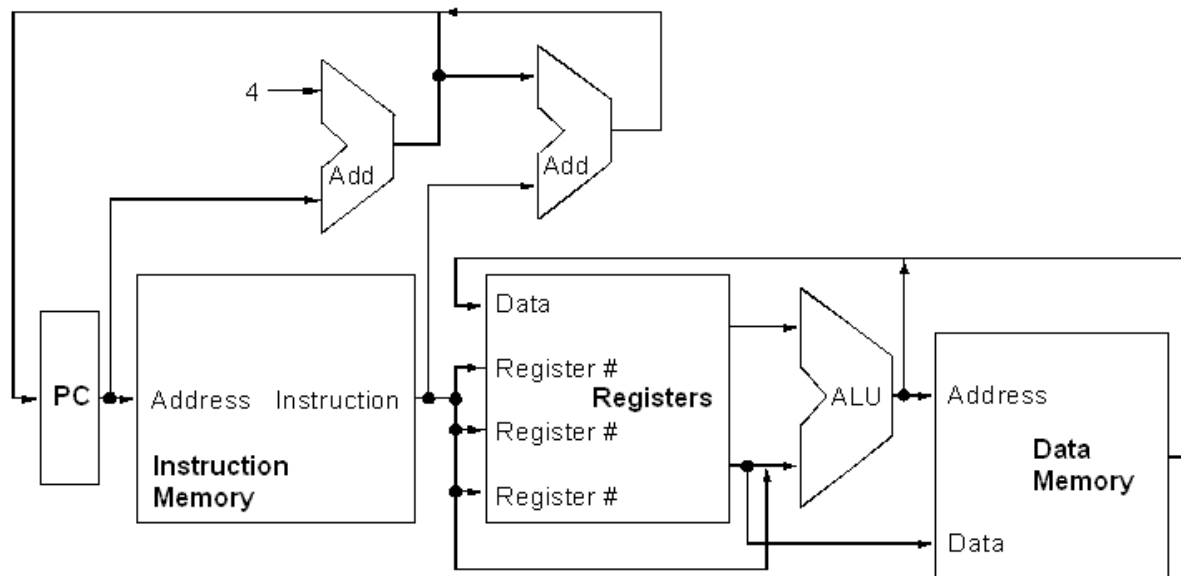
# What's missing here in the High Level view of MIPS Implementation

- No multiplexer (or data selector)
  - Data lines to PC
  - Data lines to Registers
  - Cannot be wired together
- No Control
  - Data memory read (on load) or write (on store)
  - read from and write to register





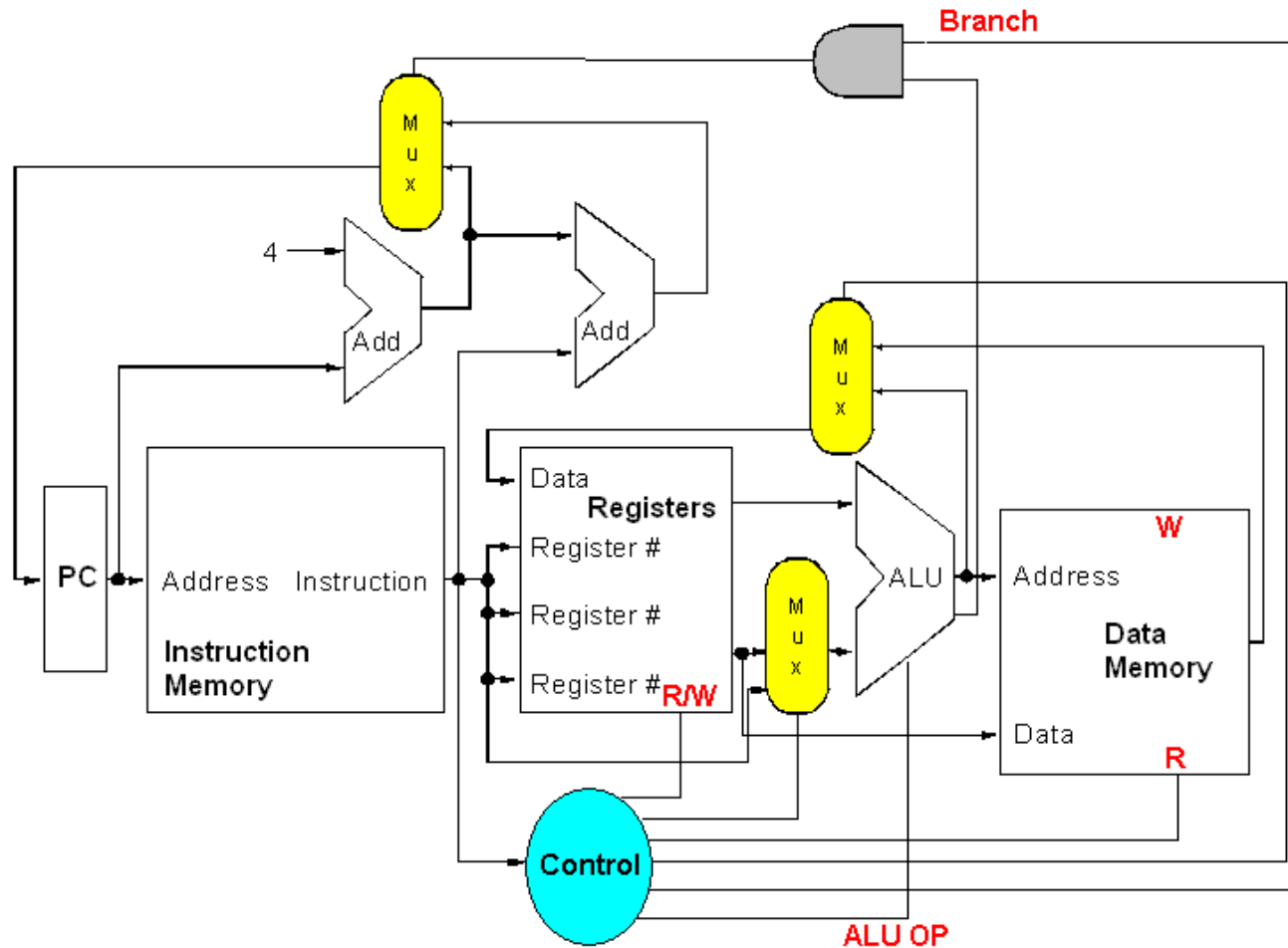
# MIPS Implementation with necessary elements



- **What comes next?**
  - **Element and Components**
  - **Building Datapath with major components**
  - **Control**

 
# Logic Design Convention

- State Elements
  - Internal Storage to indicate a state (sequential)
  - 2 inputs (data and clock) and 1 output
  - Unclocked vs. Clocked
  - Clocks used in synchronous logic
    - **when should an element that contains state be updated?**



 
# Synchronous Digital System

- An edge triggered methodology
- Typical execution:
  - read contents of some state elements,
  - send values through some combinational logic
  - write results to one or more state elements



 
# Datapath Elements - for instruction

- Components required to execute each class of MIPS instruction
- Instruction Memory - instruction store
- PC - hold address of the current instruction
- Adder - Increment the PC to the address of next instruction





 - Fetching Instructions and Incrementing PC by 4



 
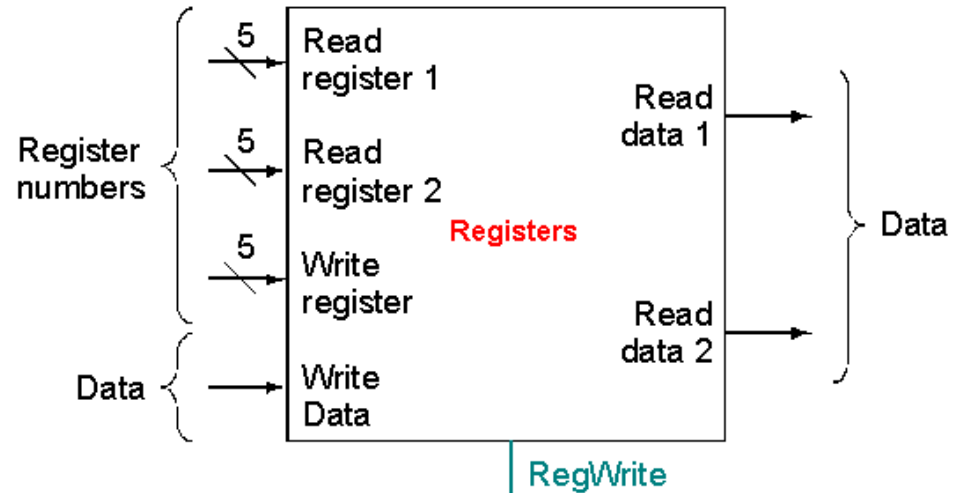
# Elements for R-type Instructions

- R-type instructions
  - add, sub, and, or, etc
  - Read two registers
  - perform ALU operation
  - Write the result
- Needed Elements
  - Register File
    - 32 registers
    - 2 read ports
    - 1 write port
  - ALU
    - Operation on the values of **read** from registers
    - two 32-bit inputs
    - one 32-bit output
    - 1-bit signal if output is zero
    - 4-bit ALU control signal



 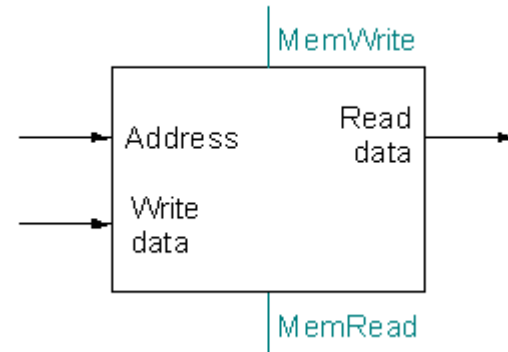
# Elements for Load and Store

- Load and Store
  - `lw $t1, offset($t2)`
  - Memory address = base\_addr [\$t2] + 16-bit signed offset
  - Registers are involved
- Elements Needed
  - Data Memory
  - Register File
  - ALU
  - Sign-Ext unit
    - extension of 16-bit offset filed into 32-bit signed value


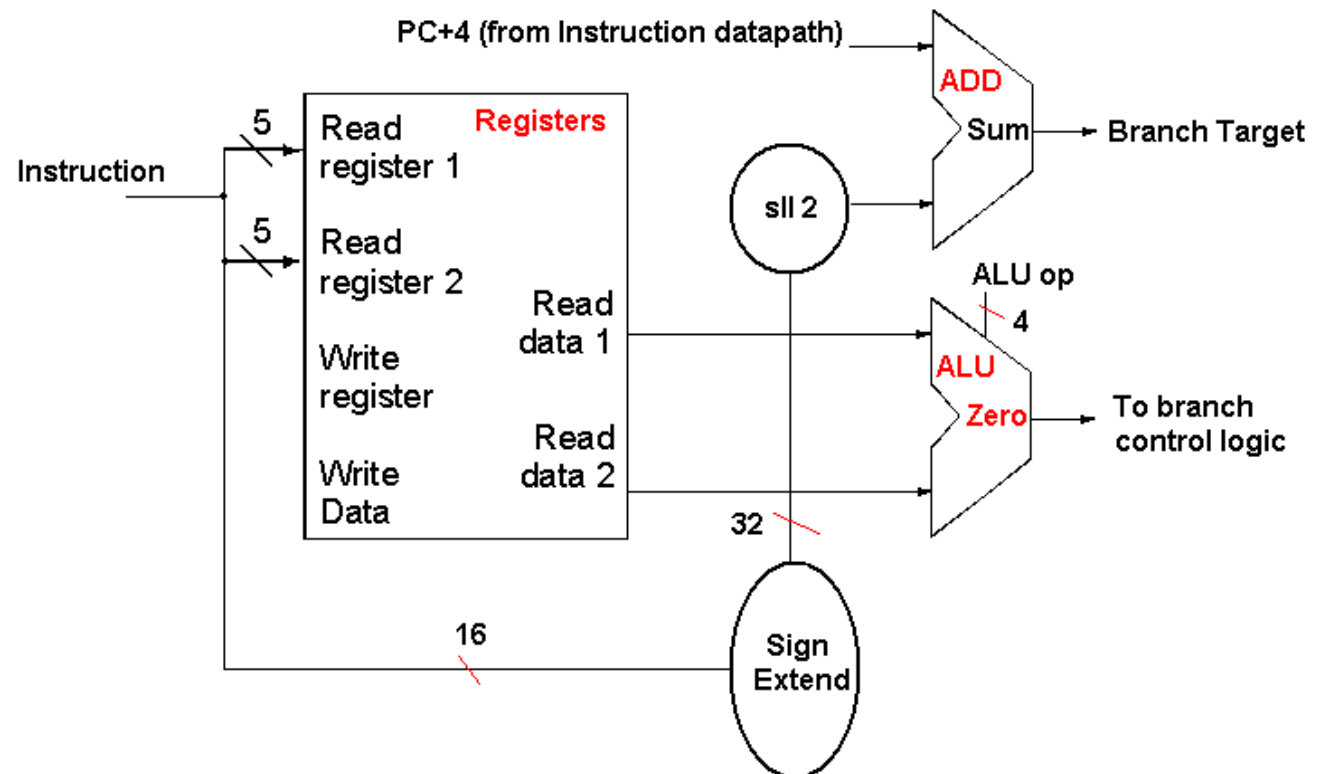
# Datapath for Branch Target Address

- `beq $t1, $t2, offset` : branch to PC+offset if [`$t1`]=`[$t2]`
  - 3 operands
  - 2 registers
  - 16-bit offset
  - Byte offset into Word offset (x4)



# Building a Datapath


- Combination of datapath components into a single datapath
- Add control
- Attempt to execute all instructions in one clock cycle
  - no datapath resource can be used more than once per instruction
  - any element needed more than once must be duplicated
  - Separation of instruction memory from data memory
- Share of datapath elements for different instruction flows
  - multiplexor
  - control signal




# Building a Datapath - Example

- Q: Build a datapath for the operational portion of the memory reference and arithmetic-logical instructions that uses a single register file and a single ALU to handle both types of instructions, adding any necessary mux.
- Analysis:
  - ALU
    - R-type -- for two registers
    - Mem - add calculation (second input is sign-ext)
  - Destination Reg
    - T-type -- from ALU
    - Mem -- from Mem
- Approach
  - 2 different sources for (2nd) ALU input ---->MUX
  - 2 different sources for data stored into register file --->MUX
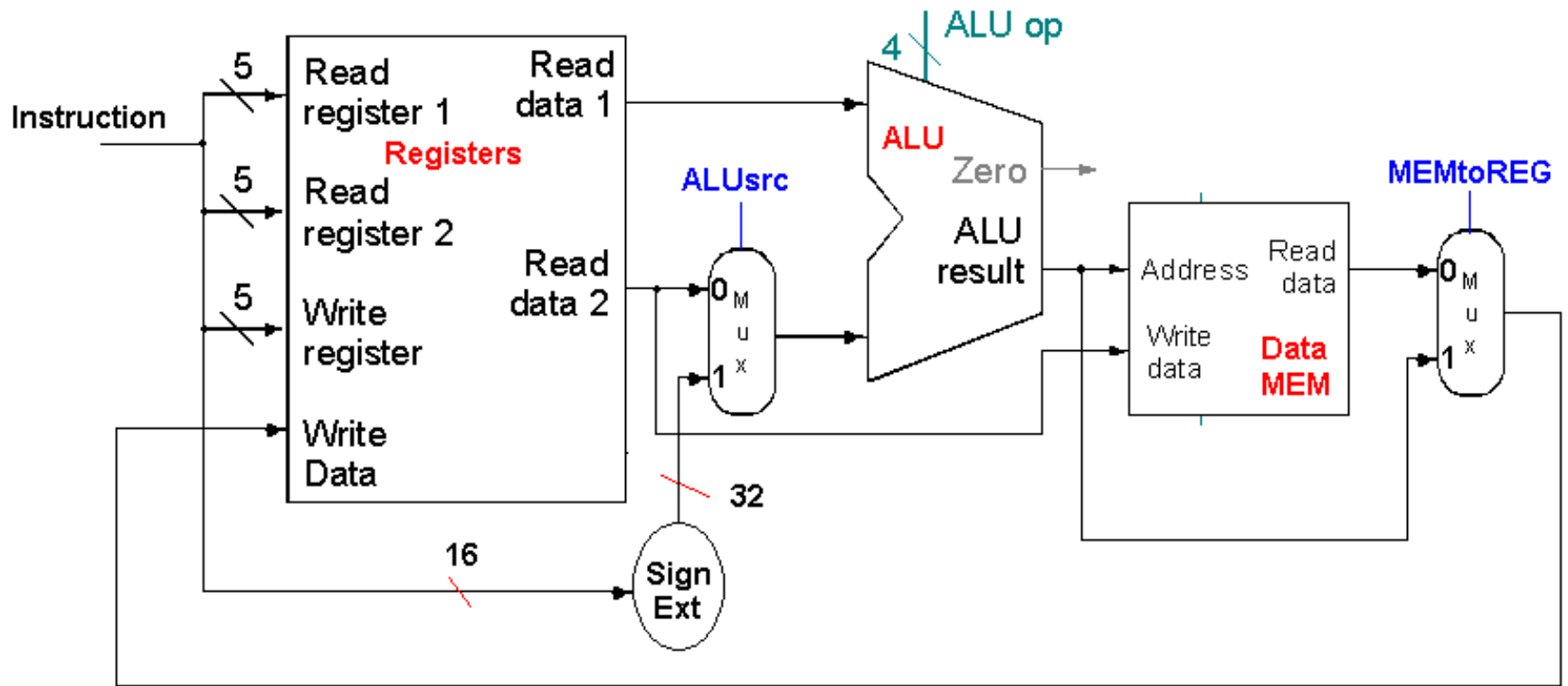
# Datapath for MEM instr and R-type instr


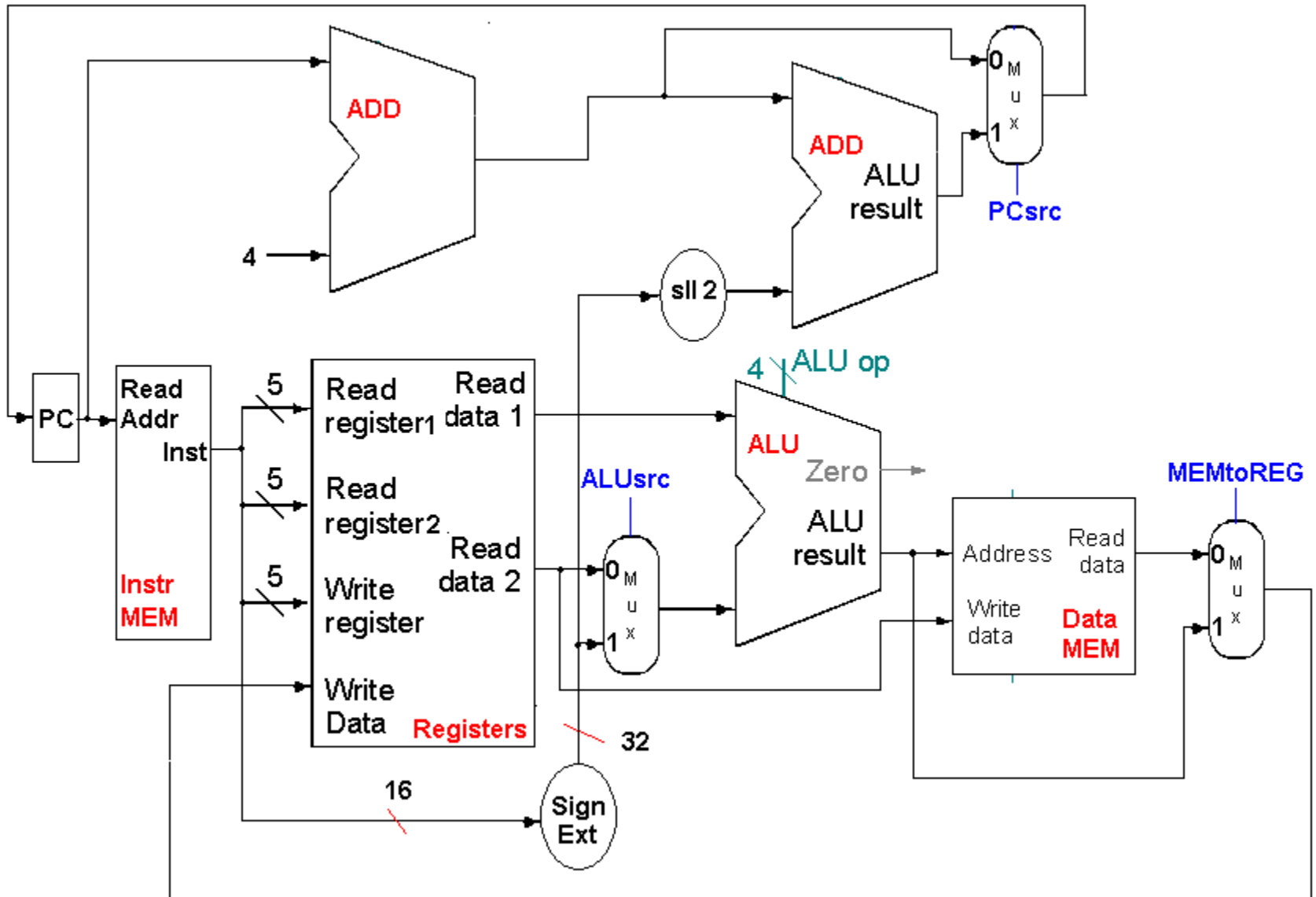
# Datapath for MEM, R-type, and Branch Instr



# A Simple Implementation Scheme

- Simplest possible implementation of MIPS subset using the datapath we discussed before plus simple control function
- Covers **load (lw)**, **store (sw)**, **branch equal (beq)**, **add (add)**, **sub (sub)**, **and (and)**, **or (or)**, **set on less than (slt)** only --"subset"
- **ALU Control (with 4 control inputs)**


0000    **and**  
0001    **or**  
0010    **add**  
0110    **sub**  
0111    **slt**  
1100    **nor**

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR


- Generation of 4-bit ALU control is not simple--what's involving?
  - 2-bit ALUop ("control" bit) --- Instruction classes
  - 6-bit function field (in machine code)
  - 4-bit info from 8 bits?

# ALUop and Function Fields


Instruction Opcode	ALUop	Instruction Operation	Function Field	Desired ALU action	ALU control Input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch Equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

 



R

 

I

 


Branch

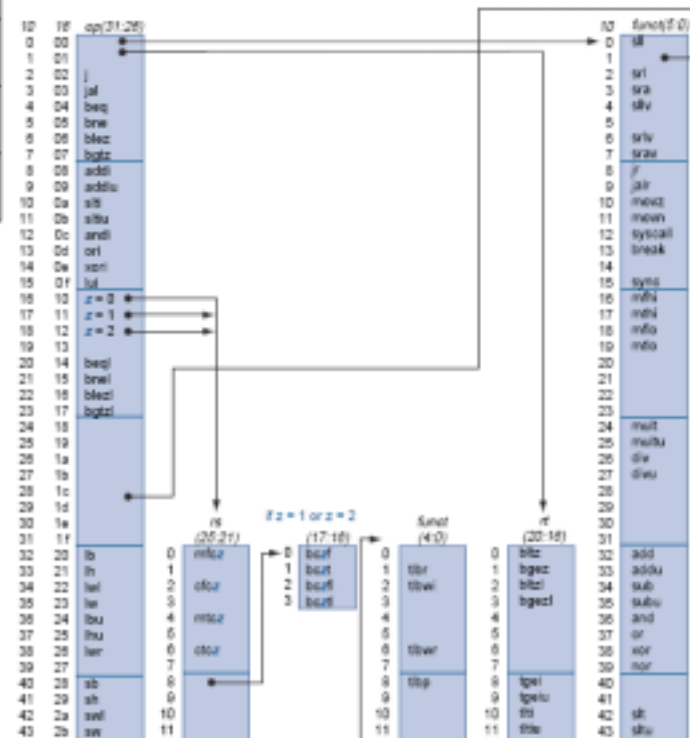 

# Truth Table for ALU control bits


Instruction Opcode	ALUop	Instruction Operation	Function Field	Desired ALU action	ALU control Input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch Equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	and	0000
R-type	10	OR	100101	or	0001
R-type	10	set on less than	101010	set on less than	0111

 


ALUop		Func field						Operation
ALUop1	ALUop0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111

# Main Control Unit

- Schematic for ALU operation

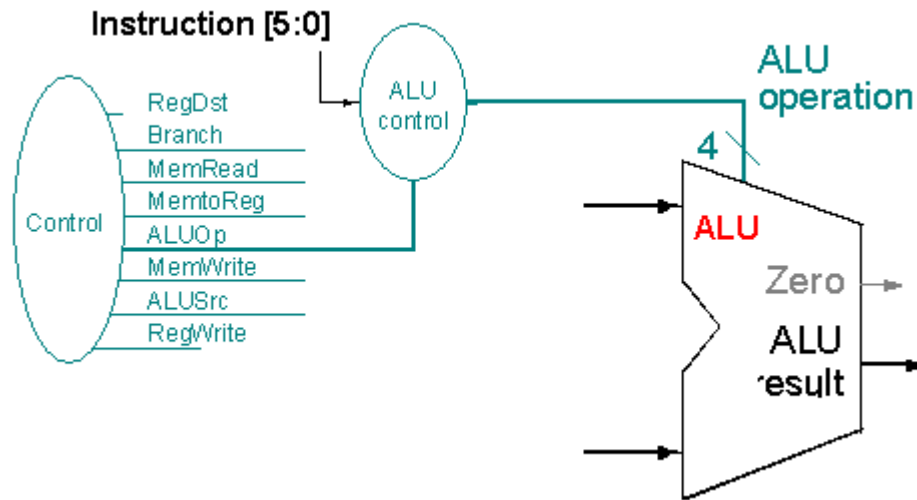

 - Design of Main Control Unit
  - Check the instruction formats first




# Main Control Unit Datapath

- Observation of the Instruction Formats


- R type

 - Opcode: 0
    - Sources: rs and rt
    - Destination: rd




- Load/Store Type

 - Opcode: 35 (load) or 43 (store)
    - Base addr: rs
    - Destination: rt (load)
    - Source: rs(store)




- Branch Type

 - Opcode: 4
    - Base addr: rs
    - Destination: rt







# Control Lines

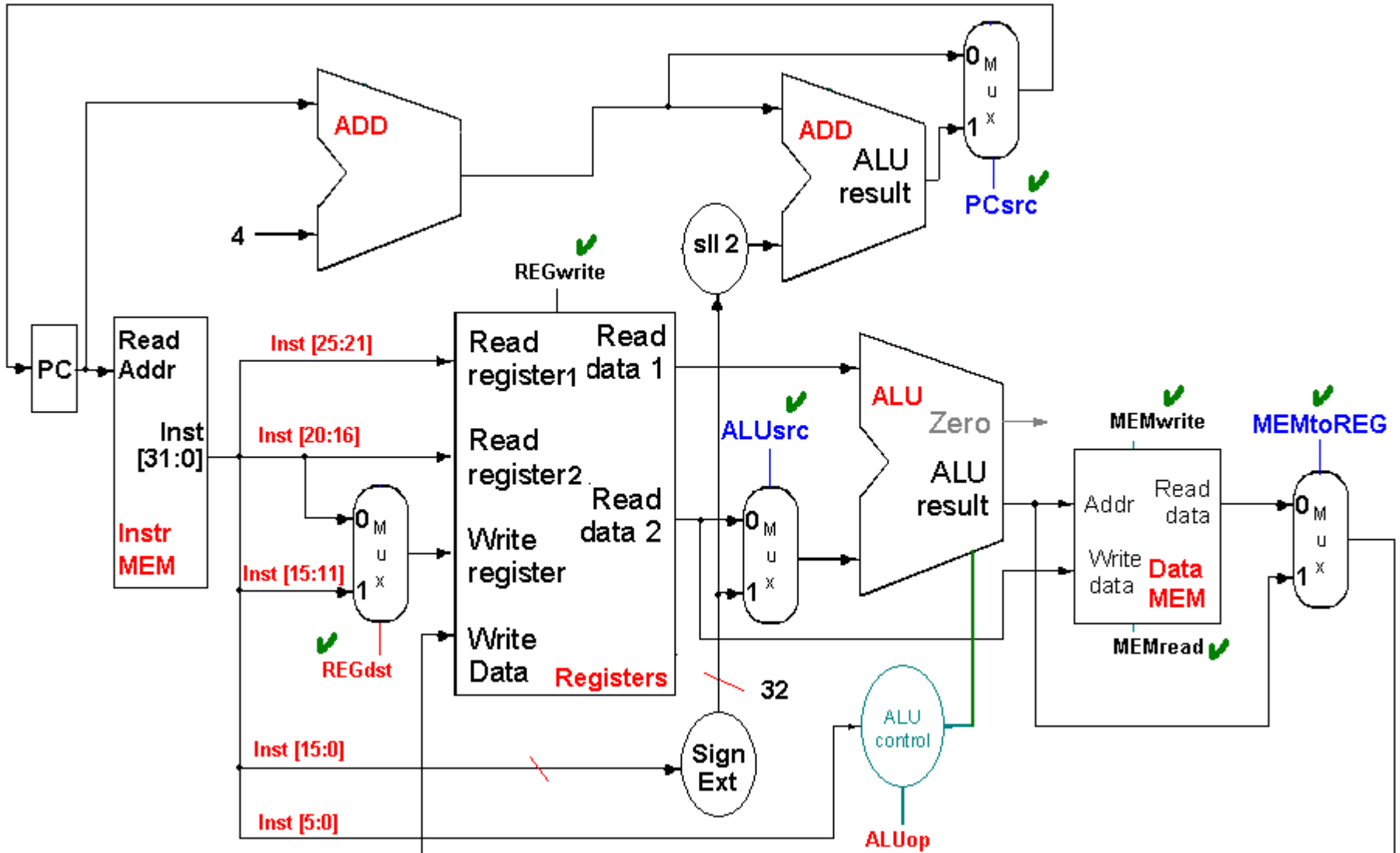


# Control Lines (also for beq)

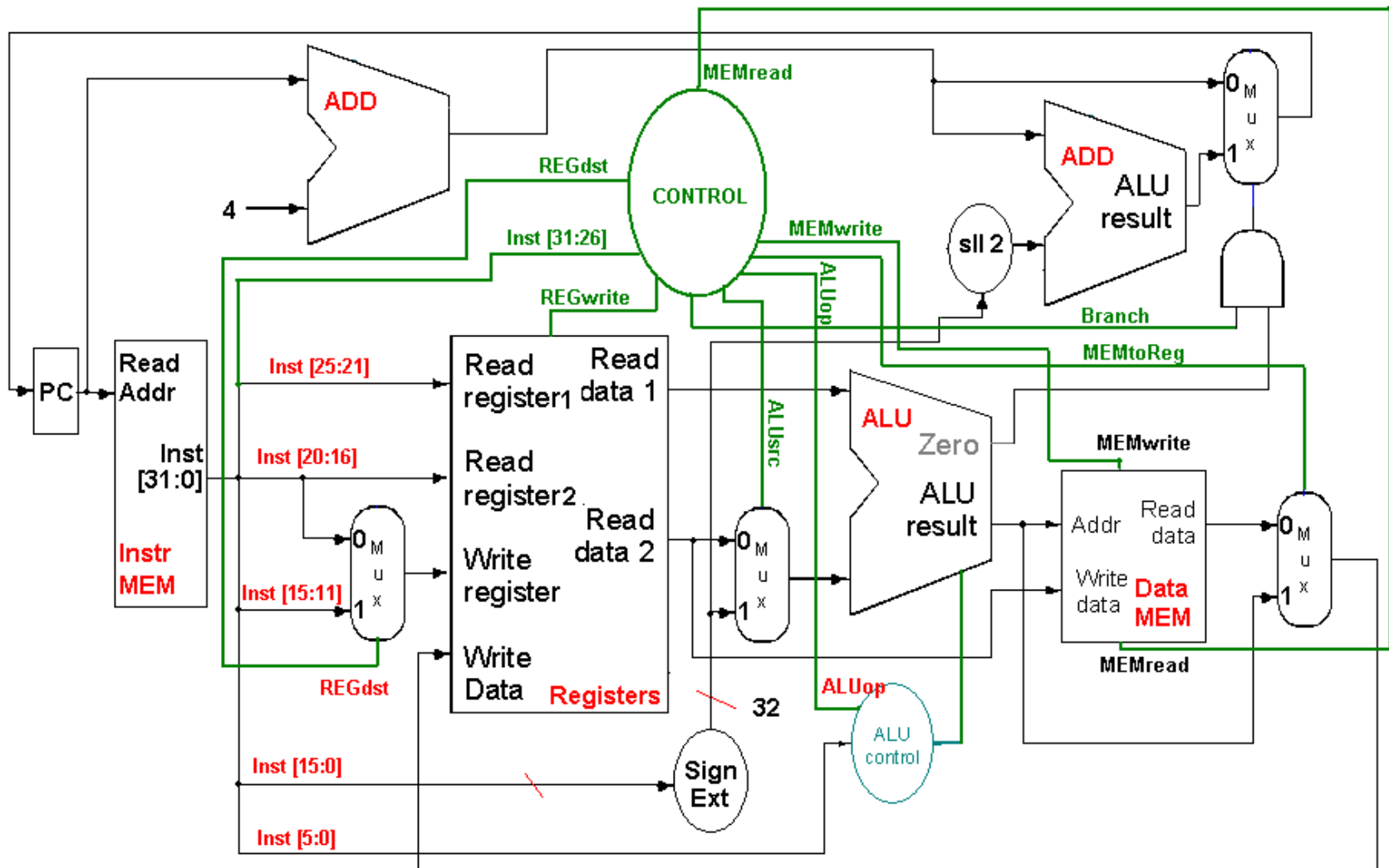

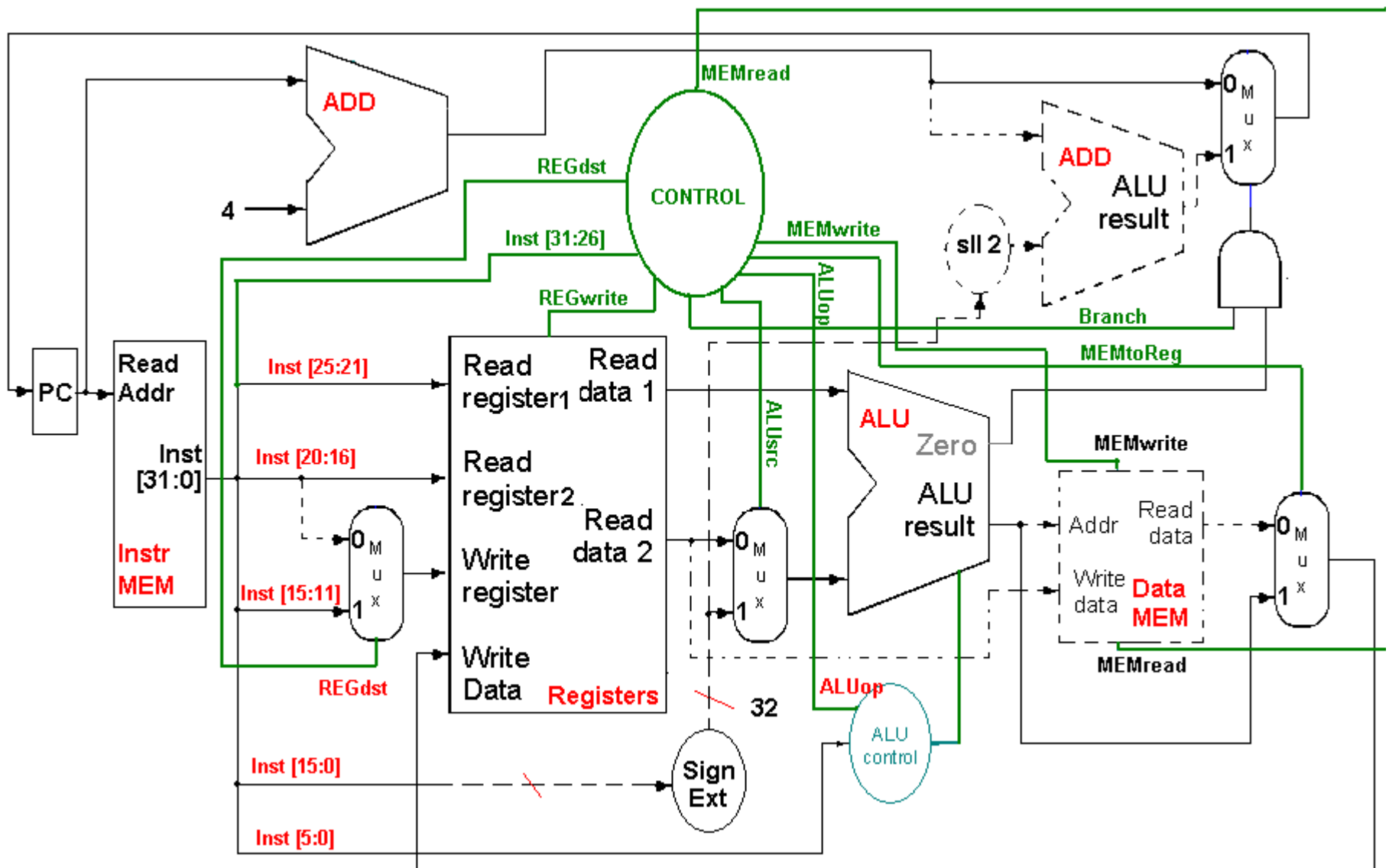
# Operation of Datapath for `add $t1, $t2, $t3`


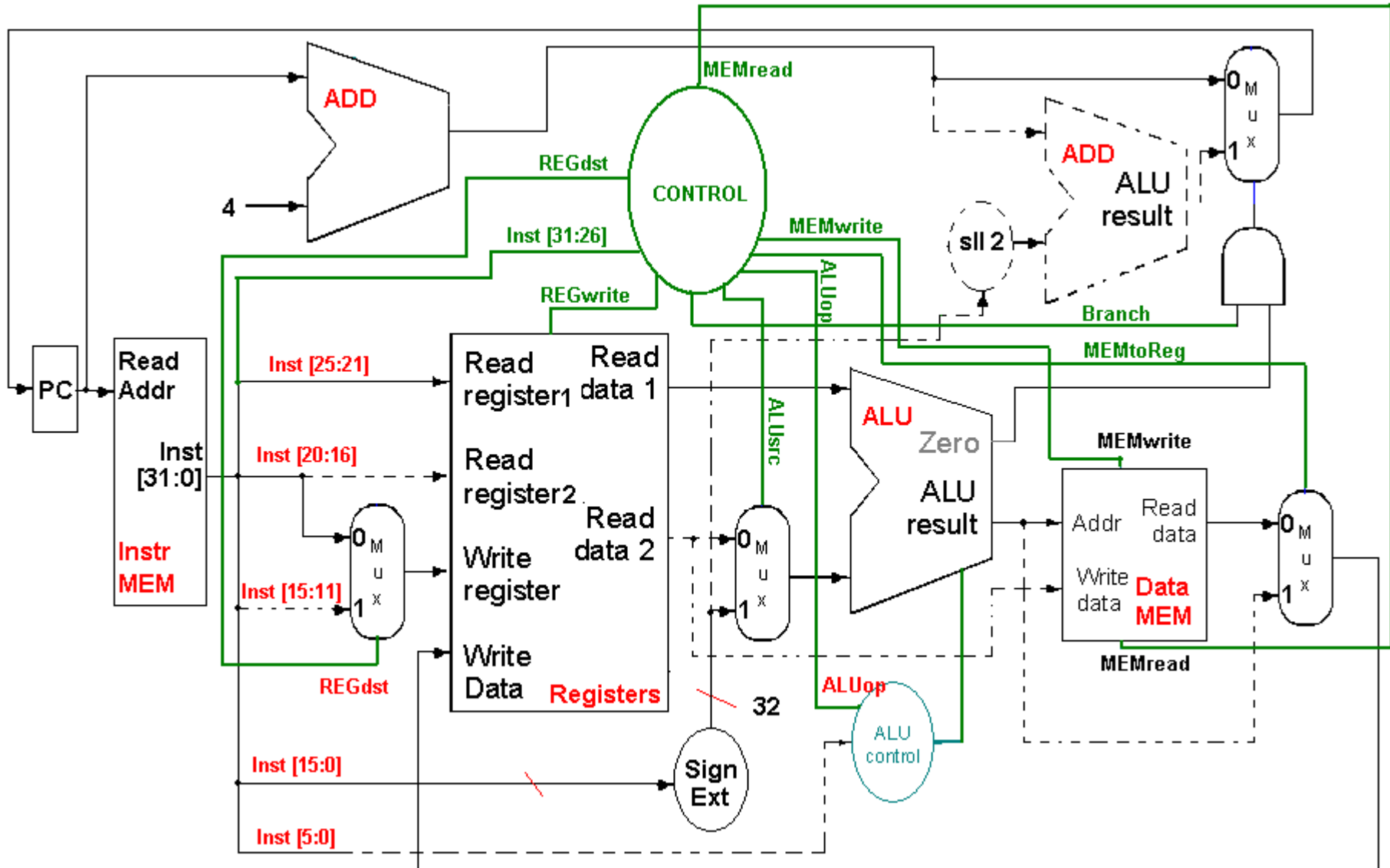
# Operation of Datapath for `lw $t1, offset($t2)`




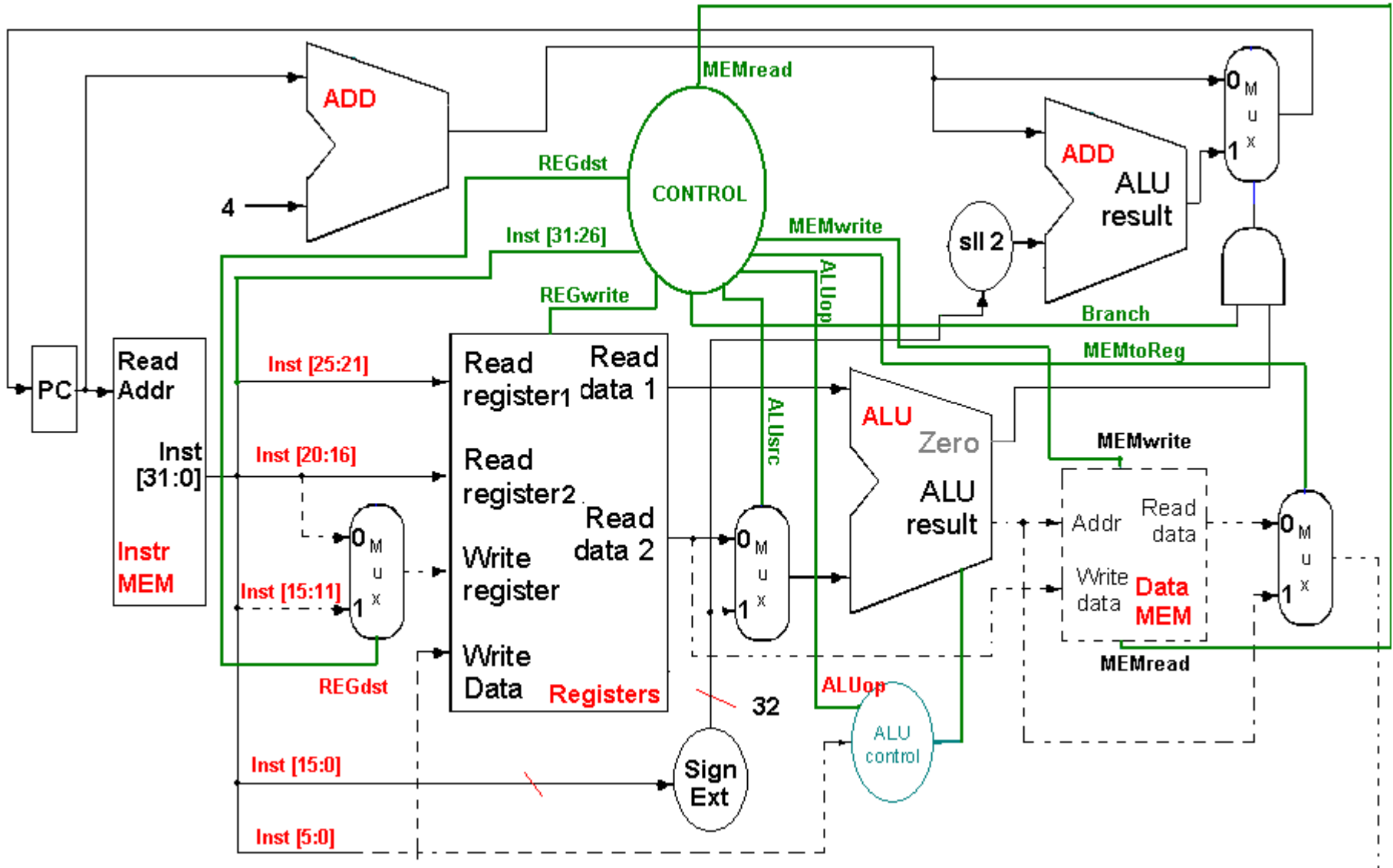
# Operation of Datapath for `beq $t1, $t2, offset`




# Control Implementation

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

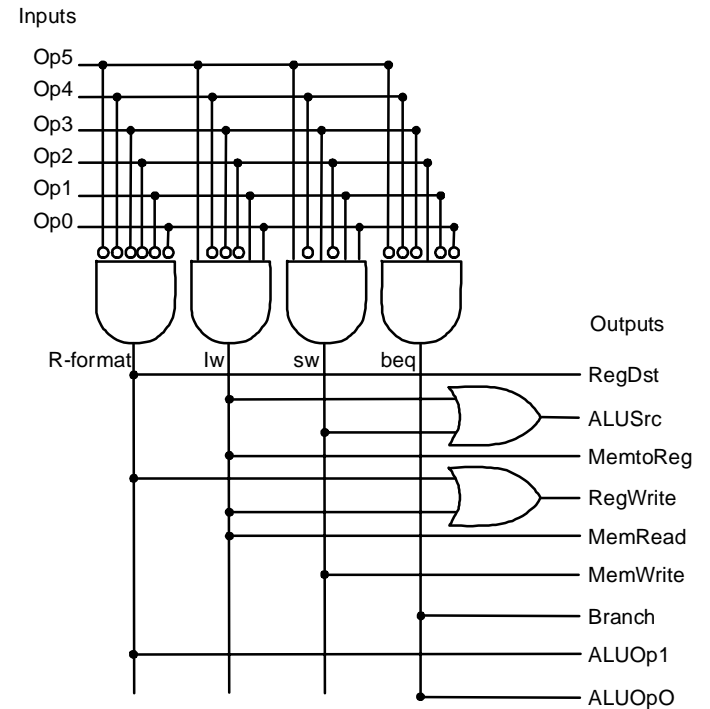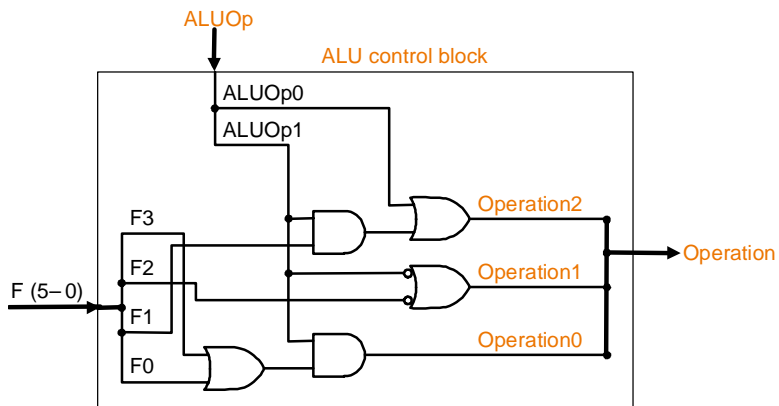
- Simple combinational logic (truth tables)




# Addition Jump Instruction to Datapath

 

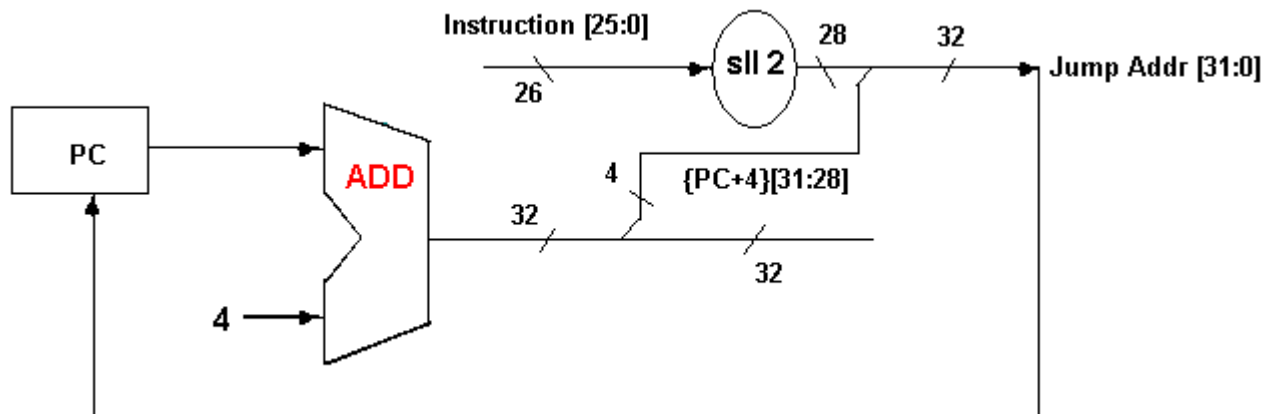- Lower 2 bits of jump address is always 00 (as in branch) **as the last two bits**. Why? Word address --> Byte address
- 26-bit address from immediate field **in the middle**
- Upper 4 bits of the current (PC+4) occupies the **upper 4 bits** of the address
- Summary for jump address [31:0]
  - $\text{jump addr}[31:0] = \{\text{PC}+4\} [31:28] // \text{Instr}[25:0] // 00$



 
# Final Datapath Including R, L, Branch, and Jump







# R-type instruction Flow

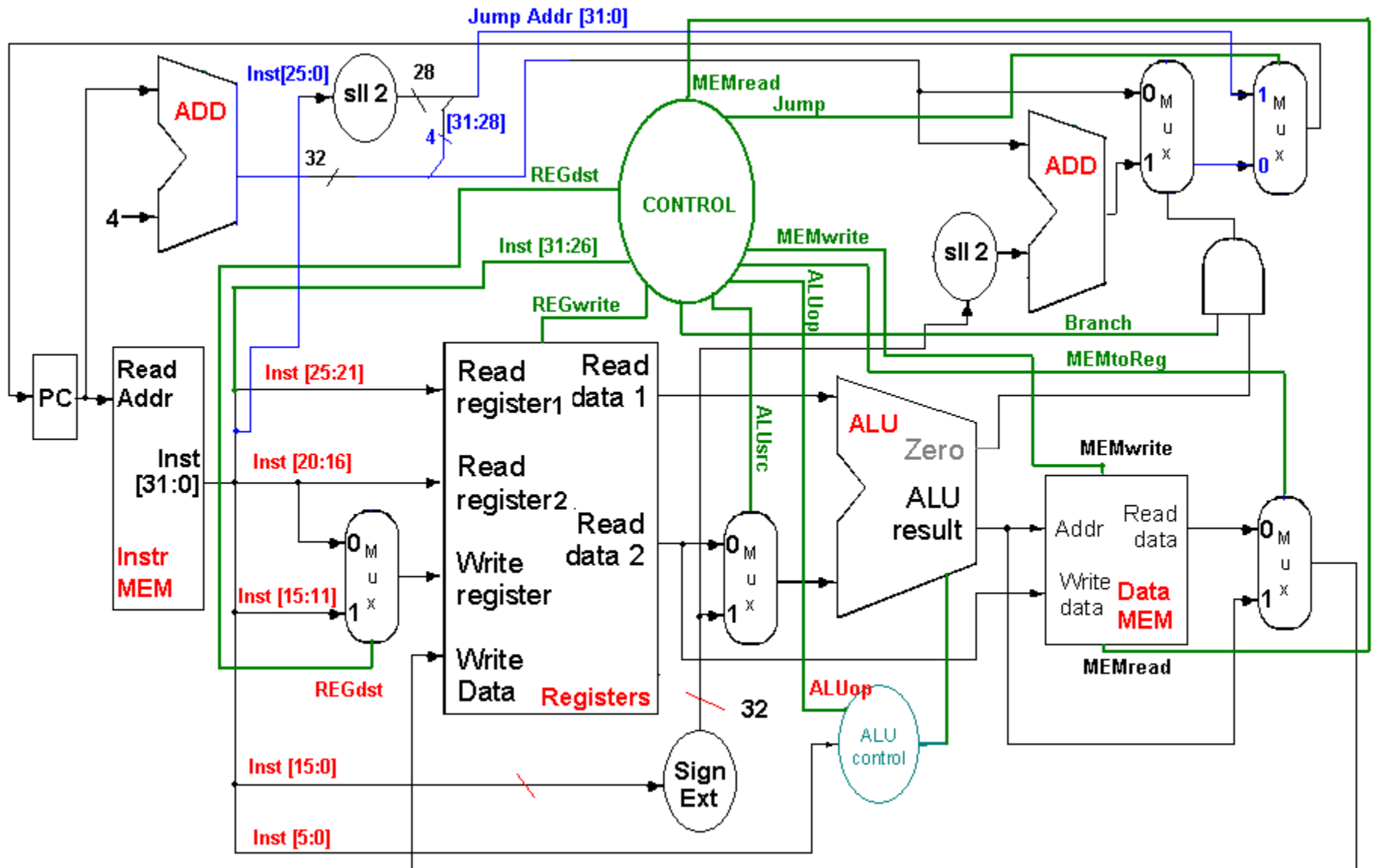


# Load Word Flow

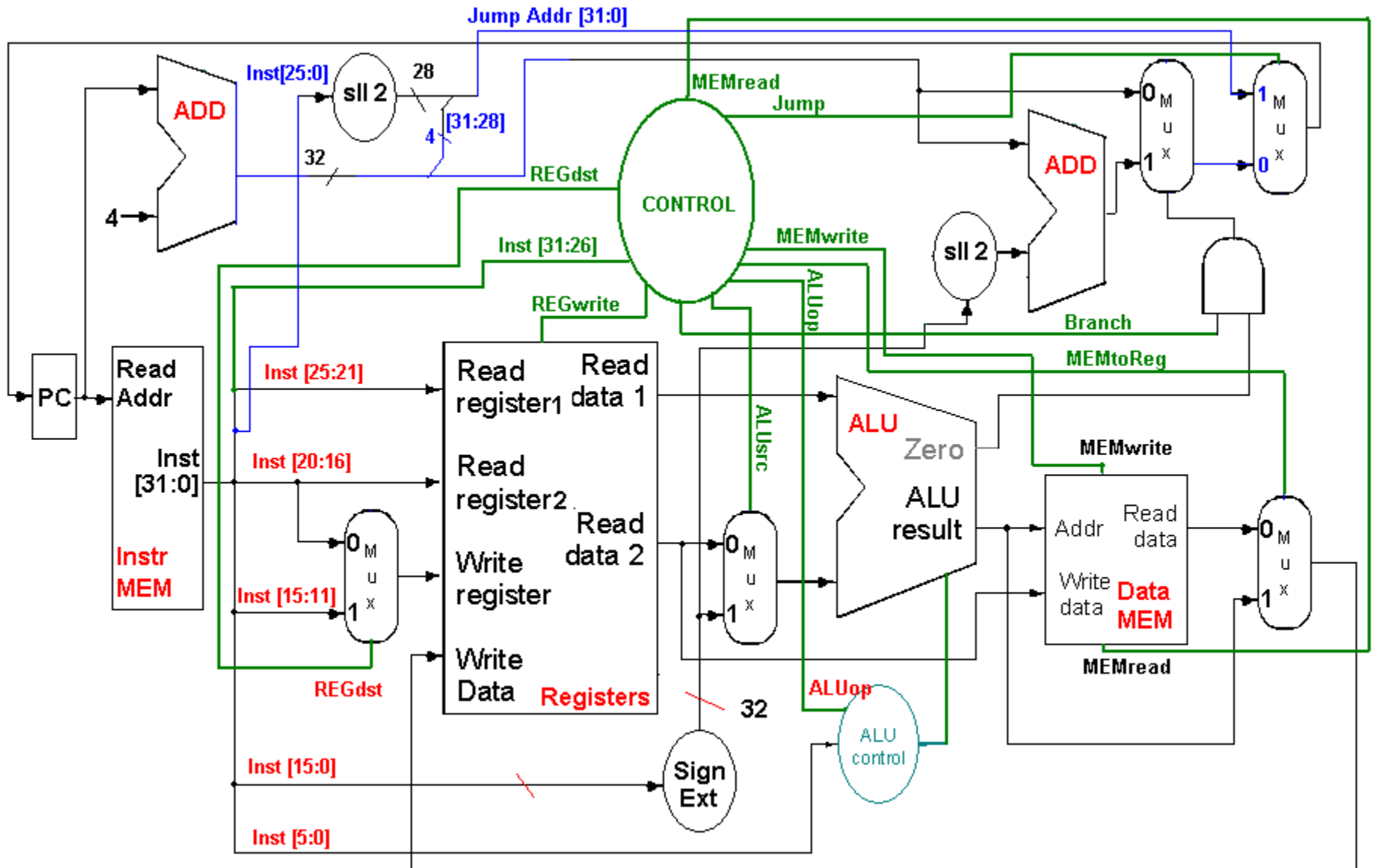

# Branch Instruction Flow

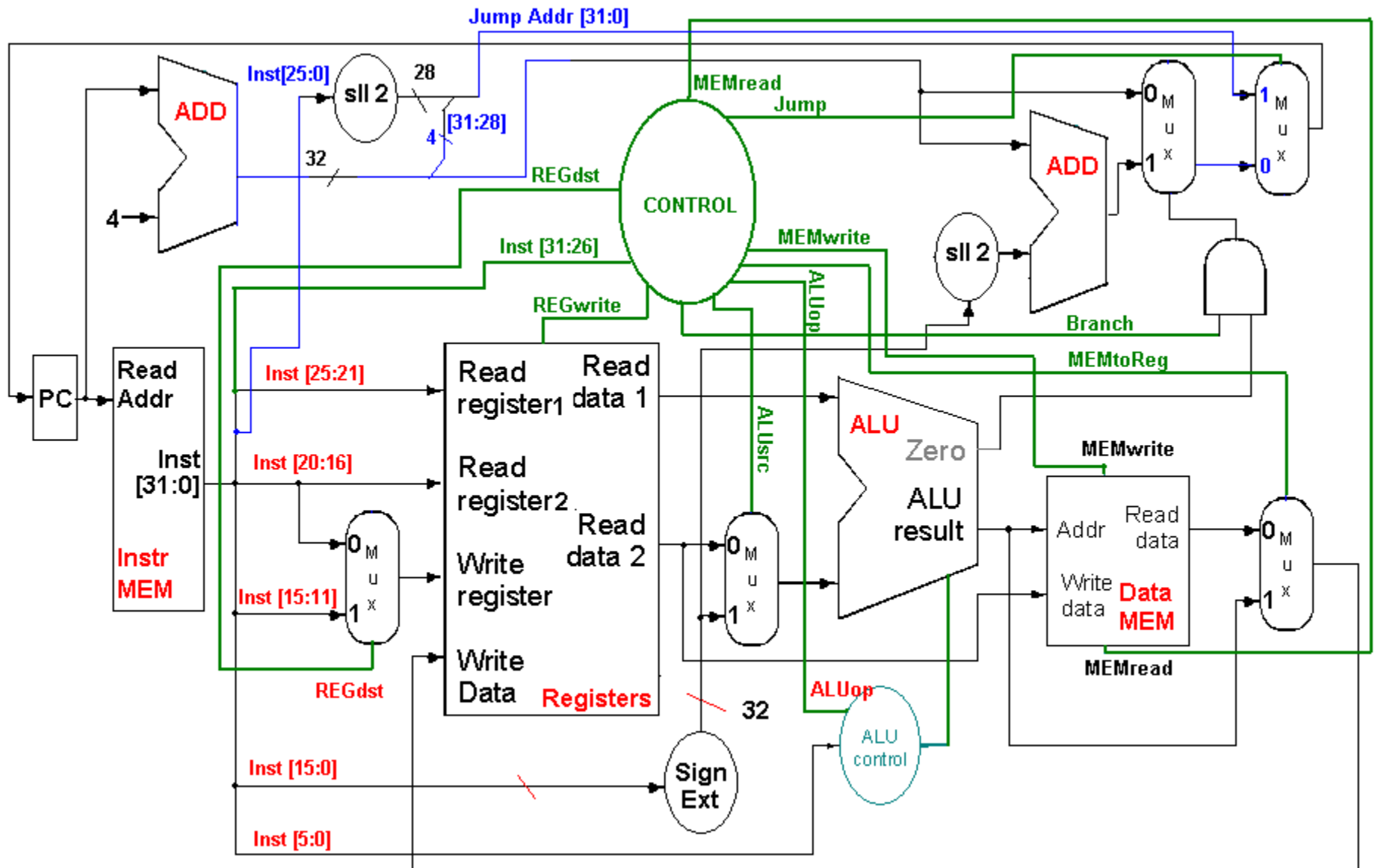

# Jump Instruction Flow

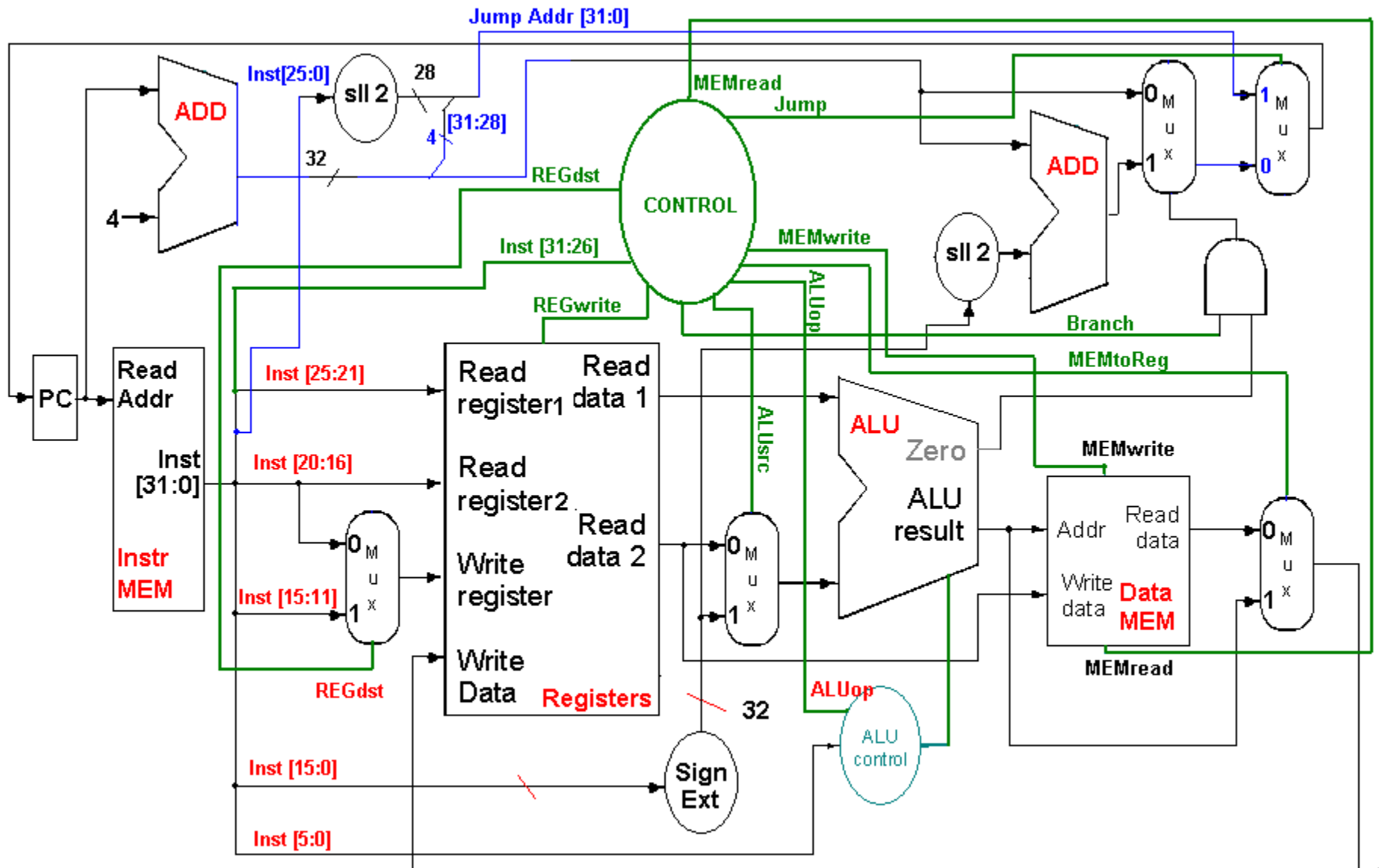


# Single Cycle Implementation--Why Not Used

- So far our implementation is single-cycle design
- Why not used in modern design? Inefficiency!
  - Clock cycle length must be the same for every instruction
  - CPI =1 for every instruction
  - Clock cycle is determined by the longest possible path in the machine
  - Load instruction uses five functional units in series
    - **Instruction Memory**
    - **Register File**
    - **ALU**
    - **Data Memory**
    - **Register File**
  - Several other instruction classes could run in a shorter cycle.
- Each functional unit can be used only once per clock ---some functional units must be duplicated. ---Hardware cost!

# Performance of Single Cycle Machine

- Performance comparison of two approaches for a program run
  - A: Every instruction operates in 1 clock cycle of fixed length
  - B: Every instruction executes in 1 clock cycle using a variable-length clock (only as long as it needs to be)
- Conditions
  - Operational times
    - memory (200ps)
    - ALU and adders (100ps)
    - Register file access (50ps)
    - All others (Negligible)
  - A program has the following instruction mix:
    - load (25%)
    - store (10%)
    - ALU instructions (45%)
    - Branch (15%)
    - Jump (5%)

# Performance Comparison

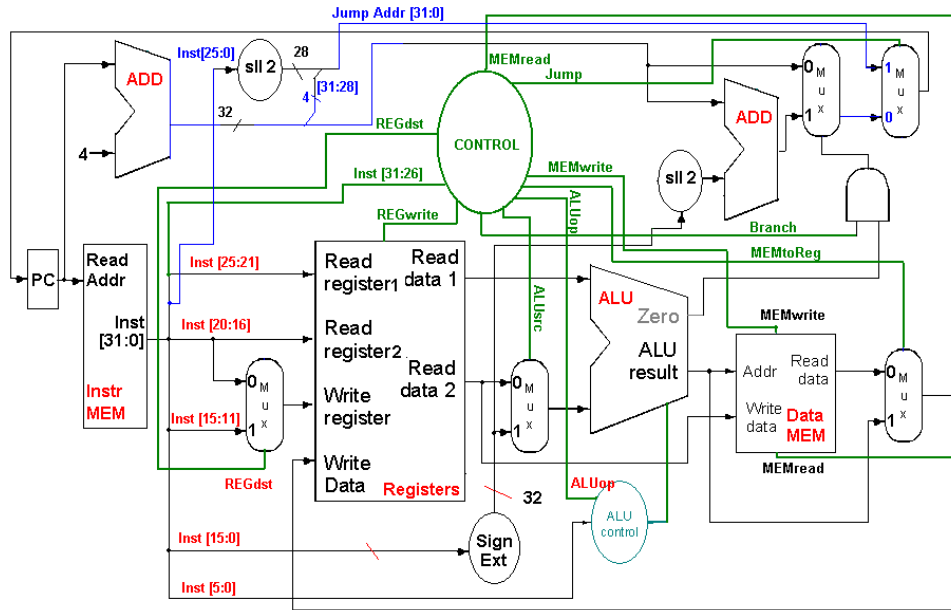

Execution	Instruction Fetch	Register Read	ALU Opr	Memory Access	Register Write
Unit	Instruction Memory	Register File	ALU	Data Memory	Register File
R-type	200	50	100	0	50
Load Word	200	50	100	200	50
Store Word	200	50	100	200	
Branch	200	50	100	0	
Jump	200				

# Comparison, Problem, and an Alternative

- Approach A:
  - single clock cycle time= 600ps
  - Total execution time =  $600 \times 1.0 = 600$  ps
- Approach B:
  - Variable clock cycle times
  - Total execution time  
 $= 600 \times 0.25 + 550 \times 0.1 + 400 \times 0.45 + 350 \times 0.15 + 200 \times 0.5$   
 $= 447.5$  ps
- Performance Comparison
  - $600/447.5=1.34$
- Approach B is faster, but
- Implementation of variable clock cycle length for every instruction is **extremely difficult**
- **Solution: Multi-cycle Implementation**
  - shorter clock cycle for less work class
  - number of clock cycles for different class