# **Motor Control**



Rotor

Rotor Shaft WWW.MWFTR.COM

### Dr. Charles J. Kim



# Department of Electrical and Computer Engineering Howard University



EECE691: Embedded Computing

# **Motors and Control Methods**

- DC Motor Control
  - Forward, Reverse, Stop
  - Control by Manual Switch
  - Control by Relay
  - Control by Transistor
  - Control by H-Bridge
  - Control by Motor Driver
- DC Stepper Motor Control
  - Bipolar Stepper Motor
    - Control Driver
  - Unipolar Stepper Motor
    - Control Driver








### **DC Motors and Manual Control**








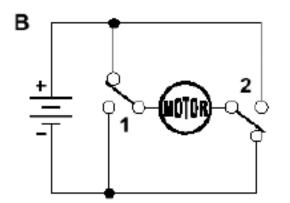


1 UP, 2 UP	= STOP [BRAKE)
1 UP, 2 DOWN	= FORWARD
1 DOWN, 2 UP	= REVERSE
1 DOWN, 2 DOWN	= STOP (BRAKE)

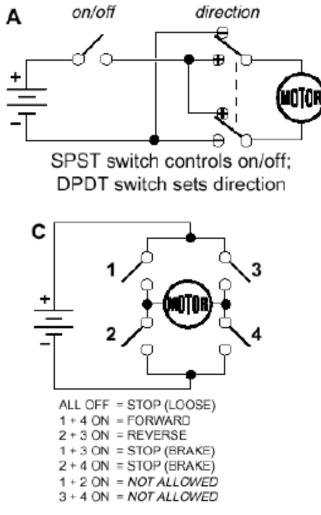A pair of SPDT switches controls on/off and direction; brakes to a stop



Four SPST switches (H bridge) control on/off, direction & braking

### **DC Motors and Manual Control**

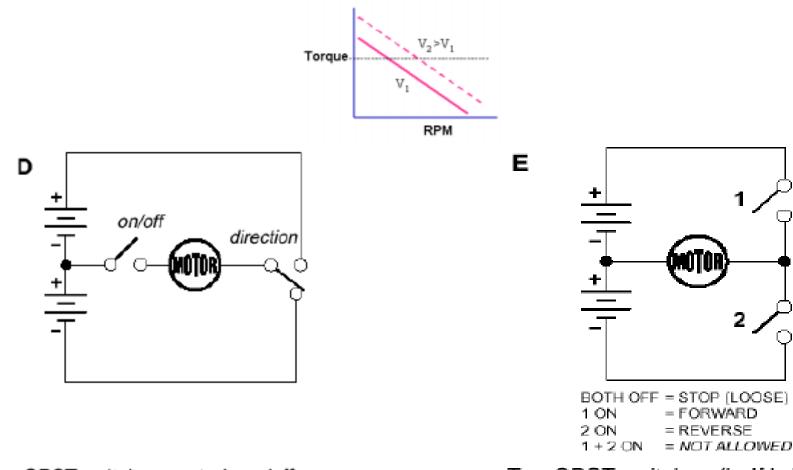

SPST switches controls on/off; SPDT sets direction Two SPST switches (half bridge) control on/off & direction

# **Selector Switch**





SPST: Single pole single throw. SPDT: Single pole double throw. DPST: Double pole single throw. DPDT: Double pole double throw DP3T: Double pole three throw. DP4T: Double pole four throw.
3PDT: Three pole double throw.
3P3T: Three pole three throw.








### **Selector Switch Diagram**


<b>Form A - SPST-NO</b>	Form X - SPST-DB-NO
Single Pole - Single Throw	Single Pole - Single Throw
Normally Open	Double Break - Normally Open
Form AA - DPST-NO	<b>Form XX - DPST-DB-NO</b>
Double Pole - Single Throw	Double Pole - Single ThrowDouble
Normally Open	Break - Normally Open
Form B - SPST-NC Single Pole - Single Throw Normally Closed	o <u> </u>

# **Switch Diagram**


G G Form BB - DPST-NC Double Pole - Single Throw Normally Closed	o
Generation C - SPDT Single Pole - Double Throw	Generation Form Z - SPDT-DB Single Pole - Double Throw Double Break
Form CC - DPDT Double Pole - Double Throw	O I   O I

### **DC Motor Control by Relay**

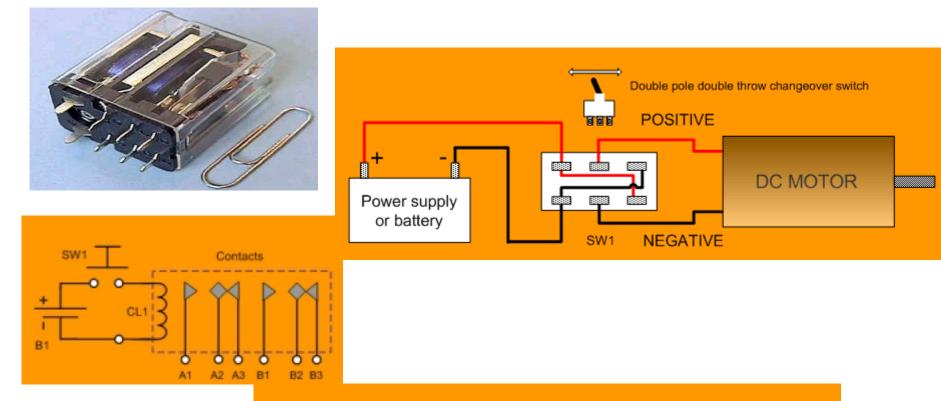

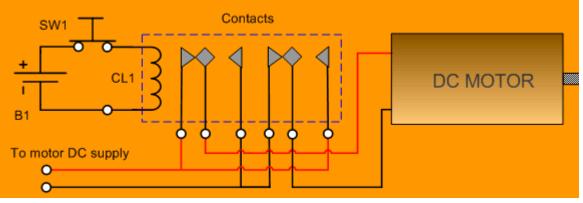


### Motor Control using a Relay

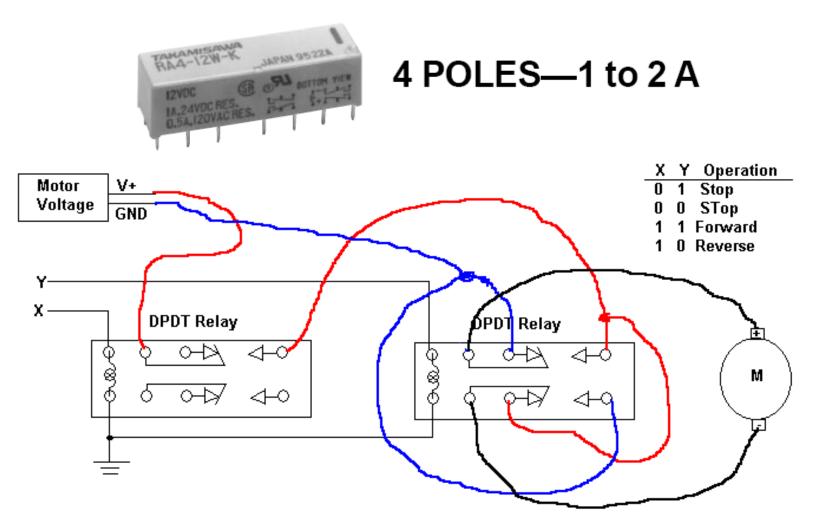

\*NOTE: Action Y first, then apply X
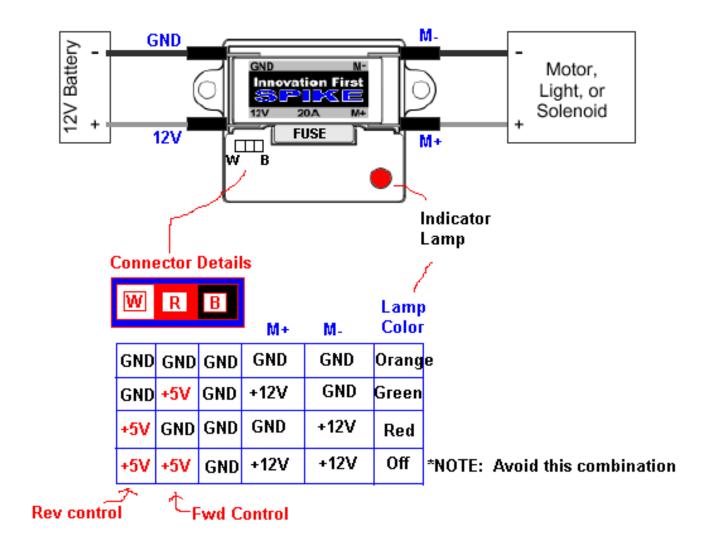
### DC Motor Control using High Current Relay



### **DC Motor Control with Transistor**




TIP41 Series(TIP41/41A/41B/41C)


#### Medium Power Linear Switching Applications



1.Base 2.Collector 3.Emitter

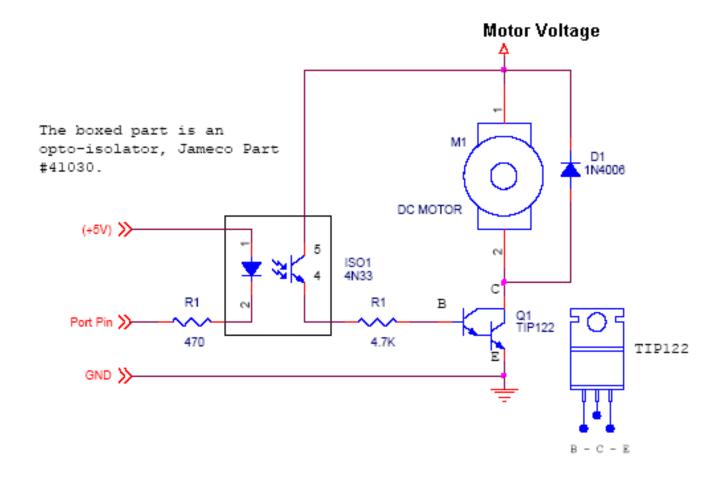

### **Transistors for Control**

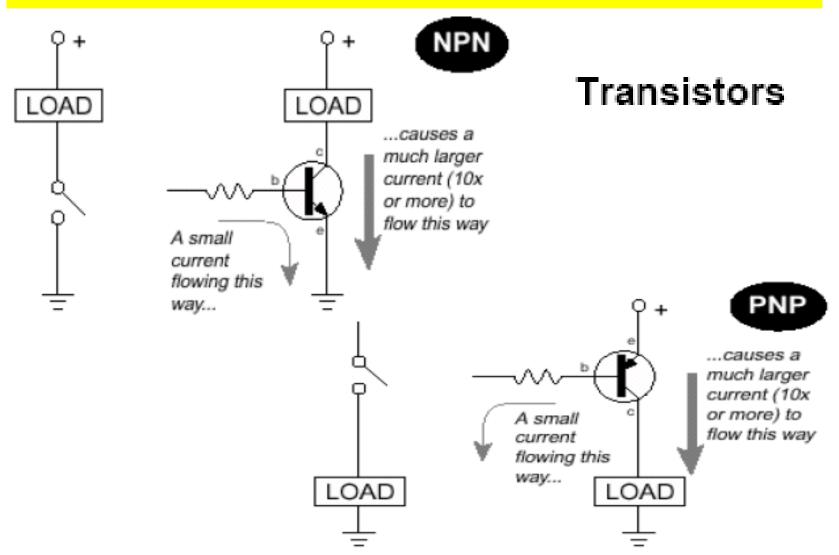


### **Transistor vs. MOSFET**

В

D


Gate B

Gate D

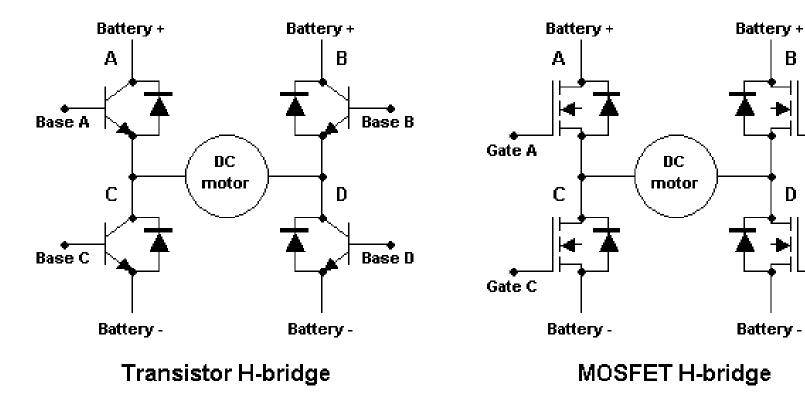
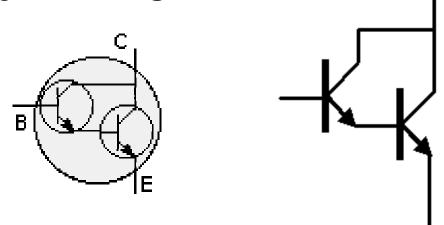
# Darlington (Transistor)

- Connection of two bipolar transistors in tandem in a single device.
- High gain (or beta)
- Less space
- Invented by Bell Laboratories engineer
   Sidney Darlington.




### **Transistor Array**




#### MC1413, MC1413B, NCV1413B High Voltage, High Current

Darlington Transistor Arrays

**ON Semiconductor®** 

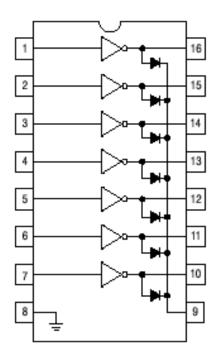



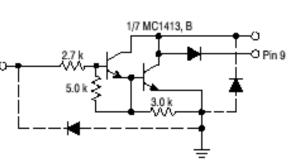


### **Darlington Array**




#### FEATURES

- TTL, DTL, PMOS, or CMOS-Compatible Inputs
- Output Current to 500 mA
- Output Voltage to 95 V
- Transient-Protected Outputs
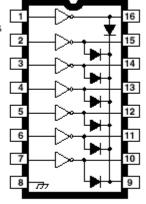
#### HIGH-VOLTAGE, HIGH-CURRENT DARLINGTON ARRAYS




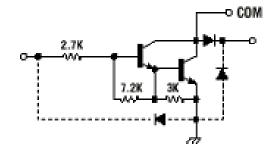


#### TYPICAL APPLICATIONS


Ideally suited for interfacing between low-level logic circuitry and multiple peripheral power loads

#### UNIPOLAR STEPPER CONTROL

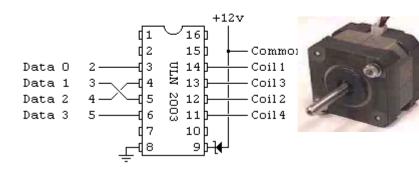

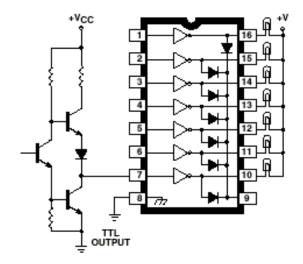


### **Darlington with DPDT relays**

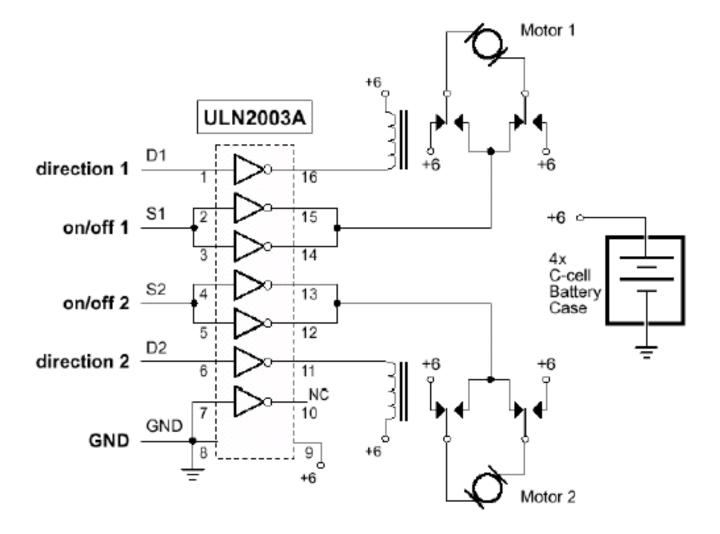


### **MOSFET for Motor Control**

# Міскоснір ТС4423/ТС4424/ТС4425
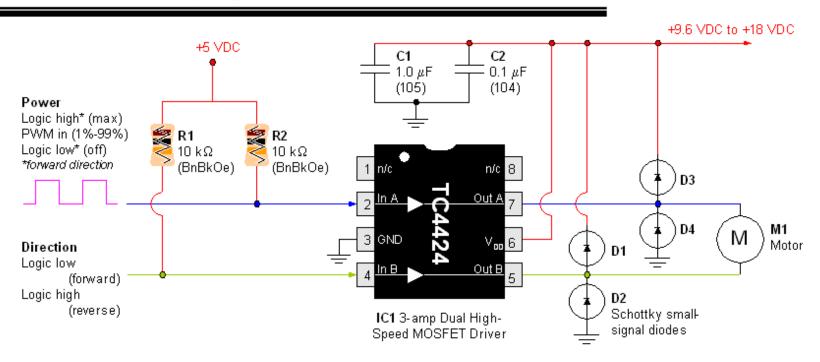
#### **3A Dual High-Speed Power MOSFET Drivers**





### **DC Motor H-Bridge Control**

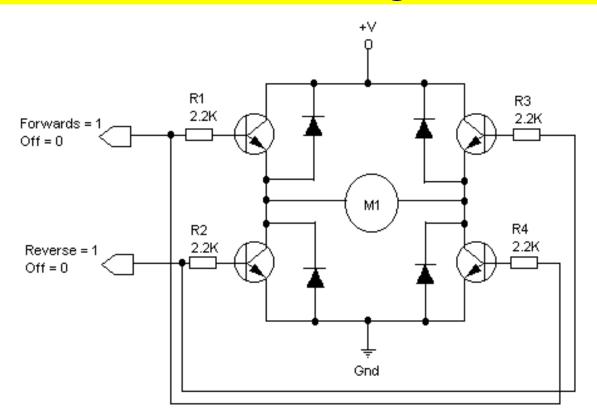


Diode 1N4002 Transistor TIP41 NPN Power Transistor Resistor 2.2 K 0.25 W

### **Rotation Control using H-Bridge**

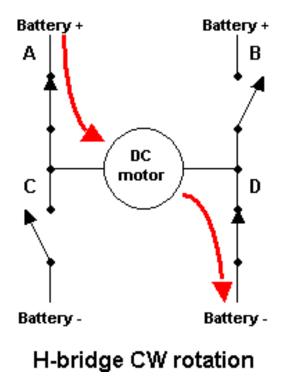


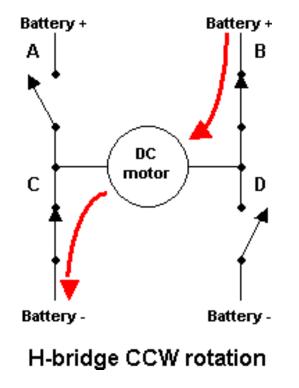


### **Standard H-Bridge Control**

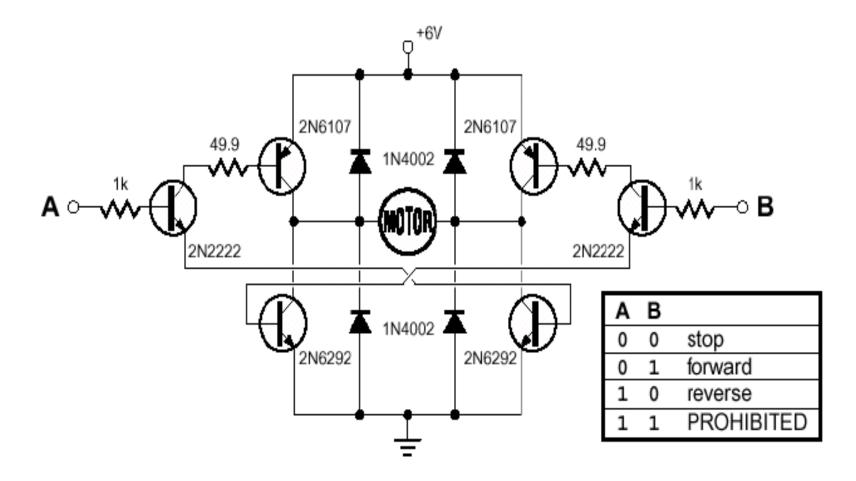

### Full/Half H-Bridge

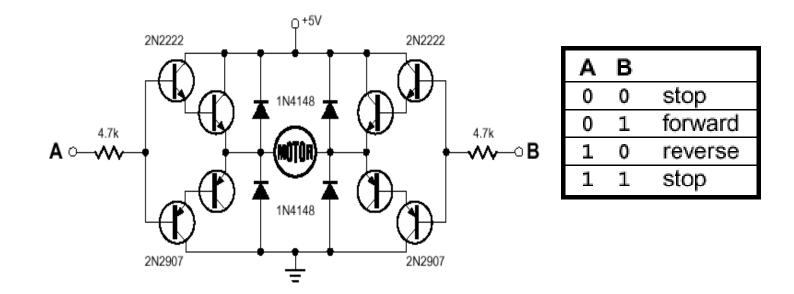

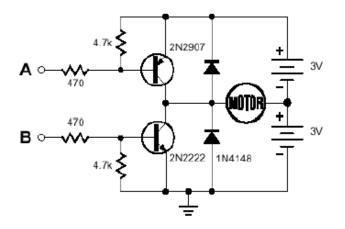


Α	в	
0	0	forward
0	1	PROHIBITED
1	0	stop
1	1	reverse


### **Bridge Motor Driver**


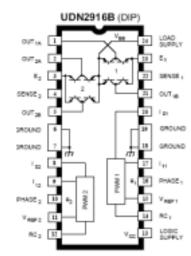
#### DUAL FULL-BRIDGE PWM MOTOR DRIVER


a bipolar stepper motor or bidirectionally control two dc motors.




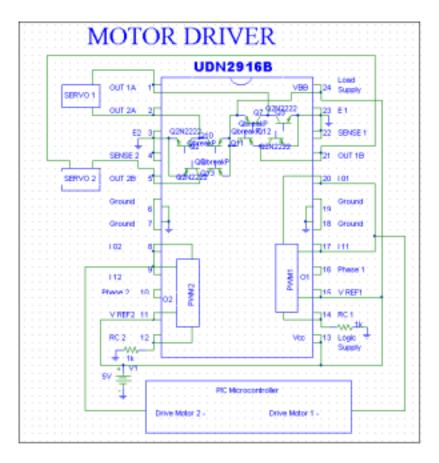

### **Bridge Driver**



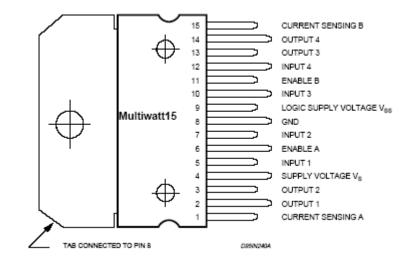

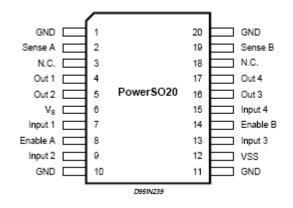


### **H-Bridge Driver**



National Semiconductor

### LMD18200 3A, 55V H-Bridge

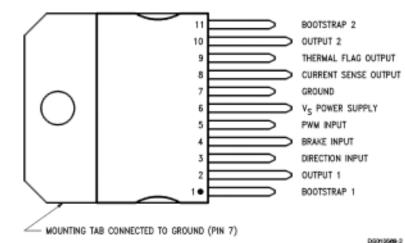


		$\cup$	
BOOTSTRAP 1A -	1	24	BOOTSTRAP 2A
VOUT 1A	2	23	VOUT 2A
DIRECTION A-	з	22	- Thermal Flag A
BRAKE A	4	21	- Current Sense A
PWM A -	5	20	- Signal GND A
V <sub>SA</sub> -	6	19	- Power GND A
V <sub>S В</sub> -	7	18	- Power GND B
Signal GND B-	8	17	- PWM B
Current Sense B-	9	16	- BRAKE B
Thermal Flag B-	10	15	DIRECTION B
VOUT 2B	11	14	VOUT 1B
BOOTSTRAP 2B-	12	13	BOOTSTRAP 1B
			1

24-Lead Dual-In-Line Package Top View Order Number LMD18200-2D-QV 5962-9232501VXA LMD18200-2D/883 5962-9232501MXA

05010509-25

11-Lead TO-220 Package Top View Order Number LMD18200T

### **Bridge Driver**

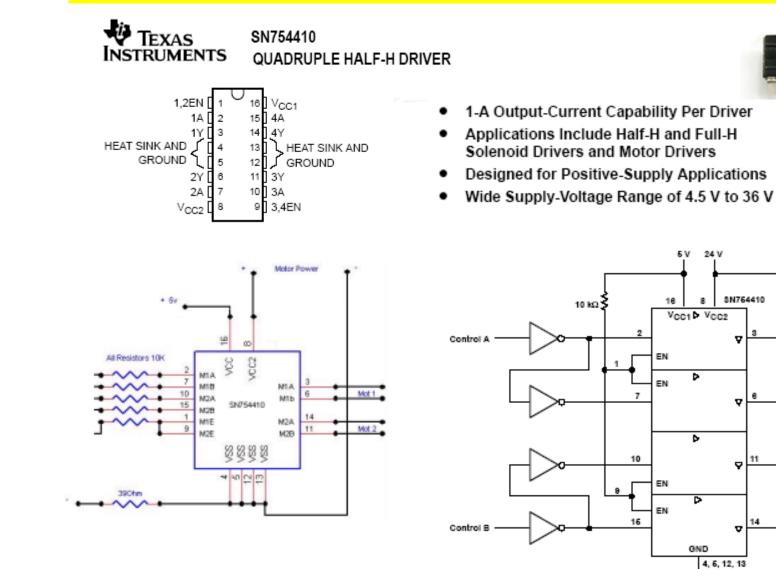



÷

11

14


Ť

Ŧ

¢1

Motor

### **DC Motor Driver**

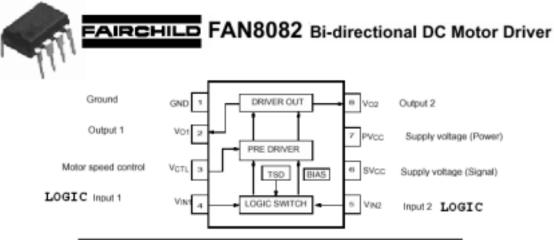

Parameter	Symbol	Operating voltage range
Operating supply voltage	SVcc,PVcc	7 ~ 18


#### 


#### LOGIC INPUT & OUTPUT TABLE

Input		Output		Motor
Pin #4	Pin #5	Pin #2	Pin #8	motor
Low	Low	*Low	*Low	Brake
High	Low	High	Low	Forward
Low	High	Low	High	Reverse
High	High	*Low	"Low	Brake


### **Stepper Motors**




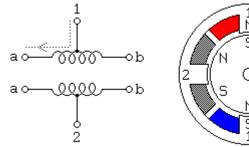


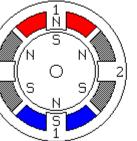




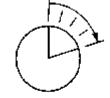

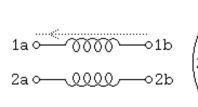

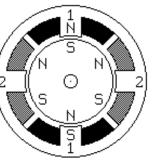

2-Phase Bipolar

 



### **Stepper Motors**








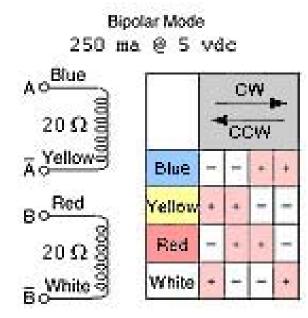

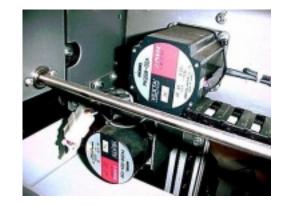


### **Stepper Motor Structure**

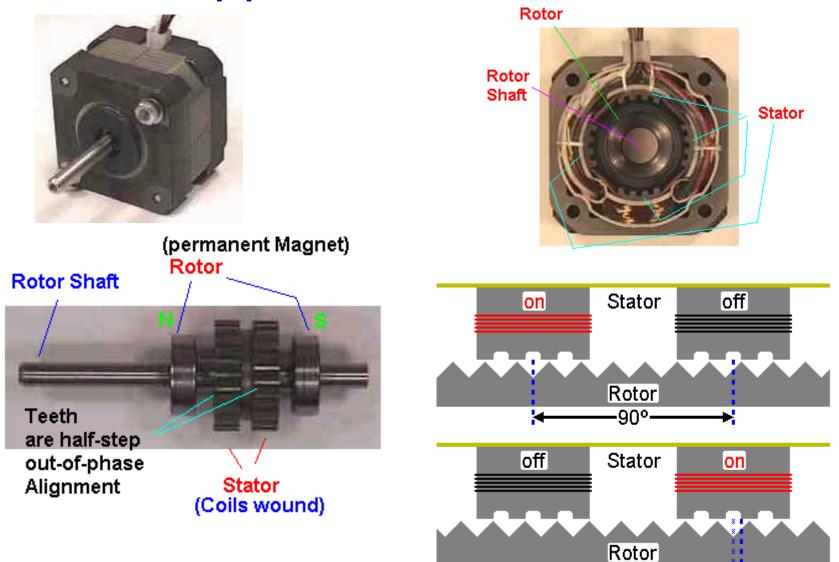



3.6°→ ←
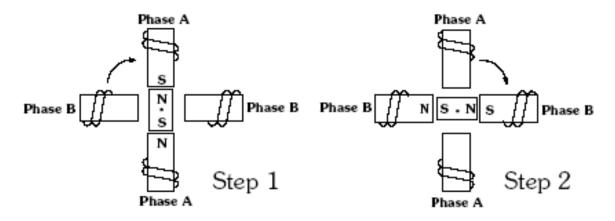
### **Stepper Motor - Theory**

- Magnetic Field Created by Energized Coil
- Steps for "One phase On" for two phase stepping motor




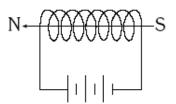


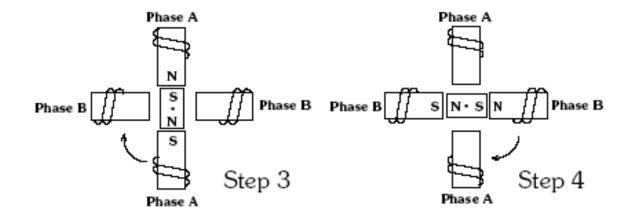



### **Stepper Motor Theory**

• "Two Phase On" for a 2-phase stepper

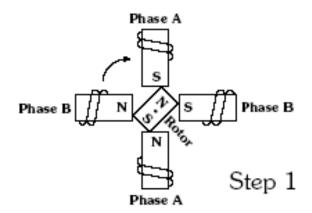


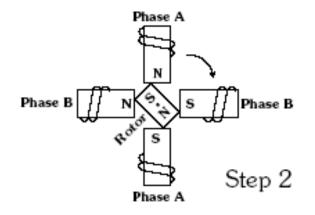


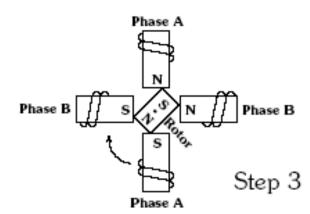


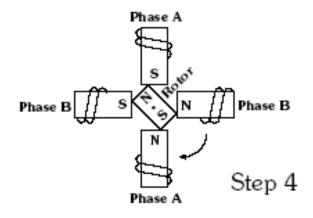


### Half-Stepping

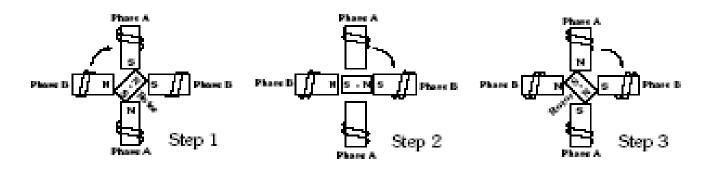

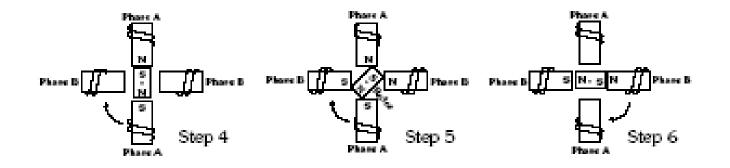


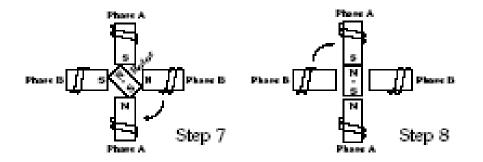



### Stepper Motor – Speed vs. Torque

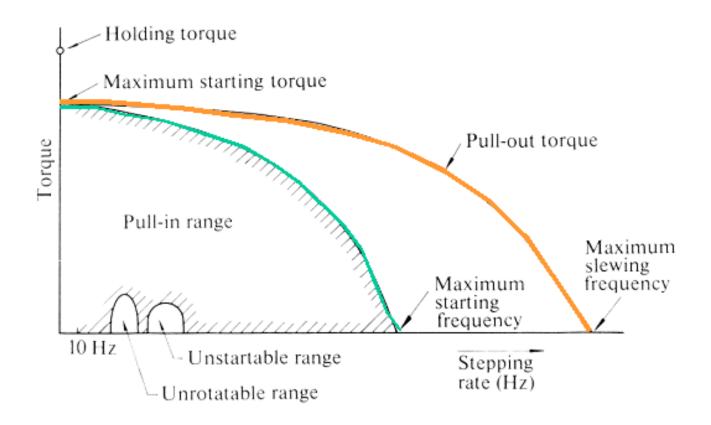
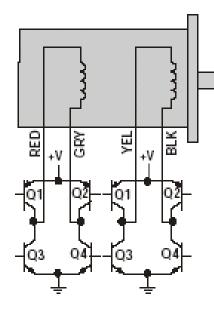
### **Sequence for Unipolar and Bipolar**



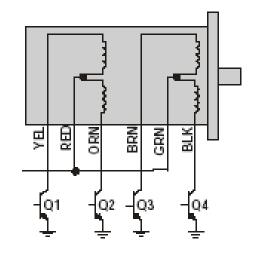

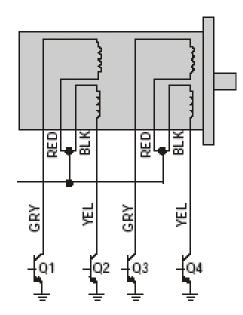

#### BIPOLAR


ROTATION	Step	Q <sub>1</sub> -Q <sub>4</sub>	$Q_{g} Q_{s}$	Q <sub>s</sub> -Q <sub>s</sub>	Q,-Q,	NOL
Ĕ	1	ON	OFF	ÖN	OFF	Ψ
<u>⊥</u> ≽	2	ON	OFF	OFF	ON	
ò	3	OFF	ON	OFF	ON	ROT
	4	OFF	ON	ON	OFF	SW
S	1	ON	OFF	ON	OFF	00

Normal 4-Step Sequence

UNIPOLAR

ROTATION	Step	Q,	Q <sub>2</sub>	Q,	Q,	NC I
Ē	1	ON	OFF	ON	OFF	
ΤA	2	ON	OFF	OFF	ON	Ê
O.	3	OFF	ON	OFF	ON	ģ
	4	OFF	ON	ON	OFF	
CW	1	ON	OFF	ON	OFF	C CMM


### **Bipolar Stepper Control Sequence**

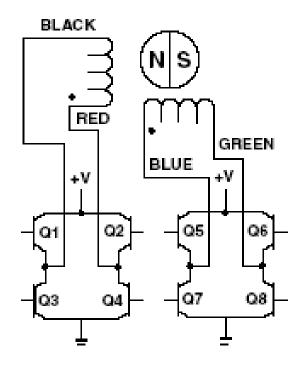

Ś
Rotation
t

_	Bipolar					1
CW.	Step	Q2-Q3	Q1-Q4	Q6-Q7	Q5-Q8	-
R	1	ON	OFF	ON	OFF	tio
Rotation	2	OFF	ON	ON	OFF	Rotation
tio	3	OFF	ON	OFF	ON	
<b>→</b>	4	ON	OFF	OFF	ON	CCW
•	1	ON	OFF	ON	OFF	Ŭ

# **Unipolar Stepper Motor Sequence**

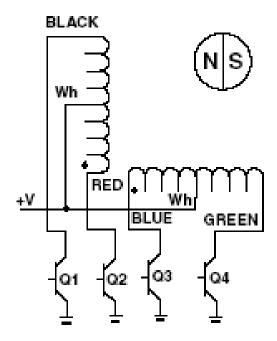

CW Rotation →

CW	Unipolar					1
a.	Step	Q1	Q2	Q3	Q4	Ş
2	1	ON	OFF	ON	OFF	] ;
÷	2	OFF	ON	ON	OFF	Rotation
3	3	OFF	ON	OFF	ON	
•	4	ON	OFF	OFF	ON	
	1	ON	OFF	ON	OFF	

# **Bipolar Stepper Motor Driver**





#### MOTOROLA MC3479 Stepper Motor Driver
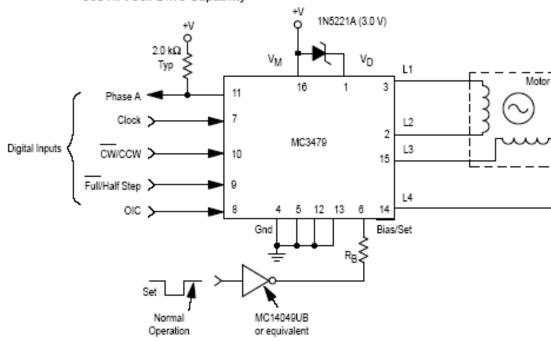
#### Stepper Motor Driver

two-phase stepper motor in the bipolar mode.

- Single Supply Operation: 7.2 to 16.5 V
- · 350 mA/Coil Drive Capability



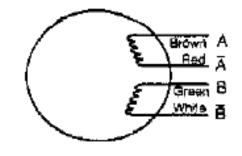

Step	A	В	Ā	B
1	+	+	-	-
2	•	+	i + i	-
3	•	•	+ 1	ŧ
4	+	•		÷
5	+	+	-	-

# **Bipolar Driver**




Part Number	Package
UDN2916B	24-Pin DIP
UDN2916EB	44-Lead PLCC
UDN2916LB	24-Lead SOIC


#### DUAL FULL-BRIDGE PWM MOTOR DRIVER For BIPOLAR STEPPER /DC

#### FEATURES

750 mA Continuous Output Current

45 V Output Sustaining Voltage

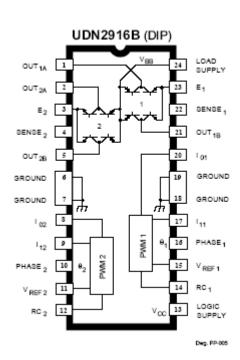

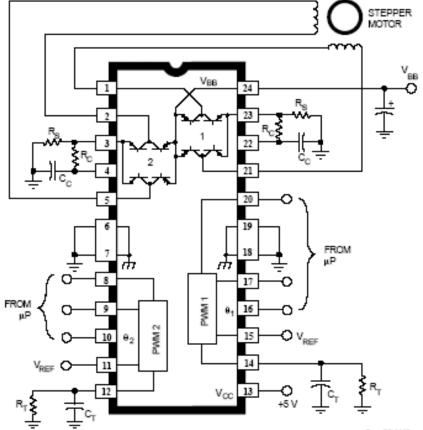

# **Unipolar Driver**










1.5 A Maximum Output Current

35 V Output Sustaining Voltage

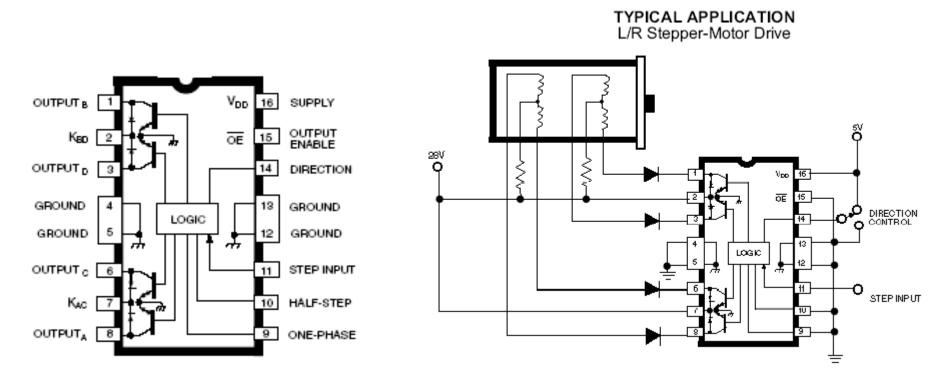



## **Unipolar Stepper Driver**



#### SLA7024M, SLA7026M, and SMA7029M
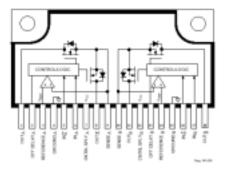
#### HIGH-CURRENT PWM, UNIPOLAR STEPPER MOTOR CONTROLLER/DRIVERS




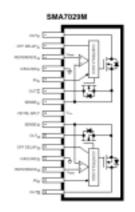

#### 2-PHASE (FULL STEP) OPERATION for SLA7024M and SLA7026M

Sequence	0	1	2	3	0
Input A	Н	L	L	н	Н
Input A	L	Н	н	L	L
Input B	Н	Н	L	L	н
Input B	L	L	Н	Н	L
Outputs ON	AB	ΑB	AB	AB	AB

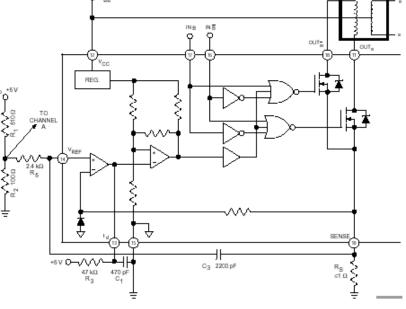TYPICAL STEPPER MOTOR APPLICATIONS (Half of Each Device Shown) SLA7024M and SLA7026M



SLA7024M and SLA7026M

## **Motors**




#### 12VDC Bipolar Stepper Motor 12VDC Unipolar Stepper Motor 12VDC Unipolar Stepper Motor 3.6' / Step 3.6" / Step .09' / Step . No. of phases: 2 No. of phases: 4 · No. of phases: 4 · Detent torque: 400 g-cm Detent torque: 80 g-cm · Detent torque: 80 g-cm · Holding torque: 600 g-cm · Holding torque: 600 g-cm · Holding torque: 400 g-cm Phase resistance: 200Ω Phase resistance: 25Ω Phase resistance: 75Ω · Phase inductance: 31mH · Phase inductance: 39mH · Phase inductance: 49.5mH Current: 480mA · Current: 150mA · Current: 60mA Mounting hole size: 0.11" · Mounting hole size: 0.11" · Mounting hole size: 0.14" Shaft size: 0.43"L x 0.197"Dia. Shaft size: 0.43"L x 0.197"Dia. Shaft size: 0.36"L x 0.194"Dia. Motor size: 1.66"Dia. x 1.31"H Motor size: 1.66 Dia. x 1.28 H Motor size: 1.18"Dia. x 0.68"H Part No. Mfr. Cross Ref. No. Mir. Cross Ref. No. Part No. Mir. Cross Ref. No. 1 10 50 Part No. 1 10 50 1 10 50 105881 SM4203 \$5.99 \$5.59 \$4.95 105890 SM4200 \$8.79 \$7.85 \$6.99 173180 30BYJ02AH \$11.49 \$10.35 \$9.35

#### Bipolar and Unipolar Stepper Motors




Part	Mir. Cross		Step	No. of	Drive	Volt.	Phase Resis.	Curr.	Phase Inductance	Detent Torque	Holding Torque	Mounting Hole Space	Mounting Holes	Shaft Dia.	Shaft Length	Motor Dia.	Motor Height		Pricing	
Number	Ref. No.	Fig.	Angle	Phases	System	(VDC)	(Ohms)	(mA)	(mH)	(g-cm)	(g-cm)	Diagonal (In.)	(In.)	(in.)	(In.)	(in.)	(In.)	1	10	50
117954	LB82773-M1	1	7.5°	2	Bipolar	5	6	800	7	100	1080	2.60	1.95	0.250	0.75	2.25	1.00	\$3.79	\$2.99	\$2.25
163395	5017-935 <sup>1</sup>	2	0.9°	2	Bipolar	8.4	30	280	25	36	791	1.73	0.15	0.155	0.29	1.64	1.20	4.95	3.75	2.65
163408	4017-8061	2	1.8°	2	Bipolar	9.2	38	240	52	36	664	1.73	0.15	0.155	0.23	1.66	1.25	2.49	1.89	1.35
105881	SM42032/3	3	3.6°	2	Bipolar	12	25	480	31	80	600	1.73	0.11	0.197	0.43	1.66	1.31	5.99	5.59	4.95
164056	M82101-P1	1	7.5°	3	Unipolar	5	20	255	5	9	94	1.4	0.13	0.078	0.35	1.00	0.46	1.85	1.69	1.55
151861	C42M048A04	4	7.5°	4	Unipolar	5	9	550	10	90	750	1.94	0.13	0.117	0.40	1.65	0.83	5.59	5.05	4.55
171601	PF35T48L4 <sup>4</sup>	1	3.6°	4	Unipolar	7	20	350	9	40	680	1.68	0.14	0.078	0.47	1.38	0.58	4.39	3.49	2.65
166705	PM42S-096	1	3.8°	4	Unipolar	12	84	140	16	60	450	1.95	0.13	0.117	0.40	1.66	1.64	3.95	2.95	2.15
105890	3M4200 <sup>3</sup>	3	3.6°	4	Unipolar	12	75	150	39	80	600	1.73	0.11	0.197	0.43	1.66	1.28	8.79	7.85	6.99
213321	35BY48-27	7	7.5°	4	Unipolar	12	15	800	68	90	460	1.96	0.13	0.078	0.25	1.38	8.30	14.95	13.49	12.29
173180	30BY102AH5	6	.09°	4	Unipolar	12	200	60	49.5	400	400	1.42	0.14	0.194	0.36	1.18	0.68	11.49	10.35	9.35
192794	PM425048 <sup>6</sup>	5	7.5°	4	Unipolar	24	45	500	17.5	39	570	1.97	0.09	0.117	0.33	1.66	0.54	4.95	3.75	2.65
210382	5620	1	7.5°	4	Unipolar	24	100	436	60	40	380	1.67	0.13	0.078	0.40	1.38	0.58	5.95	5.49	4.95
210391	STP42N196S	8	3.75°	4	Unipolar	24	110	436	60	60	600	1.95	0.13	0.118	0.42	1.65	0.54	6.95	6.25	5.59
1 400005/40	3400 5 1 1 5											4 47400		140.						


# **Motors**

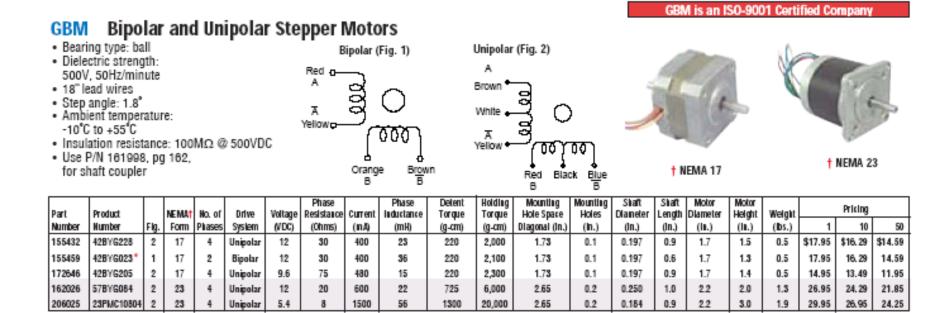




# **Dual Motor Gearbox Kit**

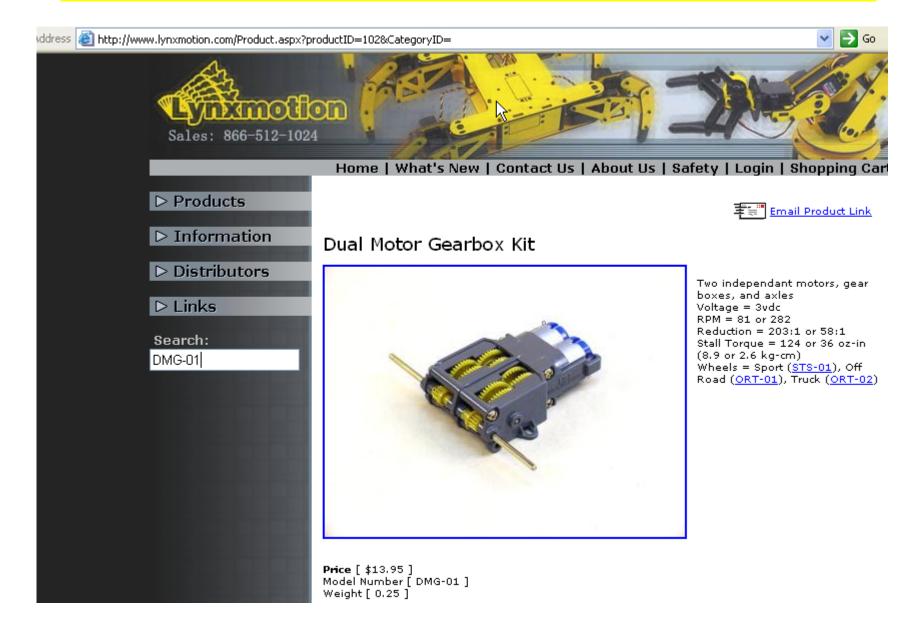

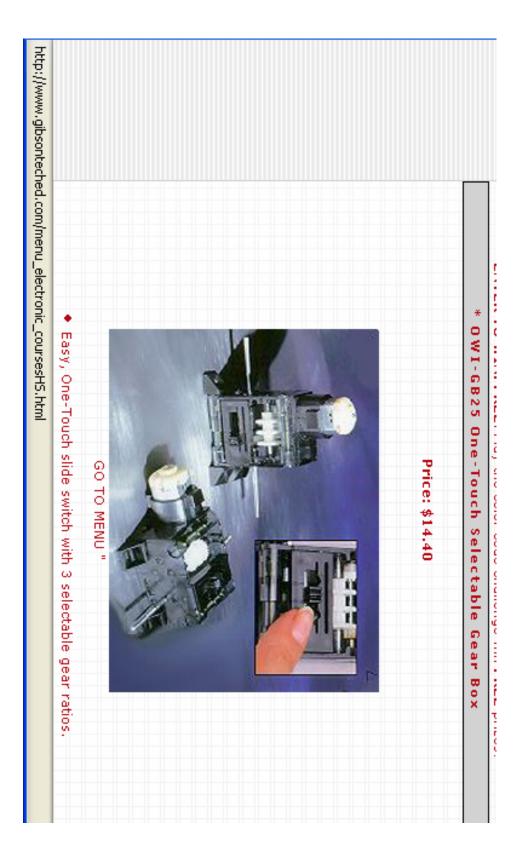

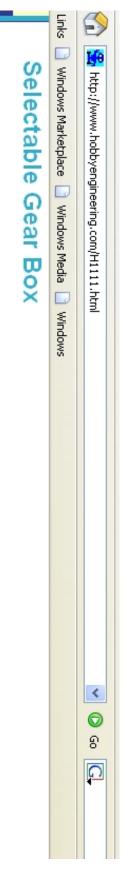



# Selectable Gear Box

A great science fair project item! If you need speed variations, then look no further. 807.93:1. Motor performance at maximum efficiency: Voltage: 1.5 - 3.0. three gear ratios are possible: 6.81:1, 45.97:1, 310.74:1, or 17.68:1, 119.52:1, brackets allow for flexibility in project applications. With one touch of a slide switch, Drive pulleys, cars, wheels, or fans with high torque or speed. Adjustable mounting

Mfr. # OWI-GB25



ltem: 1111

In Stock

Buy Now

\$14.95

In Stock

_									inks	Ð
						- CR		Other products in the Geared DC Motors (Kit) category	📔 Windows Marketplace 📔 Windows Media 📋	🏂 http://www.hobbyengineering.com/H1111.html
_	<u>2045</u>	<u>2013</u>	2238	<u>2146</u>	<u>2031</u>	2060	ltem	DC Motors (	Windows	tn]
	<u>High Speed Gear Box H.E.</u>	<u>High Power Gear Box H.E.</u>	Double 4-Speed Gearbox	<u>6-Speed Gear Box H.E.</u>	4-Speed Crank Axle Gearbox	3-Speed Crank Axle Gearhox	Title	Kit) category		

# **Dual Motor Gearbox Kit**



💌 💈 🎧 🔎 Search 🤺 Favorites 🚱 🔗 - 🚵 📼 🕤

Home | What's New | Contact Us |



Off-Road Tire

#### Products

Robotic Arms Bipeds Quadrapods Hexapods Polypods Carpet Rovers 4WD Rovers Sumo Robots Mechanical Hardware Electronics Batteries & Acces. Cables Motors, Wheels Planetary Motors Spur Gear Motors Misc. Motors Mounts / Hubs Wheels Servos, Access. Robot Books Misc Stuff SSC Software

#### Sport Tire - 2.2" x 1.0" (pair)



Price [ \$7.95 ] Model Number [ STS-01 ] Weight [ 0.19 ]  $\begin{array}{l} \mbox{Diameter} = 2.2" \\ \mbox{Width} = 1.0" \\ \mbox{Motor} = \mbox{Dual Motor Gearbox} \\ (\mbox{DMG-01}) \end{array}$ 

Image: Non-Abla and the set (2)Image: Non-Abla and the set (3)Image: Non-Abla and	Nks 📄 Windows Marketplace 📄 Windows Media 📄 Windows	iml Windows	
Truck Tire	2	<u>2033</u>	Off-Road Tire Set (2)
		<u>2027</u>	Truck Tire Set (4)

# Motor with Wheels

