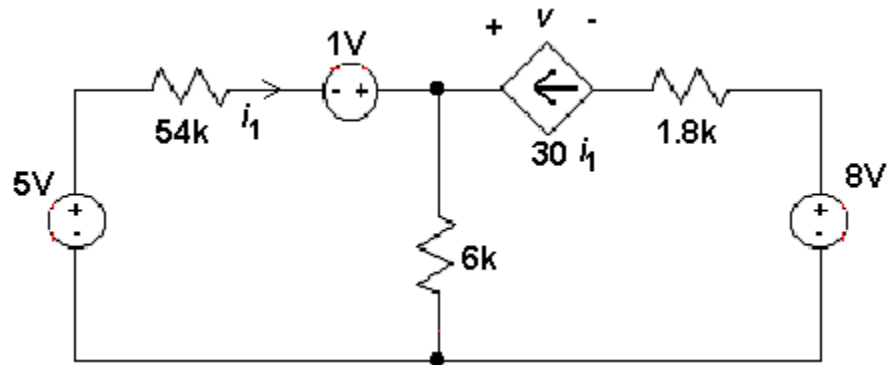


**Class Note 3: Example Problem with Dependent Source**

**Problem 1:**


Find  $v$  and  $i_1$  from the circuit given below



**SOLUTION:**

Strategy: KCL at the center node for current calculation, and KVL for the voltage.

(a) node and current marks and loops

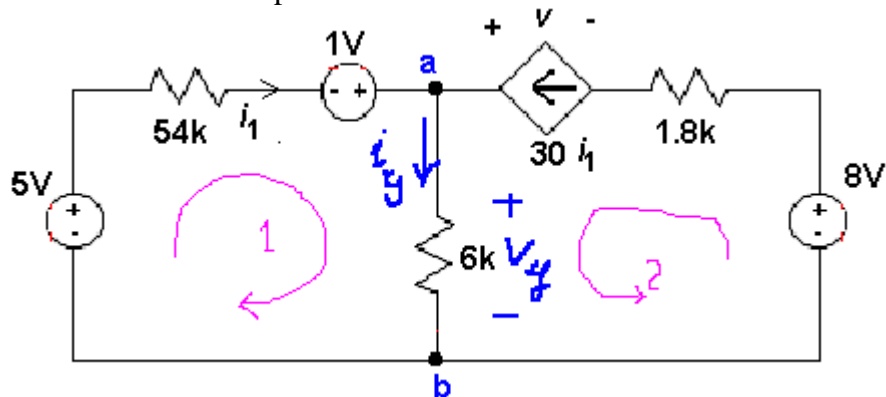


(b) Equations:

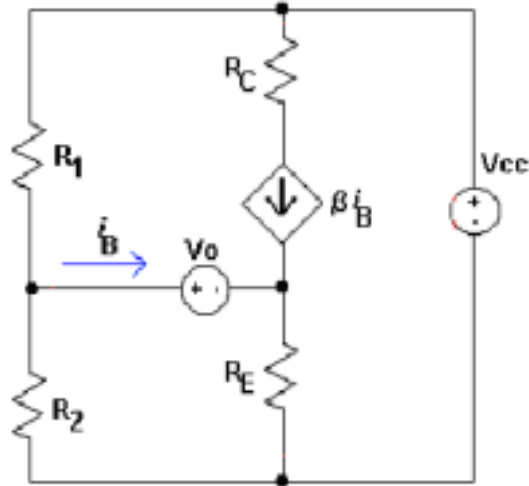**Problem 2:**

In a given circuit below, all the resistances and sources are known:  $V_{cc}=15[V]$ ,  $V_o=200[mV]$ ,  $R_1=20K$ ,  $R_2=80K$ ,  $R_E=100$ , and  $R_C=500$ .  $\beta=39$ .

Find equation for  $i_B$  and  $I_{cc}$ .



**SOLUTION**

**Procedure:**

1. The first thing we do is to mark nodes (a, b, c, and d) and flow indication of the currents ( $i_1$ ,  $i_2$ ,  $i_B$ ,  $i_E$ ,  $i_C$ , and  $i_{cc}$ )

