

## Class Note 23: Summary of Chapter 6

**A. Summary Table for Inductors and Capacitors**

	<b>Inductor</b>	<b>Capacitor</b>
<b>Voltage Equation</b>	$v(t) = L \frac{di(t)}{dt}$	$v(t) = \frac{1}{C} \int_{t_0}^t i(x) dx + v(t_0)$
<b>Current Equation</b>	$i(t) = \frac{1}{L} \int_{t_0}^t v(y) dy + i(t_0),$	$i(t) = C \frac{dv(t)}{dt}$
<b>Power Equation</b>	$p(t) = v(t) \cdot i(t)$ or $p(t) = L \cdot i(t) \cdot \frac{di(t)}{dt}$ or $p(t) = v(t) \cdot \left\{ \frac{1}{L} \int_0^t v(y) dy + i(0) \right\}$	$p(t) = v(t) \cdot i(t)$ or $p(t) = C \cdot v(t) \cdot \frac{dv(t)}{dt}$ or $p(t) = i(t) \cdot \left\{ \frac{1}{C} \int_0^t i(x) dx + v(0) \right\}$
<b>Energy Equation</b>	$w = \frac{1}{2} L \cdot i(t)^2$	$w = \frac{1}{2} C \cdot v(t)^2$
<b>Series Combination</b>	$L_{eq} = \sum_{k=1}^n L_k$	$\frac{1}{C_{eq}} = \sum_{k=1}^n \frac{1}{C_k}$
<b>Parallel Combination</b>	$\frac{1}{L_{eq}} = \sum_{k=1}^n \frac{1}{L_k}$	$C_{eq} = \sum_{k=1}^n C_k$
<b>Behavior at DC</b>	Short Circuit	Open Circuit
<b>Variable that cannot change abruptly</b>	Voltage, $v$	Current, $i$