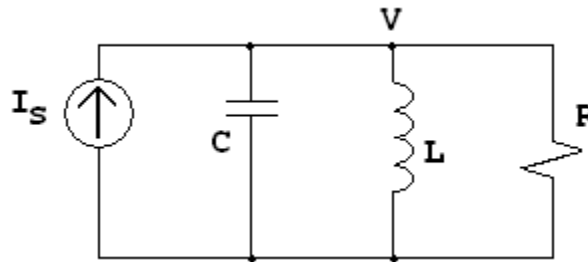


Class Note 25: Second-Order Circuits**A. Preface**

1. A second-order circuit is a circuit environment where an inductor and a capacitor are present simultaneously.
2. The second-order circuit analysis is, in this class, is limited to one loop (series RLC) or one non-reference node (parallel RLC) case.
3. PSpice analysis practice is encouraged.

A. Basic Circuit Equation of Second-Order Circuit

1. Let's first consider a parallel RLC circuit powered by a DC current source.




2. Let's assume that there is no energy initially stored in the capacitor and inductor.
3. The node voltage equation is:

$$-I_s + \frac{v}{R} + \frac{1}{L} \int v dx + C \frac{dv}{dt} = 0 \rightarrow \frac{v}{R} + \frac{1}{L} \int v dx + C \frac{dv}{dt} = I_s$$

4. By derivation with respect to time t , we have:

$$C \frac{d^2v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{v}{L} = 0 \quad \text{or} \quad \frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0 \text{-----(1)}$$

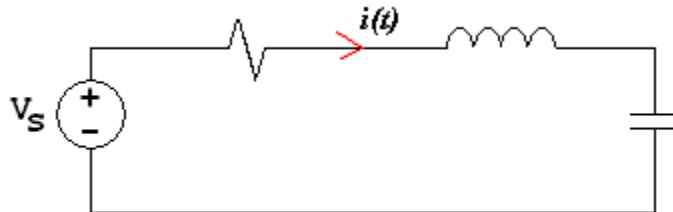5. Let's now consider a series RLC circuit powered by a DC voltage source.



6. Again, let's assume that there is no energy initially stored in the capacitor and inductor.
7. The loop KVL equation for the current is:

$$-V_s + Ri + \frac{1}{C} \int i(x) dx + L \frac{di}{dt} = 0 \rightarrow Ri + \frac{1}{C} \int i(x) dx + L \frac{di}{dt} = V_s$$

8. By derivation with respect to time t , we have:

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0 \rightarrow \frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \text{-----(2)}$$

9. We can see that the equation for the node voltage in the parallel RLC [equation (1) above] and the equation for the loop current in the series RLC [equation (2) above] are identical: a second-order differential equation with constant coefficients.

B. Solution of a Second-Order differential Equation (part 1: solution for forced function)

- Let's change equations (1) and (2) to a more general second-order differential equation form:

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2x(t) = K \text{ -----(3)}$$

- As we did in the first-order analysis, the solution of the equation (3) is:

$$x(t) = x_p(t) + x_c(t)$$

where, $x(t) = x_p(t)$ is a solution to $\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2x(t) = K$ -----(3a)

and $x(t) = x_c(t)$ is a solution to $\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2x(t) = 0$ -----(4)

- Let's observe equation (3a) for a while. Since the right hand side is a constant K, therefore $x_p(t)$ must be a constant (at left hand side). Let say $x_p(t)=C$ (C is a constant), then the left hand side is: a_2C . Therefore, $x_p(t) = C = \frac{K}{a_2}$.

- The, the complete solution of equation (3) is of the form:

$$x(t) = x_p(t) + x_c(t) = \frac{K}{a_2} + x_c(t)$$

- The solution of the homogeneous equation for $x_c(t)$ [eq. (4)] starts in the next section.

C. Solution of a Second-Order differential Equation (part 2: solution for homogeneous eq.)

- For simplicity (you will see why soon), let's rewrite the equation (4), by simple substitutions for $a_1 = 2\alpha$ and $a_2 = w_o^2$, in the form of:

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + w_o^2x(t) = 0 \text{ -----(5)}$$

*Note: For this revised equation form, $x_p(t) = \frac{K}{w_o^2}$ since $a_2 = w_o^2$.

- We assume a solution that: $x_c(t) = Ae^{st}$
- The substitution of the assumed solution into equation (5) yields

$$s^2 Ae^{st} + 2\alpha s Ae^{st} + w_o^2 Ae^{st} = 0$$

- Simplification of the above equation yields to: $(s^2 + 2\alpha s + w_o^2)Ae^{st} = 0$

Since $x_c(t) = Ae^{st}$ cannot be zero, $s^2 + 2\alpha s + w_o^2 = 0$ -----(6)

- The equation (6) is called the characteristic equation, where

α is referred to *Neper Frequency*

w_o is referred to *Undamped Natural Frequency* (or *Resonant Frequency*)

and $\left(\frac{\alpha}{w_o}\right)$ is referred to *Exponential Damping Ratio*.

- If the characteristic equation is satisfied, then, the assumed solution $x(t) = Ae^{st}$ is correct.

- Employing the quadratic formula, the roots for the characteristic equation are:

$$s = \frac{-2\alpha \pm 2\sqrt{\alpha^2 - w_o^2}}{2} = -\alpha \pm \sqrt{\alpha^2 - w_o^2}$$

- Therefore, the two roots are:

$$s_1 = -\alpha + \sqrt{\alpha^2 - w_o^2} \quad \text{and} \quad s_2 = -\alpha - \sqrt{\alpha^2 - w_o^2}$$

9. This means that we have two solutions of the homogeneous equation:

$$x_1(t) = A_1 e^{s_1 t} \quad \text{and} \quad x_2(t) = A_2 e^{s_2 t}$$

10. Note that the sum of two solutions is also a solution. Therefore, in general the solution of the homogeneous equation is of the form:

$$x_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \text{ -----(7)}$$

11. Finally, the solution for the original second-order equation of

$$\frac{d^2 x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + w_o^2 x(t) = K$$

is:

$$x(t) = \frac{K}{w_o^2} + x_c(t) = \frac{K}{w_o^2} + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{with, } s_1 = -\alpha + \sqrt{\alpha^2 - w_o^2} \quad \text{and} \quad s_2 = -\alpha - \sqrt{\alpha^2 - w_o^2}.$$

12. From the solution, we can easily see the final value: $x(\infty) = \frac{K}{w_o^2}$.

D. Examination of the solution of the homogeneous equation: Natural Frequency Analysis

1. Let's have a closer examination of the roots of the characteristics roots:

$$s_1 = -\alpha + \sqrt{\alpha^2 - w_o^2} \quad \text{and} \quad s_2 = -\alpha - \sqrt{\alpha^2 - w_o^2}$$


2. The roots s_1 and s_2 are called the natural frequencies because they determine the natural (unforced) response of the network.

3. We see that the roots are dependent upon the value of $(\alpha^2 - w_o^2)$.

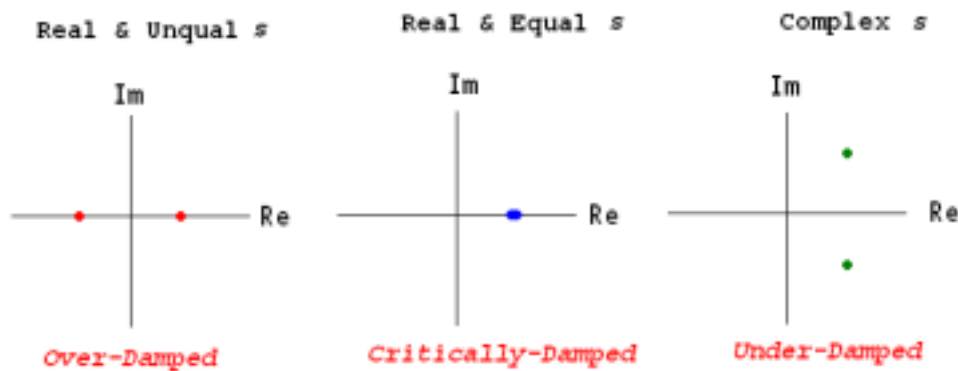4. If $\alpha^2 = w_o^2$: the roots are **real and equal** --> "Critically Damped"

If $\alpha^2 > w_o^2$: the roots are **real and unequal** --> "Overdamped"

If $\alpha^2 < w_o^2$: the roots are **complex numbers** --> "Underdamped"



5. “Critically Damped” case: (real and equal s)

(a) Condition: $\alpha^2 = \omega_o^2 \Rightarrow s_1 = s_2 = -\alpha$

(b) Solution Form: $x(t) = x(\infty) + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

[Note: $x(t) = x(\infty) + A_1 e^{-\alpha t} + A_2 e^{-\alpha t} = (A_1 + A_2) e^{-\alpha t} = A_3 e^{-\alpha t}$. This simple form,

however, in general does not satisfy the two initial conditions, i.e., $x(0)$ and $\left. \frac{dx(t)}{dt} \right|_{t=0}$

with the single constant A_3 . After applying an approach for repeated roots, the solution for critically damped case is of the form: $x(t) = x(\infty) + A_3 e^{-\alpha t} (A_1 + A_2 t)$]

(c) Constraints (equations to find the two coefficients, D_1 , and D_2):

i) $x(0) = x(\infty) + D_2$

ii) $\left. \frac{dx(t)}{dt} \right|_{t=0} = D_1 - \alpha D_2$

6. “Overdamped” case: (real and unequal s)

(a) Condition: $\alpha^2 > \omega_o^2$

(b) Solution: $x(t) = x(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$

(c) Constraints (or equations to find two coefficients A_1 and A_2)

i) $x(0) = x(\infty) + A_1 + A_2$

ii) $\left. \frac{dx(t)}{dt} \right|_{t=0} = s_1 A_1 + s_2 A_2$

7. “Underdamped” case: (complex s)

(a) Condition: $\alpha^2 < \omega_o^2$. Also define $\omega_d = \sqrt{\omega_o^2 - \alpha^2}$

The roots are rewritten as:

$$s_1 = -\alpha + j\sqrt{\omega_o^2 - \alpha^2} = -\alpha + j\omega_d \quad \text{and} \quad s_2 = -\alpha - j\sqrt{\omega_o^2 - \alpha^2} = -\alpha - j\omega_d$$

Then, the solution can be rewritten as:

$$x(t) = x(\infty) + A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$

$$= x(\infty) + e^{-\alpha t} [A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}]$$

$$= x(\infty) + e^{-\alpha t} [A_1 \{\cos \omega_d t + j \sin \omega_d t\} + A_2 \{\cos \omega_d t - j \sin \omega_d t\}]$$

$$= x(\infty) + e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t]$$

$$= x(\infty) + e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

(b) The solution form: $x(t) = x(\infty) + e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$



(c) Constraints (Coefficient equations)

i) $x(0) = x(\infty) + B_1$

ii) $\left. \frac{dx(t)}{dt} \right|_{t=0} = -\alpha B_1 + \omega_d B_2$


Second-Order Equation Summary Table

Second-Order Differential Equation		$\frac{d^2x}{dt^2} + 2\alpha \frac{dx}{dt} + \omega_0^2 x = K$		
Final Value		$x(\infty) = \frac{K}{\omega_0^2}$		
Characteristics Roots		$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ and $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$		
S o l u t i o n s	Damping Types	Overdamped case	Underdamped case	Critically Damped case
	Condition	$\alpha^2 > \omega_0^2$	$\alpha^2 < \omega_0^2$	$\alpha^2 = \omega_0^2$
	Solution Form $x(t) =$	$x(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$x(\infty) + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$	$x(\infty) + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$
	Coefficient Determination Relationship	$x(0) = x(\infty) + A_1 + A_2$ $\frac{dx(t)}{dt} \Big _{t=0} = s_1 A_1 + s_2 A_2$	$x(0) = x(\infty) + B_1$ $\frac{dx(t)}{dt} \Big _{t=0} = -\alpha B_1 + \omega_d B_2$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$x(0) = x(\infty) + D_2$ $\frac{dx(t)}{dt} \Big _{t=0} = D_1 - \alpha D_2$

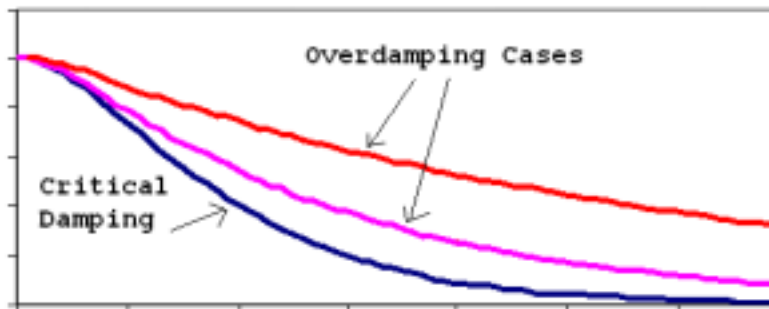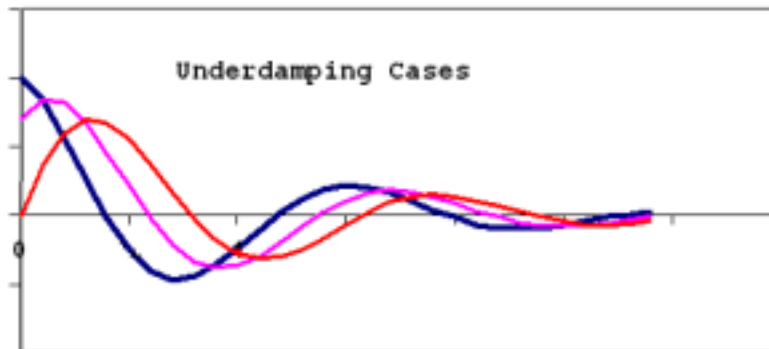

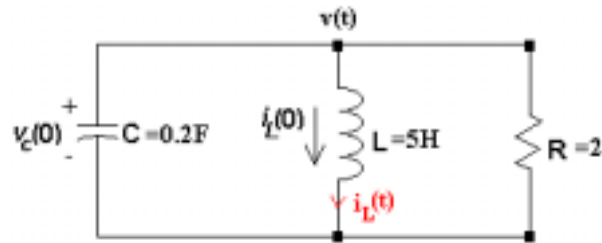E. Parallel RLC Natural Response Example


Consider the parallel RLC circuit shown below. Let's assume that the initial conditions on the storage elements are: $i_L(0) = -1$ [A] and $v_C(0) = 4$ [V]. Find the node voltage $v(t)$ and the current through the inductor $i_L(t)$.



SOLUTION:

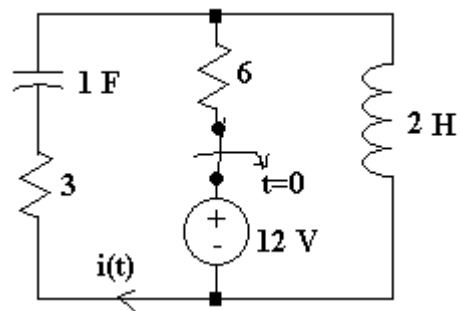F. Series RLC Natural Response Example


The switch in the circuit has been closed for a long time. At $t=0$, the switch opens. Find $i(t)$.



SOLUTION:

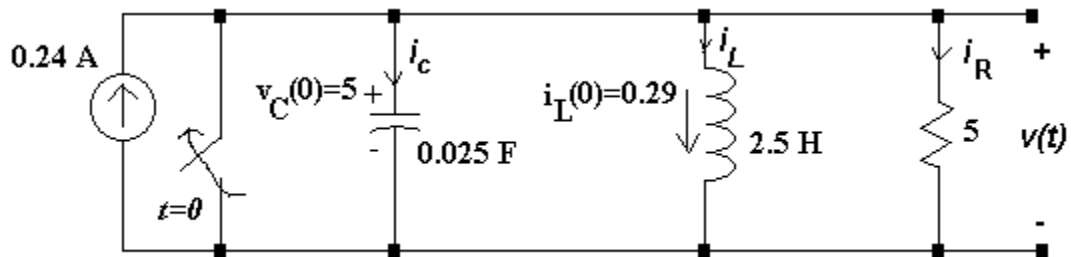G. Step Response of Parallel RLC Example


Energy is stored in the circuit before the DC current source is applied, with $i_L(0) = 0.29$ [A] and $v_C(0) = 5$ [V]. Find $i_L(t)$.



SOLUTION

H. Step Response of Series RLC Example


Find $v_C(t)$.

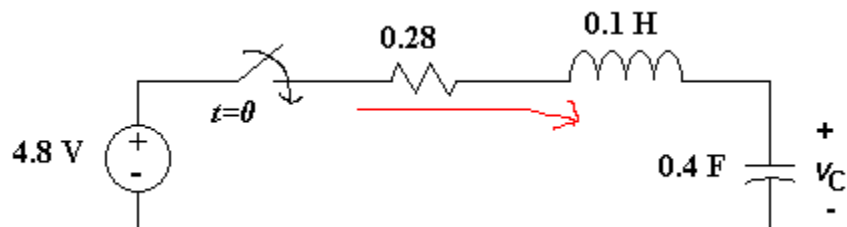


SOLUTION:

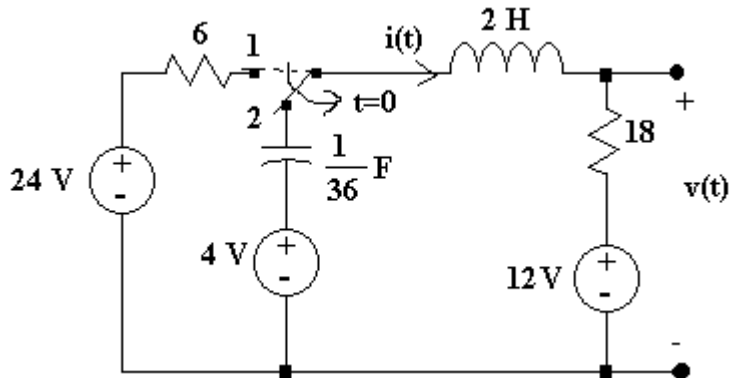I. RLC Response Extra Problems

I.1. The switch in the circuit has been in position 1 for a long time. At $t=0$, it moves from position 1 to position 2. Compute $i(t)$ for $t>0$ and use this current to determine the voltage $v(t)$.



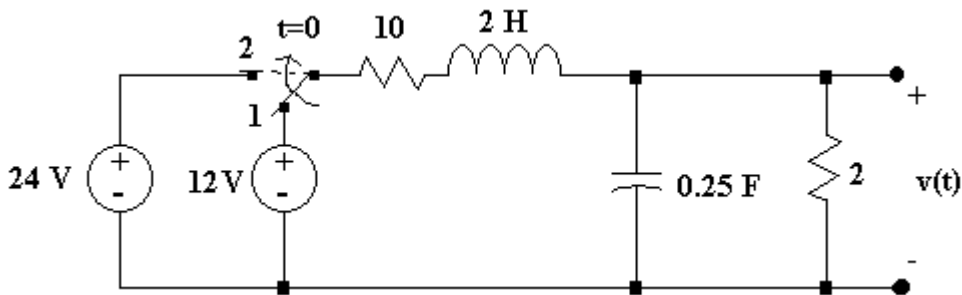I.2. The switch in the circuit has been in position 1 for a long time. At $t=0$, it moves from position 1 to position 2. Compute $v(t)$ for $t>0$.



I.3. Find $v(t)$ and $i(t)$

