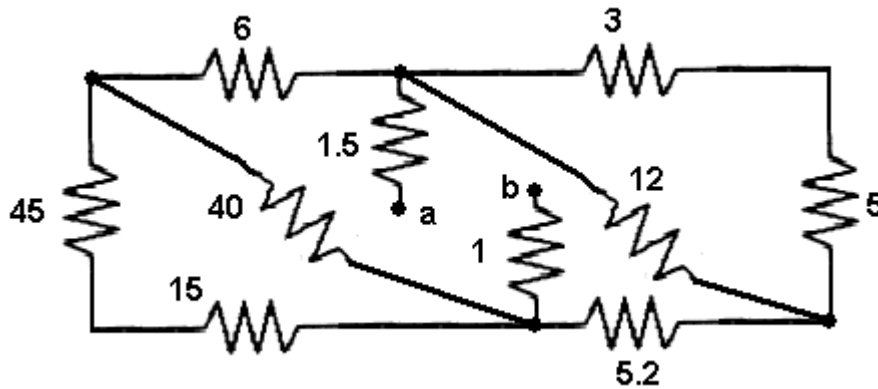



HOMEWORK #1 – Part 2 of 2

NOTE: Show your works


1. Find the equivalent resistance  $R_{ab}$ .



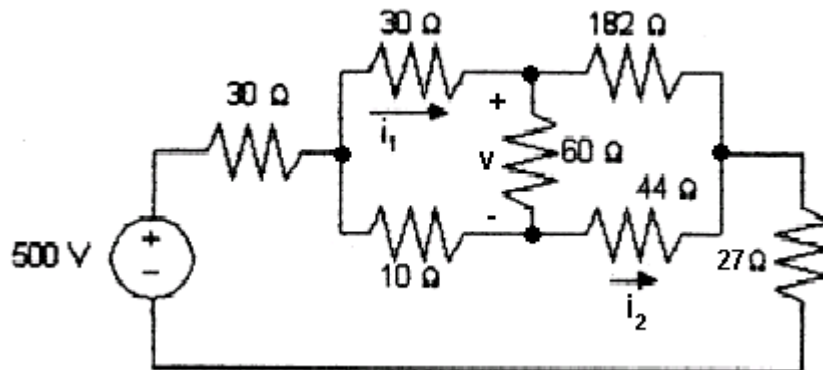
2. For the circuit shown below, find  $i_1$ ,  $i_2$ , and  $v$ .



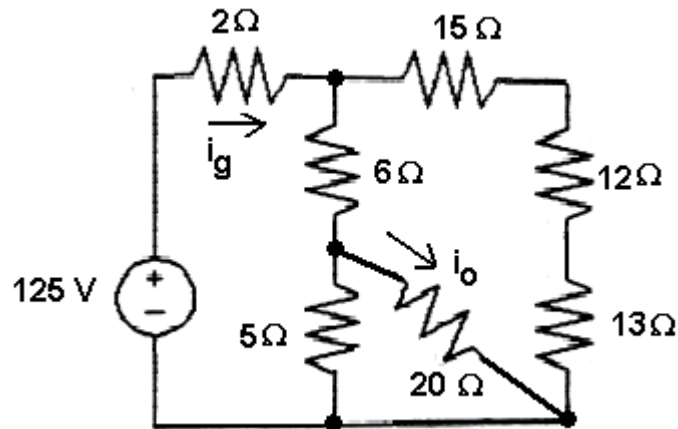3. Find  $i_o$  and  $i_g$  in the circuit below.




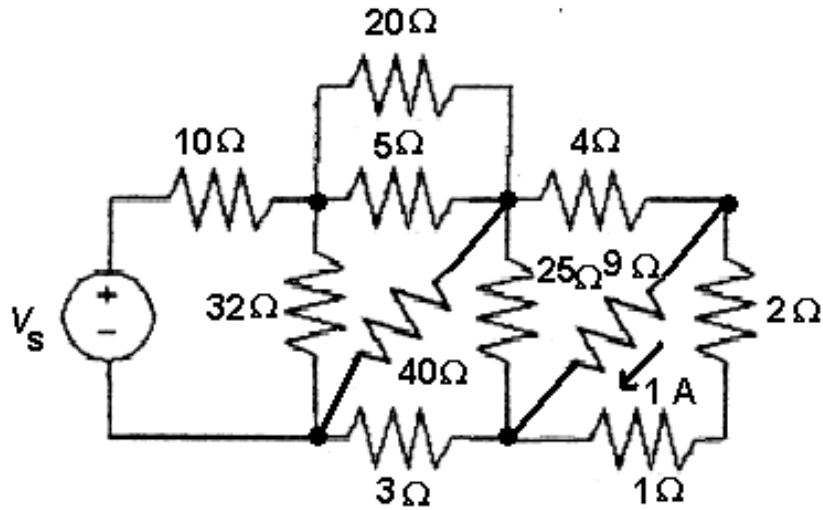4. The current through the  $9\ \Omega$  resistor in the circuit is  $1\ \text{A}$ . Find  $V_s$ .




5. A shunt resistor and a  $50\text{mV}$ ,  $1\ \text{mA}$  d'Arsonval movement are used to build a (full scale)  $10\ \text{A}$  Ammeter. If a new resistance of  $0.015\ \Omega$  is placed across the terminals of the Ammeter, what is the new full scale of the Ammeter?

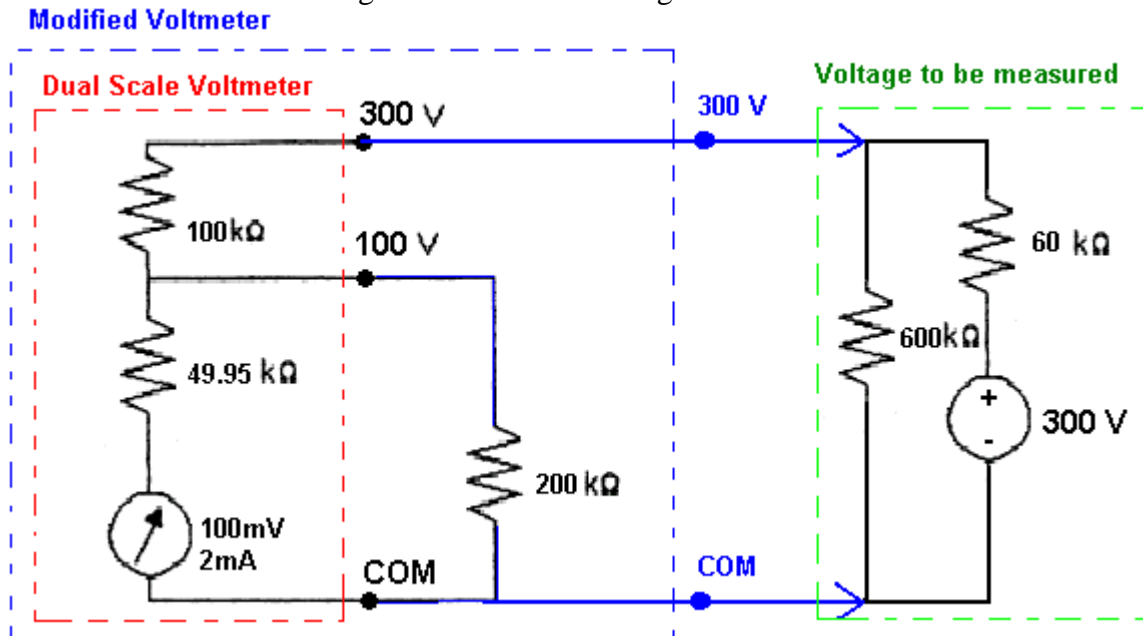6. A  $200\text{k}\Omega$  is connected from the  $100\text{V}$  terminal to the COM terminal of a dual-scale voltmeter as shown below. This modified voltmeter is then used to measure the voltage across the  $600\ \text{k}\Omega$  resistor in the circuit of below right. What is the reading of the  $300\text{V}$  scale of the meter?



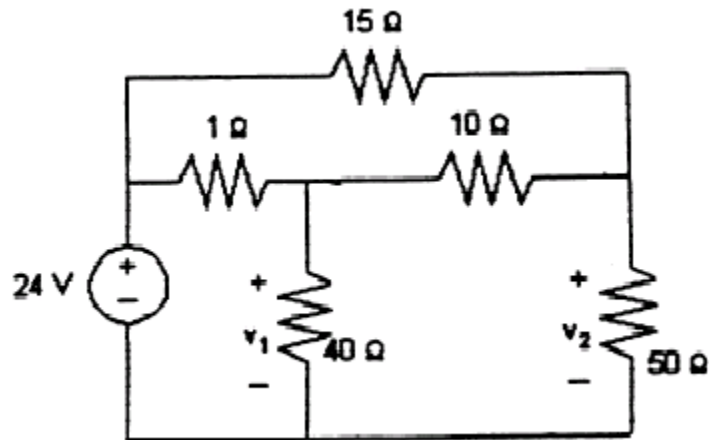7. Use Delta-to-Y transformation to find the voltages  $v_1$  and  $v_2$  in the circuit below.



8. The no-load voltage of the voltage-divider circuit is 150 [V]. The smallest load resistor ( $R_L$ ) that is ever connected to the divider is 60 k $\Omega$ . When the load resistor is connected to the divider, the voltage of the load  $V_o$  should not drop below 100 [V]. (a) Specify the numerical values of  $R_1$  and  $R_2$ . (b) Assuming the power ratings of commercially available resistors are 1/16, 1/8, 1/4, 1, and 2 W, what power rating would you specify to the resistors  $R_1$  and  $R_2$ ?

