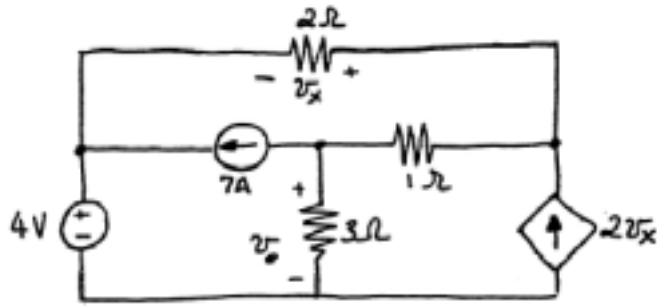


HOMEWORK #2 – Part 1 of 2


Solve the following problems using **any** or **combination** of the analysis techniques you learned:
 Nodal Analysis (i.e., KCL), Mesh Analysis (i.e., KVL),
 Thevenin Equivalent Circuit and Maximum Power Transfer, and
 Source Transformation,

SHOW YOUR WORK


1. Find v_o in the circuit below.



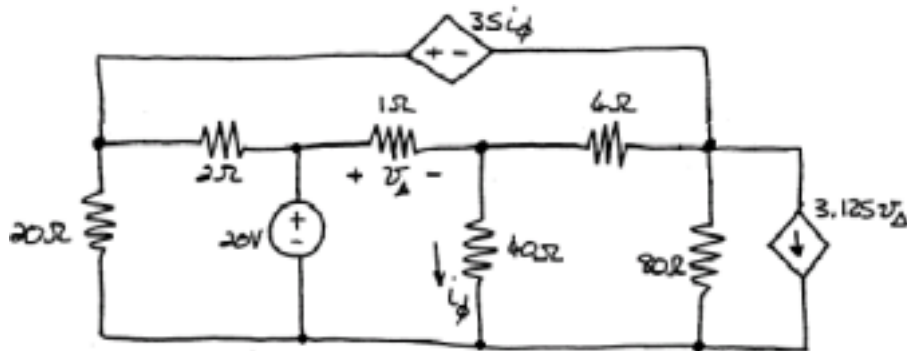
2. Calculate the power delivered by the 20 V source.




3. Find v_1 and v_2 .

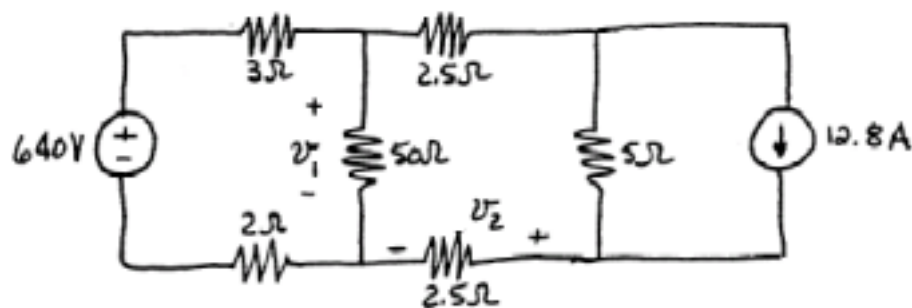

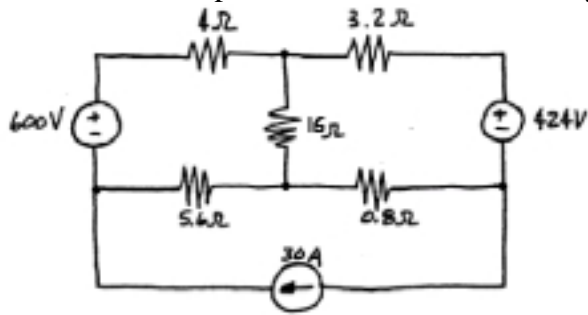
4. Calculate the power delivered/consumed by the 30 A source.



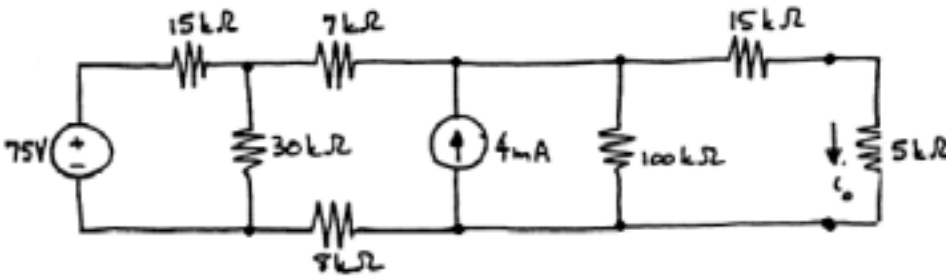5. Find the current through the 5 kΩ resistor in the circuit.



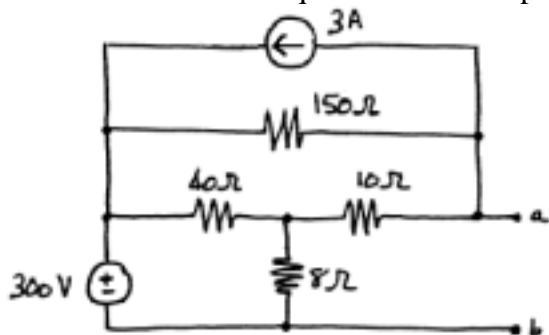6. Find the Thevenin equivalent with respect to the terminals *a* and *b* for the circuit below.



7. Find the value the resistor *R* that can deliver the maximum power to the resistor.

