
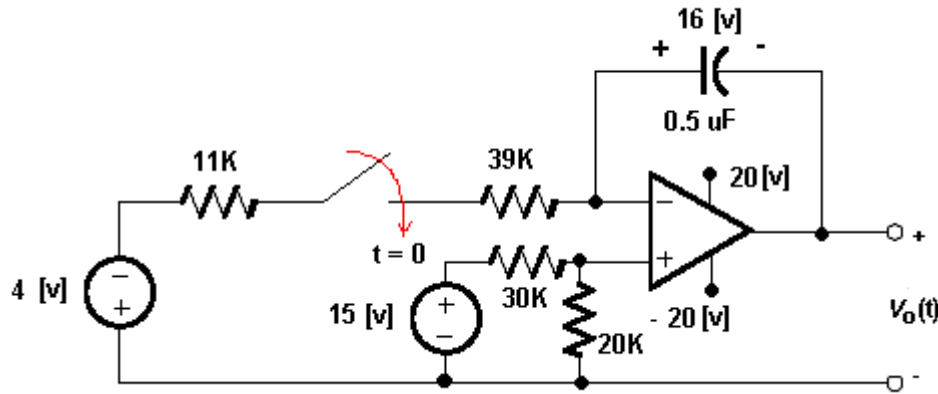


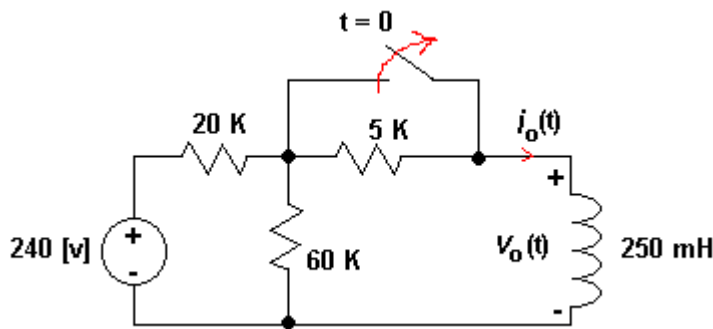
1. At the instant the switch is closed, the voltage on the capacitor is 16 [V]. The Op Amp in the circuit is ideal. How many seconds after the switch is closed will the output voltage v_o equal zero?




2. The switch in the circuit has been closed for a long time. The switch opens at $t=0$. Find the numerical expressions for $i_o(t)$ and $v_o(t)$ for $t \geq 0$.



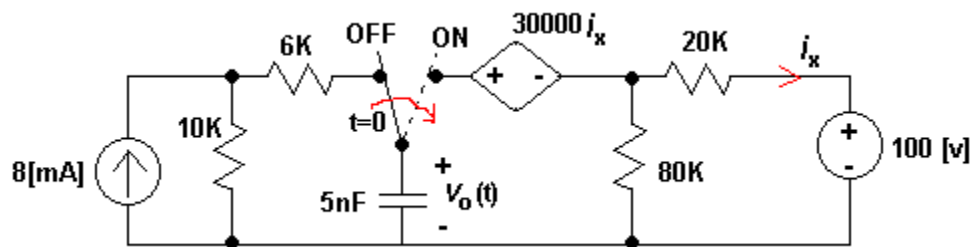3. The switch in the circuit has been in the OFF position for a long time. At $t=0$, the switch moves instantaneously to the ON position. Find $v_o(t)$ for $t \geq 0$.



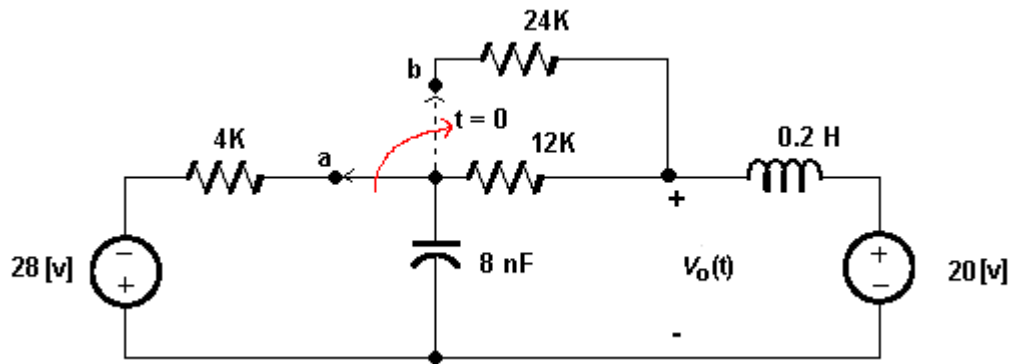4. The switch in the circuit has been in position *a* for a long time. At $t = 0$, the switch moves instantaneously to position *b*. Find $v_o(t)$ for $t \geq 0$.



5. The switch in the circuit has been in the closed position for a long time, and at $t=0$, it is opened instantaneously. Find $i(t)$ for $t > 0$. (A final exam problem of Spring 2004)

