
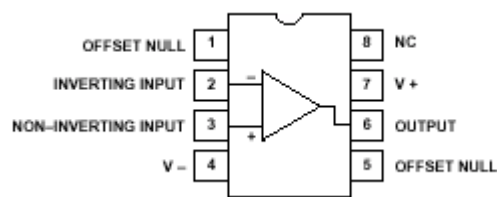



Note09: Active Filters ---Part 1

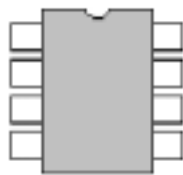1. Active circuits employing OP Amps, resistors, and capacitors
2. Amplification gain
3. No load effect (Remember in passive filters with load at the filter terminals?)
4. Topics
 - (i) Simple LPF
 - (ii) Simple HPF
 - (iii) Prototype Filter and Scaling Concept
 - (iv) Higher Order Filter
 - * Cascading Identical Filters
 - * Butterworth Filters



0. General First-Order Active Filter

Circuit Configuration:

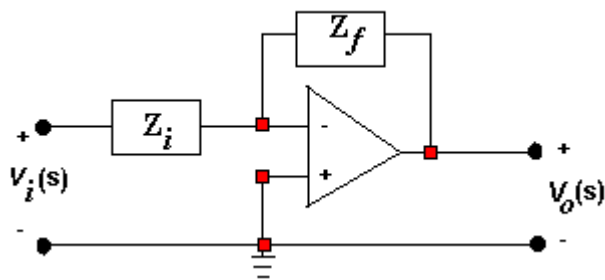


Node voltage equation at the (-) node: Remember that there is no current to the Op-Amp.

$$\frac{0 - V_i}{Z_i} = \frac{0 - V_o}{Z_f} \implies V_o = -V_i \cdot \frac{Z_f}{Z_i}$$

$$\text{s-domain Transfer Function: } H(s) = \frac{V_o(s)}{V_i(s)} = \frac{-V_i(s) \frac{Z_f}{Z_i}}{V_i(s)} = -\frac{Z_f}{Z_i}$$

1. First-Order Low Pass Filter

Circuit Configuration:

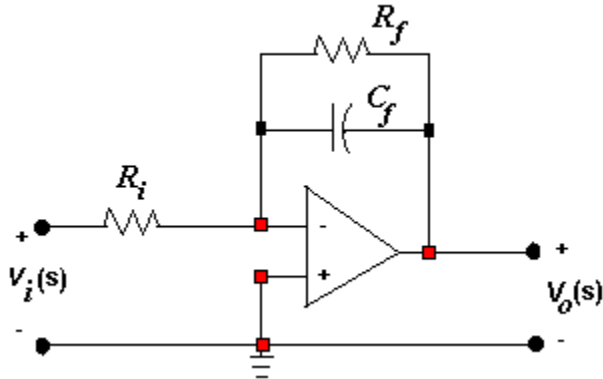

s-domain Transfer Function:

$$Z_i = R_i \quad \text{and} \quad Z_f = R_f \parallel C_f \Rightarrow \frac{\frac{R_f}{sC_f}}{R_f + \frac{1}{sC_f}}$$

Therefore,

$$H(s) = -\frac{Z_f}{Z_i} = -\frac{\frac{\frac{R_f}{sC_f}}{R_f + \frac{1}{sC_f}}}{R_i} = -\frac{R_f / sC_f}{R_i(R_f + 1/sC_f)} = -\frac{R_f}{R_i(sR_fC_f + 1)} = -\frac{R_f}{R_i} \cdot \frac{1}{(1 + R_fC_f s)}$$

Steady-State Transfer Function: $H(j\omega) = -\frac{R_f}{R_i} \cdot \frac{1}{1 + jR_fC_f\omega}$

Pass Band Gain: $A(0) = -\frac{R_f}{R_i}$

Relative dB Amplitude: $A_{dB}(\omega) = 20\log\left(\frac{R_f}{R_i}\right) - 10\log\left[1 + \left(\frac{\omega}{1/R_fC_f}\right)^2\right]$

$$= 20\log\left(\frac{R_f}{R_i}\right) - 10\log\left[1 + \left(\frac{\omega}{\omega_c}\right)^2\right]$$

where $\omega_c =$ cutoff frequency in [rad/sec]


Bode-Plot:

What is the cut-off frequency? Is it $\frac{\omega_c}{1/R_fC_f} = 1.0$?

What is the cut-off frequency and passband gain with $R_i=400$, $R_f=1600$, $C_f=0.2\mu\text{F}$?

Example Problem: Using the circuit below, design a low-pass filter with a pass-band gain of 15 dB and a cut-off frequency of 10 kHz. Assume a 5 nF capacitor is available.

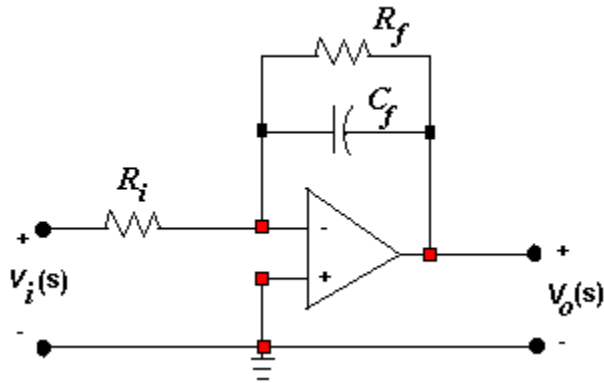- (a) Specify the values of the resistors.
- (b) Draw a Bode Plot



Solution

Given Information:

- (1) Pass band gain (i.e. $G_{dB}(0)=15\text{dB}$)
- (2) $f_c=10000$ (i.e., $\omega_c=2\pi(10000)$ rad/s)
- (3) $C=5\text{nF}$

What's the question, then? --> **Find R_1 and R_2 .**

SOLUTION:

Bode Plot:

2. Scaling

1. Drawing a transfer function would be much easier with values of 1Ω , $1F$, and $1H$ than with realistic values of elements.

2. From the LPF, the transfer function of $H(j\omega) = -\frac{R_f}{R_i} \cdot \frac{1}{1 + jR_f C_f \omega}$, can then become

$H(j\omega) = -\frac{1}{1 + \omega}$. And the cutoff frequency is $\frac{1}{R_f C_f} = \frac{1}{1 \cdot 1} = 1$ [rad/sec]. This filter with all

convenient values with $\omega_c = 1$ [rad/sec] is called a **prototype filter**.

3. After making computation for a transfer function using the convenient values of R , L , and C , we can transform the convenient values to realistic values using the process known as **scaling**.

4. Two types of scaling:

(a) magnitude scaling (k_m : scale factor for magnitude)

R, L, C : convenient values

R', L', C' : actual (realistic values)

Then, $R' = k_m R$, $L' = k_m L$, and $C' = C/k_m$

(b) frequency scaling (k_f : scale factor for frequency)

Then, $k_f = \omega_c' / \omega_c$, $R' = R$, $L' = L/k_f$, and $C' = C/k_f$

(since $\omega L = \omega' L'$ and $\frac{1}{\omega C} = \frac{1}{\omega' C'}$)

(c) Combination of two scale factors:


$R' = k_m R$, $L' = \frac{k_m}{k_f} L$, and $C' = \frac{1}{k_m k_f} C$

5. **Scaling Example:** use the prototype active LPF, along with magnitude and frequency scaling, to compute the resistor values with a gain of 5, a cutoff frequency of 1000 Hz, and a feedback capacitor of 0.01 μF .

Solution:

3. First Order High Pass Filter

Circuit Configuration:

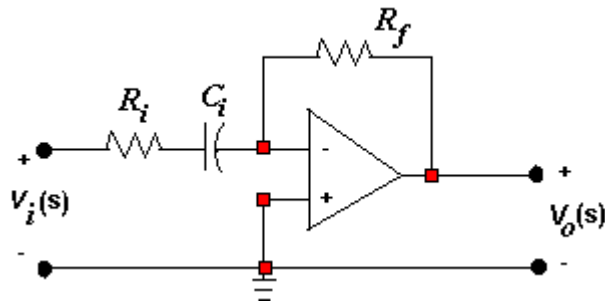

$$Z_i = R_i + 1/sC_i \quad \text{and} \quad Z_f = R_f$$

s-domain Transfer Function:

$$H(s) = -\frac{Z_f}{Z_i} = -\frac{R_f}{R_i + 1/sC_i} = -\frac{R_f}{R_i} \cdot \frac{1}{(1 + 1/R_iC_i s)} = -\frac{R_f}{R_i} \cdot \frac{R_iC_i s}{(1 + R_iC_i s)} = -\frac{R_f}{R_i} \cdot \frac{\frac{s}{1/R_iC_i}}{[1 + \frac{s}{1/R_iC_i}]}$$

$$\text{Steady-State: } H(j\omega) = -\frac{R_f}{R_i} \cdot \frac{j\frac{\omega}{1/R_iC_i}}{1 + j\frac{\omega}{1/R_iC_i}} = -\frac{R_f}{R_i} \cdot \frac{j\frac{\omega}{\omega_c}}{1 + j\frac{\omega}{\omega_c}}, \quad \text{with } \omega_c = \frac{1}{R_iC_i}$$

$$\text{Pass band Gain: } A(\infty) = -\frac{R_f}{R_i}$$

$$\text{Relative dB Amplitude: } A_{dB}(\omega) = 20\log\left(\frac{R_f}{R_i}\right) + 20\log\left[\left(\frac{\omega}{1/R_iC_i}\right)\right] - 10\log\left[1 + \left(\frac{\omega}{1/R_iC_i}\right)^2\right]$$

What is the cut-off frequency? Is it $\frac{\omega_c}{1/R_iC_i} = 1.0$?

What is the cut-off frequency and DC gain with $R_i=800$, $R_f=4000$, and $C_i=0.1\mu\text{F}$?