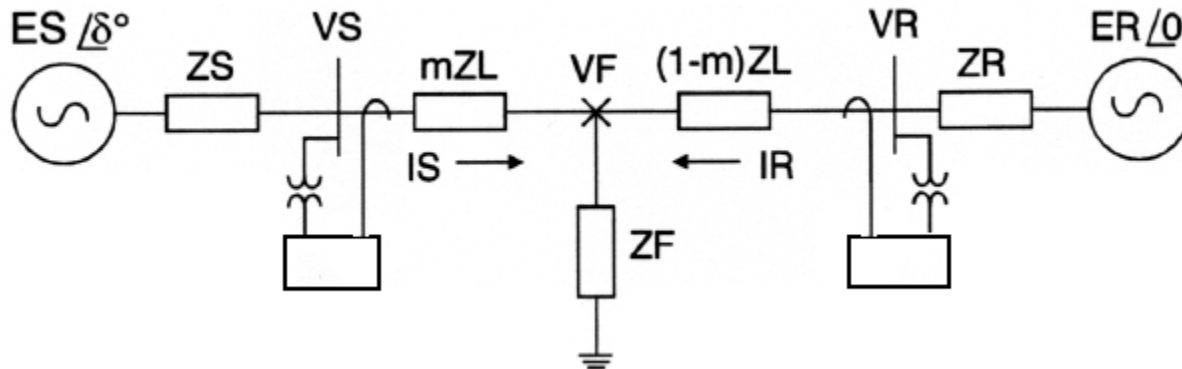



Exam June 2010

Heidi Krohns
 Student number: nnnnnn
 heidi.krohns@tut.fi

SIMPLE ONE LINE DIAGRAM



FAULT IMPEDANCE

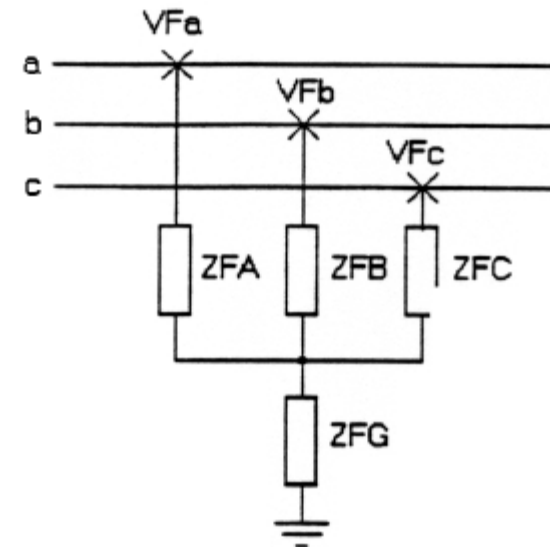

INPUT DATA

$\delta := 1.1$ **Voltage Phase Angle**
 $es := 70 \cdot e^{j \cdot \delta \cdot \text{deg}}$ **Source S Voltage** $es = 69.987 + 1.344i$
 $er := 70$ **Source R Voltage**
 $er := 0$
 $Z1S := 4.104 + j \cdot 11.276$ **Source S Positive Sequence Impedance**
 $Z0S := 25.357 + j \cdot 54.378$ **Source S Zero Sequence Impedance**
 $Z1R := 0.518 + j \cdot 1.932$ **Source R Positive Sequence Impedance**
 $Z0R := 3 \cdot Z1R$ **Source S Zero Sequence Impedance**
 $Z1L := 1.035 + j \cdot 3.864$ **Positive Sequence Line Impedance**

Fault Location

$$m := .5$$

Fault Impedances (for AG fault case) INF := 10¹⁰

$$ZFA := 0 + j \cdot 0 \quad ZFB := INF + j \cdot 0 \quad ZFC := INF + j \cdot 0$$

Fault Resistance

$$ZFG := 0.85 + j \cdot 0 \quad ZFG := 0.1 \quad ZFG := 0.4 + j \cdot 0 \quad ZFG := 1.57 + j \cdot 0 \quad ZFG := 10 + j \cdot 0$$

CONSTANTS

$$\text{rad} := 1 \quad \text{deg} := \frac{\pi}{180} \cdot \text{rad}$$

Operator

$$a := e^{j \cdot 120 \cdot \text{deg}} \quad a = -0.5 + 0.866i$$

$$\text{BAL} := \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \text{one} := \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{pmatrix} \quad \text{zero} := \begin{pmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{pmatrix}$$

Three phase voltages at S and R

$$ES := es \cdot \text{BAL}$$

$$ER := er \cdot \text{BAL}$$

$$ES = \begin{pmatrix} 69.987 + 1.344i \\ -33.83 - 61.283i \\ -36.157 + 59.939i \end{pmatrix}$$

$$ER = \begin{pmatrix} 70 \\ -35 - 60.622i \\ -35 + 60.622i \end{pmatrix}$$

CIRCUIT EQUATION

In 3-phase matrix form, the equation looks like this:

$$\begin{bmatrix} \mathbf{ES} \\ \mathbf{ER} \\ \mathbf{null} \end{bmatrix} = \begin{bmatrix} \mathbf{ZSS} & \mathbf{zero} & \mathbf{one} \\ \mathbf{zero} & \mathbf{ZRR} & \mathbf{one} \\ \mathbf{-ZF} & \mathbf{-ZF} & \mathbf{one} \end{bmatrix} \begin{bmatrix} \mathbf{IS} \\ \mathbf{IR} \\ \mathbf{VF} \end{bmatrix}$$

How do we form the source impedance ZS and ZR?

Let us consider the link between 3-phase circuit and symmetrical components

Conversion of positive sequence and zero sequence impedances to Self and Mutual impedances

$$z_s(z_0, z_1) := \frac{2 \cdot z_1 + z_0}{3} \quad z_m(z_0, z_1) := \frac{z_0 - z_1}{3}$$

Conversion Matrix Format

$$Z(z_0, z_1) := \begin{pmatrix} z_s(z_0, z_1) & z_m(z_0, z_1) & z_m(z_0, z_1) \\ z_m(z_0, z_1) & z_s(z_0, z_1) & z_m(z_0, z_1) \\ z_m(z_0, z_1) & z_m(z_0, z_1) & z_s(z_0, z_1) \end{pmatrix}$$

Now Conversion

$$Z_S := Z(Z_{0S}, Z_{1S}) \quad Z_L := Z(Z_{0L}, Z_{1L}) \quad Z_R := Z(Z_{0R}, Z_{1R})$$

$$Z_S = \begin{pmatrix} 11.188 + 25.643i & 7.084 + 14.367i & 7.084 + 14.367i \\ 7.084 + 14.367i & 11.188 + 25.643i & 7.084 + 14.367i \\ 7.084 + 14.367i & 7.084 + 14.367i & 11.188 + 25.643i \end{pmatrix}$$

Source and Line Impedances to the Fault

$$Z_{SS} := Z_S + m \cdot Z_L \quad Z_{SS} = \begin{pmatrix} 12.051 + 28.863i & 7.429 + 15.655i & 7.429 + 15.655i \\ 7.429 + 15.655i & 12.051 + 28.863i & 7.429 + 15.655i \\ 7.429 + 15.655i & 7.429 + 15.655i & 12.051 + 28.863i \end{pmatrix}$$

$$Z_{RR} := Z_R + (1 - m) \cdot Z_L \quad Z_{RR} = \begin{pmatrix} 1.726 + 6.44i & 0.69 + 2.576i & 0.69 + 2.576i \\ 0.69 + 2.576i & 1.726 + 6.44i & 0.69 + 2.576i \\ 0.69 + 2.576i & 0.69 + 2.576i & 1.726 + 6.44i \end{pmatrix}$$

Build System Part of the Impedance Matrix

$$\begin{bmatrix} \mathbf{ES} \\ \mathbf{ER} \\ \mathbf{null} \end{bmatrix} = \begin{bmatrix} \mathbf{ZSS} & \mathbf{zero} & \mathbf{one} \\ \mathbf{zero} & \mathbf{ZRR} & \mathbf{one} \\ -\mathbf{ZF} & -\mathbf{ZF} & \mathbf{one} \end{bmatrix} \begin{bmatrix} \mathbf{IS} \\ \mathbf{IR} \\ \mathbf{VF} \end{bmatrix}$$

$$\mathbf{ES} = \begin{bmatrix} \mathbf{ES}_a \\ \mathbf{ES}_b \\ \mathbf{ES}_c \end{bmatrix} \quad \mathbf{ER} = \begin{bmatrix} \mathbf{ER}_a \\ \mathbf{ER}_b \\ \mathbf{ER}_c \end{bmatrix} \quad \mathbf{VF} = \begin{bmatrix} \mathbf{VF}_a \\ \mathbf{VF}_b \\ \mathbf{VF}_c \end{bmatrix} \quad \mathbf{IS} = \begin{bmatrix} \mathbf{IS}_a \\ \mathbf{IS}_b \\ \mathbf{IS}_c \end{bmatrix} \quad \mathbf{IR} = \begin{bmatrix} \mathbf{IR}_a \\ \mathbf{IR}_b \\ \mathbf{IR}_c \end{bmatrix}$$

$$\mathbf{ZTOP} := \text{augment}(\text{augment}(\mathbf{ZSS}, \mathbf{zero}), \mathbf{one})$$

$$\mathbf{ZTOP} = \begin{pmatrix} 12.051 + 28.863i & 7.429 + 15.655i & 7.429 + 15.655i & 0 & 0 & 0 & 1 & 0 & 0 \\ 7.429 + 15.655i & 12.051 + 28.863i & 7.429 + 15.655i & 0 & 0 & 0 & 0 & 1 & 0 \\ 7.429 + 15.655i & 7.429 + 15.655i & 12.051 + 28.863i & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}$$

$$\mathbf{ZMID} := \text{augment}(\text{augment}(\mathbf{zero}, \mathbf{ZRR}), \mathbf{one})$$

$$\mathbf{ZMID} = \begin{pmatrix} 0 & 0 & 0 & 1.726 + 6.44i & 0.69 + 2.576i & 0.69 + 2.576i & 1 & 0 & 0 \\ 0 & 0 & 0 & 0.69 + 2.576i & 1.726 + 6.44i & 0.69 + 2.576i & 0 & 1 & 0 \\ 0 & 0 & 0 & 0.69 + 2.576i & 0.69 + 2.576i & 1.726 + 6.44i & 0 & 0 & 1 \end{pmatrix}$$

$$\mathbf{ZSYS} := \text{stack}(\mathbf{ZTOP}, \mathbf{ZMID})$$

$$\mathbf{ZSYS} = \begin{pmatrix} 12.051 + 28.863i & 7.429 + 15.655i & 7.429 + 15.655i & 0 & 0 & 0 & 1 & 0 & 0 \\ 7.429 + 15.655i & 12.051 + 28.863i & 7.429 + 15.655i & 0 & 0 & 0 & 0 & 1 & 0 \\ 7.429 + 15.655i & 7.429 + 15.655i & 12.051 + 28.863i & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1.726 + 6.44i & 0.69 + 2.576i & 0.69 + 2.576i & 1 & 0 & 0 \\ 0 & 0 & 0 & 0.69 + 2.576i & 1.726 + 6.44i & 0.69 + 2.576i & 0 & 1 & 0 \\ 0 & 0 & 0 & 0.69 + 2.576i & 0.69 + 2.576i & 1.726 + 6.44i & 0 & 0 & 1 \end{pmatrix}$$

Pre-fault conditions:

$$\mathbf{ZPRE} := \mathbf{ZS} + \mathbf{ZL} + \mathbf{ZR}$$

$$\mathbf{ZPRE} = \begin{pmatrix} 13.777 + 35.303i & 8.12 + 18.231i & 8.12 + 18.231i \\ 8.12 + 18.231i & 13.777 + 35.303i & 8.12 + 18.231i \\ 8.12 + 18.231i & 8.12 + 18.231i & 13.777 + 35.303i \end{pmatrix}$$

$$\mathbf{ISPRES} := \mathbf{ZPRE}^{-1} \cdot (\mathbf{ES} - \mathbf{ER})$$

$$\mathbf{ISPRES} = \begin{pmatrix} 0.071 + 0.024i \\ -0.014 - 0.073i \\ -0.056 + 0.049i \end{pmatrix}$$

$$\text{IRPRE} := \text{ZPRE}^{-1} \cdot (\text{ER} - \text{ES})$$

$$\text{IRPRE} = \begin{pmatrix} -0.071 - 0.024i \\ 0.014 + 0.073i \\ 0.056 - 0.049i \end{pmatrix}$$

Pre_fault voltage at S end

$$\text{VSP} := \text{ES} - \text{ZS} \cdot \text{IRPRE}$$

$$\text{VSP} = \begin{pmatrix} 69.97 + 0.447i \\ -34.597 - 60.819i \\ -35.372 + 60.372i \end{pmatrix}$$

$$\text{ES} = \begin{pmatrix} 69.987 + 1.344i \\ -33.83 - 61.283i \\ -36.157 + 59.939i \end{pmatrix}$$

$$\text{VRP} := \text{ZS} \cdot \text{IRPRE} - \text{ER}$$

$$\text{VRP} = \begin{pmatrix} -70.017 - 0.896i \\ 34.232 + 61.085i \\ 35.785 - 60.189i \end{pmatrix}$$

Build the voltage Vector

$$\text{null} := (0 \ 0 \ 0)$$

$$\text{E} := \text{stack}(\text{stack}(\text{ES}, \text{ER}), \text{null}^T)$$

$$\text{TS} := \text{augment}(\text{augment}(\text{one}, \text{zero}), \text{zero})$$

$$\text{TR} := \text{augment}(\text{augment}(\text{zero}, \text{one}), \text{zero})$$

$$\text{E} = \begin{pmatrix} 69.987 + 1.344i \\ -33.83 - 61.283i \\ -36.157 + 59.939i \\ 70 \\ -35 - 60.622i \\ -35 + 60.622i \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\text{TS} = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix}$$

$$\text{TR} = \begin{pmatrix} 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \end{pmatrix}$$

Building Fault Part of the Impedance Matrix:

$$ZFAG := ZFA + ZFG$$

$$ZFBG := ZFB + ZFG$$

$$ZFCG := ZFC + ZFG$$

$$ZFAG = 1.57$$

$$ZFBG = 1 \times 10^{10}$$

$$ZF := \begin{pmatrix} ZFAG & ZFG & ZFG \\ ZFG & ZFBG & ZFG \\ ZFG & ZFG & ZFCG \end{pmatrix}$$


$$ZF = \begin{pmatrix} 1.57 & 1.57 & 1.57 \\ 1.57 & 1 \times 10^{10} & 1.57 \\ 1.57 & 1.57 & 1 \times 10^{10} \end{pmatrix}$$

$$\begin{bmatrix} ES \\ ER \\ \text{null} \end{bmatrix} = \begin{bmatrix} ZSS & \text{zero} & \text{one} \\ \text{zero} & ZRR & \text{one} \\ -ZF & -ZF & \text{one} \end{bmatrix} \begin{bmatrix} IS \\ IR \\ VF \end{bmatrix}$$

$$FABCG := \text{augment}(\text{augment}(-ZF, -ZF), \text{one})$$

$$FABCG = \begin{pmatrix} -1.57 & -1.57 & -1.57 & -1.57 & -1.57 & -1.57 & 1 & 0 & 0 \\ -1.57 & -1 \times 10^{10} & -1.57 & -1.57 & -1 \times 10^{10} & -1.57 & 0 & 1 & 0 \\ -1.57 & -1.57 & -1 \times 10^{10} & -1.57 & -1.57 & -1 \times 10^{10} & 0 & 0 & 1 \end{pmatrix}$$

FINAL Z MATRIX

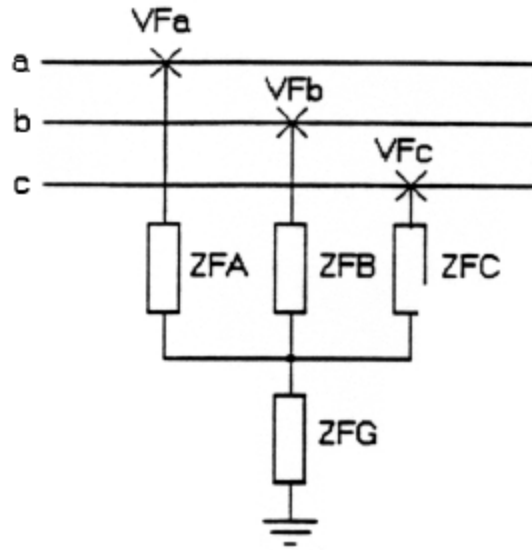

ZABCG := stack(ZSYS, FABCG)

$$ZABCG = \begin{pmatrix} 12.051 + 28.863i & 7.429 + 15.655i & 7.429 + 15.655i & 0 & 0 & 0 & 1 & 0 & 0 \\ 7.429 + 15.655i & 12.051 + 28.863i & 7.429 + 15.655i & 0 & 0 & 0 & 0 & 1 & 0 \\ 7.429 + 15.655i & 7.429 + 15.655i & 12.051 + 28.863i & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1.726 + 6.44i & 0.69 + 2.576i & 0.69 + 2.576i & 1 & 0 & 0 \\ 0 & 0 & 0 & 0.69 + 2.576i & 1.726 + 6.44i & 0.69 + 2.576i & 0 & 1 & 0 \\ 0 & 0 & 0 & 0.69 + 2.576i & 0.69 + 2.576i & 1.726 + 6.44i & 0 & 0 & 1 \\ -1.57 & -1.57 & -1.57 & -1.57 & -1.57 & -1.57 & 1 & 0 & 0 \\ -1.57 & -1 \times 10^{10} & -1.57 & -1.57 & -1 \times 10^{10} & -1.57 & 0 & 1 & 0 \\ -1.57 & -1.57 & -1 \times 10^{10} & -1.57 & -1.57 & -1 \times 10^{10} & 0 & 0 & 1 \end{pmatrix}$$

YABCG := ZABCG⁻¹

Fault Currents:

IABCG := YABCG·E

$$E = \begin{pmatrix} 69.987 + 1.344i \\ -33.83 - 61.283i \\ -36.157 + 59.939i \\ 70 \\ -35 - 60.622i \\ -35 + 60.622i \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad IABCG = \begin{pmatrix} 1.394 - 1.848i \\ -0.125 + 0.169i \\ -0.166 + 0.292i \\ 4.487 - 8.018i \\ 0.125 - 0.169i \\ 0.166 - 0.292i \\ 9.233 - 15.489i \\ -60.923 - 67.382i \\ -61.44 + 53.826i \end{pmatrix}$$

S - End Fault Currents:

$$IS := TS \cdot IABCG$$

$$IS = \begin{pmatrix} 1.394 - 1.848i \\ -0.125 + 0.169i \\ -0.166 + 0.292i \end{pmatrix}$$

R - End Fault Currents:

$$IR := TR \cdot IABCG$$

$$IR = \begin{pmatrix} 4.487 - 8.018i \\ 0.125 - 0.169i \\ 0.166 - 0.292i \end{pmatrix}$$

S - End Voltages

$$VS := ES - ZS \cdot IS$$

$$VS = \begin{pmatrix} 15.691 - 12.811i \\ -59.148 - 66.593i \\ -59.923 + 54.598i \end{pmatrix} \quad VSP = \begin{pmatrix} 69.97 + 0.447i \\ -34.597 - 60.819i \\ -35.372 + 60.372i \end{pmatrix}$$

R End Voltages * Additional Component for FI

$$VR := (ZR \cdot IR - ER)$$

$$VR = \begin{pmatrix} -39.614 + 7.741i \\ 47.962 + 64.001i \\ 48.221 - 57.225i \end{pmatrix} \quad VRP = \begin{pmatrix} -70.017 - 0.896i \\ 34.232 + 61.085i \\ 35.785 - 60.189i \end{pmatrix}$$

Line Prefault Load Currents from S Bus

$$\begin{array}{llllll} I_a := ISP_{RE_0} & |I_a| = 0.075 & \frac{\arg(I_a)}{\text{deg}} = 18.883 & 0.32 \cdot \frac{180}{3.14} = 18.344 & ISP_{RE} = \begin{pmatrix} 0.071 + 0.024i \\ -0.014 - 0.073i \\ -0.056 + 0.049i \end{pmatrix} \\ I_b := ISP_{RE_1} & |I_b| = 0.075 & \frac{\arg(I_b)}{\text{deg}} = -101.117 & & \\ I_c := ISP_{RE_2} & |I_c| = 0.075 & \frac{\arg(I_c)}{\text{deg}} = 138.883 & & IR_{PRE} = \begin{pmatrix} -0.071 - 0.024i \\ 0.014 + 0.073i \\ 0.056 - 0.049i \end{pmatrix} \end{array}$$

Line Prefault Voltages at S Bus

$$V_a := VSP_0 \quad |V_a| = 69.971 \quad \frac{\arg(V_a)}{\text{deg}} = 0.366$$

$$V_b := VSP_1 \quad |V_b| = 69.971 \quad \frac{\arg(V_b)}{\text{deg}} = -119.634$$

$$V_c := VSP_2 \quad |V_c| = 69.971 \quad \frac{\arg(V_c)}{\text{deg}} = 120.366$$

$$VSP = \begin{pmatrix} 69.97 + 0.447i \\ -34.597 - 60.819i \\ -35.372 + 60.372i \end{pmatrix}$$

Line Fault Currents from S Bus

$$I_{asf} := IS_0 \quad |I_{asf}| = 2.315 \quad \frac{\arg(I_{asf})}{\text{deg}} = -52.972$$

$$I_{bsf} := IS_1 \quad |I_{bsf}| = 0.21 \quad \frac{\arg(I_{bsf})}{\text{deg}} = 126.344$$

$$I_{csf} := IS_2 \quad |I_{csf}| = 0.336 \quad \frac{\arg(I_{csf})}{\text{deg}} = 119.705$$

$$IS = \begin{pmatrix} 1.394 - 1.848i \\ -0.125 + 0.169i \\ -0.166 + 0.292i \end{pmatrix}$$

Line Fault Currents from R Bus

$$I_{arf} := IR_0 \quad |I_{arf}| = 9.188 \quad \frac{\arg(I_{arf})}{\text{deg}} = -60.768$$

$$I_{brf} := IR_1 \quad |I_{brf}| = 0.21 \quad \frac{\arg(I_{brf})}{\text{deg}} = -53.656$$

$$I_{crf} := IR_2 \quad |I_{crf}| = 0.336 \quad \frac{\arg(I_{crf})}{\text{deg}} = -60.295$$

$$IR = \begin{pmatrix} 4.487 - 8.018i \\ 0.125 - 0.169i \\ 0.166 - 0.292i \end{pmatrix}$$

Line Fault Voltages at S Bus

$$VSP = \begin{pmatrix} 69.97 + 0.447i \\ -34.597 - 60.819i \\ -35.372 + 60.372i \end{pmatrix}$$

$$V_{asf} := VS_0 \quad |V_{asf}| = 20.256 \quad \frac{\arg(V_{asf})}{\text{deg}} = -39.229$$

$$V_{bsf} := VS_1 \quad |V_{bsf}| = 89.068 \quad \frac{\arg(V_{bsf})}{\text{deg}} = -131.611$$

$$V_{csf} := VS_2 \quad |V_{csf}| = 81.066 \quad \frac{\arg(V_{csf})}{\text{deg}} = 137.662$$

$$VS = \begin{pmatrix} 15.691 - 12.811i \\ -59.148 - 66.593i \\ -59.923 + 54.598i \end{pmatrix}$$

Line Fault Voltage at R Bus

$$V_{arf} := VR_0 \quad |V_{arf}| = 40.364$$

$$\frac{\arg(V_{arf})}{\text{deg}} = 168.943$$

$$V_{brf} := VR_1 \quad |V_{brf}| = 79.978$$

$$\frac{\arg(V_{brf})}{\text{deg}} = 53.152$$

$$V_{crf} := VR_2 \quad |V_{crf}| = 74.833$$

$$\frac{\arg(V_{crf})}{\text{deg}} = -49.881$$

$$IS = \begin{pmatrix} 1.394 - 1.848i \\ -0.125 + 0.169i \\ -0.166 + 0.292i \end{pmatrix}$$

Residual Current and Voltage Vsr, Vrr, Isr, Irr

$$I_{srf} := \sum_{i=0}^2 IS_j = 1.103 - 1.387i$$

$$I_{rrf} := \sum_{i=0}^2 IR_j = 4.778 - 8.479i$$

$$IR = \begin{pmatrix} 4.487 - 8.018i \\ 0.125 - 0.169i \\ 0.166 - 0.292i \end{pmatrix}$$

$$V_{srf} := \sum_{j=0}^2 VS_j = -103.38 - 24.806i$$

$$V_{rrf} := \sum_{j=0}^2 VR_j = 56.569 + 14.516i$$

$$VS = \begin{pmatrix} 15.691 - 12.811i \\ -59.148 - 66.593i \\ -59.923 + 54.598i \end{pmatrix}$$

$$\arg(I_{srf}) = -0.899$$

$$\arg(V_{srf}) = -2.906$$

$$\arg(I_{rrf}) = -1.058$$

$$\arg(V_{rrf}) = 0.251$$

$$IRPRE_r := \sum_{j=0}^2 IRPRE_j = 0$$

$$ISPRE_r := \sum_{j=0}^2 ISPRE_j = 0$$

$$VR = \begin{pmatrix} -39.614 + 7.741i \\ 47.962 + 64.001i \\ 48.221 - 57.225i \end{pmatrix}$$

$$VRPr := \sum_{j=0}^2 VRP_j = 7.105 \times 10^{-15} - 2.842i \times 10^{-14}$$

$$VSPr := \sum_{j=0}^2 VSP_j = -1.421 \times 10^{-14} + 2.132i \times 10^{-14}$$

$$Z0s := \frac{Vsrf}{Isrf} = -25.357 - 54.378i$$

$$Z0r := \frac{Vrrf}{Irrf} = 1.554 + 5.796i$$

Wattmeteric Method ????

$$S0S := Vsrf \cdot \overline{Isrf}$$

$$S0R := Vrrf \cdot \overline{Irrf}$$

$$\text{Re}(S0S) = -79.613$$

$$\text{Re}(S0R) = 147.195$$

So How do we generate digital signals of Voltage and Current of the Simulation 4 Cycles with 7680 samples per second (128 samples per cycle in 60HZ system)?

For S side

$$k := 0 .. 511$$

$$\text{delT} := 0.0001302$$

$$\frac{1}{\text{delT}} = 7.68 \times 10^3$$

$$\frac{7680}{60} = 128$$

$$V_{an_k} := |VSP_0| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(VSP_0))$$

$$T1_k := k \cdot \text{delT}$$

$$T2_k := 512 \cdot \text{delT} + k \cdot \text{delT}$$

$$T3_k := 1024 \cdot \text{delT} + k \cdot \text{delT}$$

$$V_{bn_k} := |VSP_1| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(VSP_1))$$

$$V_{cn_k} := |VSP_2| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(VSP_2))$$

$$V_{af_k} := |VS_0| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(VS_0))$$

$$V_{bf_k} := |VS_1| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(VS_1))$$

$$V_{cf_k} := |VS_2| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(VS_2))$$

$$T1_k =$$

| |
|--------------------------|
| 0 |
| 1.302 · 10 ⁻⁴ |
| 2.604 · 10 ⁻⁴ |
| 3.906 · 10 ⁻⁴ |
| 5.208 · 10 ⁻⁴ |

$$I_{an_k} := |ISP_{RE_0}| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(ISP_{RE_0}))$$

$$I_{bn_k} := |ISP_{RE_1}| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(ISP_{RE_1}))$$



$$I_{cn_k} := |ISP_{RE_2}| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(ISP_{RE_2}))$$

$$I_{af_k} := |IS_0| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(IS_0))$$

$$I_{bf_k} := |IS_1| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(IS_1))$$

$$I_{cf_k} := |IS_2| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{delT} + \arg(IS_2))$$

| |
|-----------------------|
| $6.51 \cdot 10^{-4}$ |
| $7.812 \cdot 10^{-4}$ |
| $9.114 \cdot 10^{-4}$ |
| $1.042 \cdot 10^{-3}$ |
| $1.172 \cdot 10^{-3}$ |
| $1.302 \cdot 10^{-3}$ |
| $1.432 \cdot 10^{-3}$ |
| $1.562 \cdot 10^{-3}$ |
| $1.693 \cdot 10^{-3}$ |
| $1.823 \cdot 10^{-3}$ |
| ... |

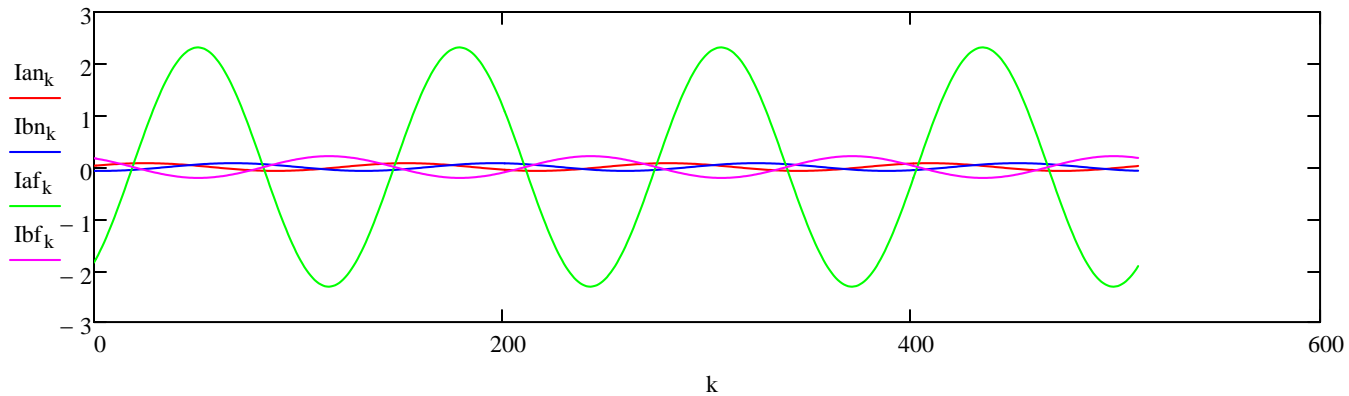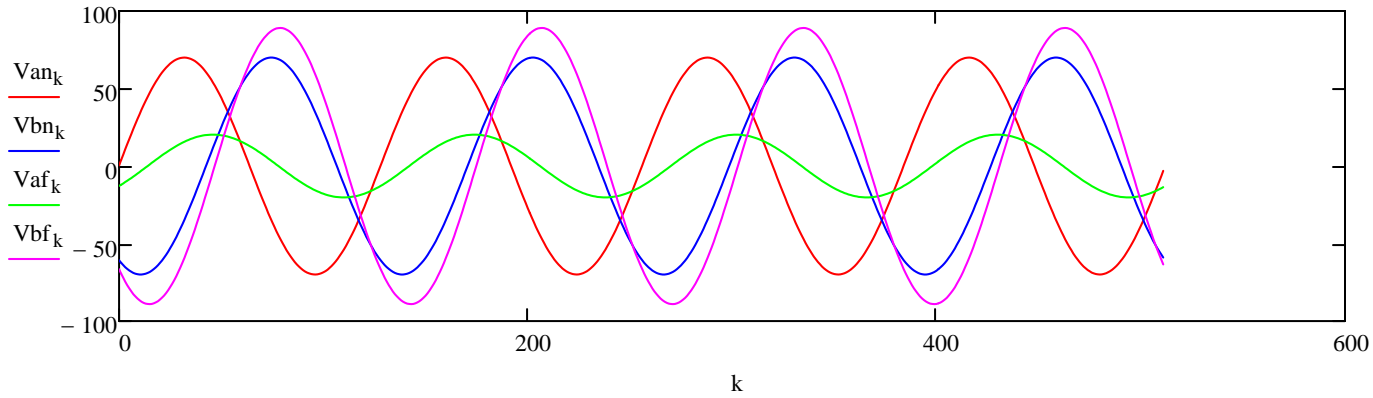

Let us make Normal (4 cycle)+ Fault (4 cycle) +Normal (4 cycle)

Seg1 := augment(T1, Ian, Ibn, Icn, Van, Vbn, Vcn)

Seg2 := augment(T2, Iaf, Ibf, Icf, Vaf, Vbf, Vcf)


Seg3 := augment(T3, Ian, Ibn, Icn, Van, Vbn, Vcn)



Final := stack(Seg1, Seg2, Seg3)

$T := \text{Final}^{(0)}$ $IaS := \text{Final}^{(1)}$ $IbS := \text{Final}^{(2)}$ $IcS := \text{Final}^{(3)}$ $VaS := \text{Final}^{(4)}$ $VbS := \text{Final}^{(5)}$ $VcS := \text{Final}^{(6)}$

$IrS := IaS + IbS + IcS$

$VrS := VaS + VbS + VcS$

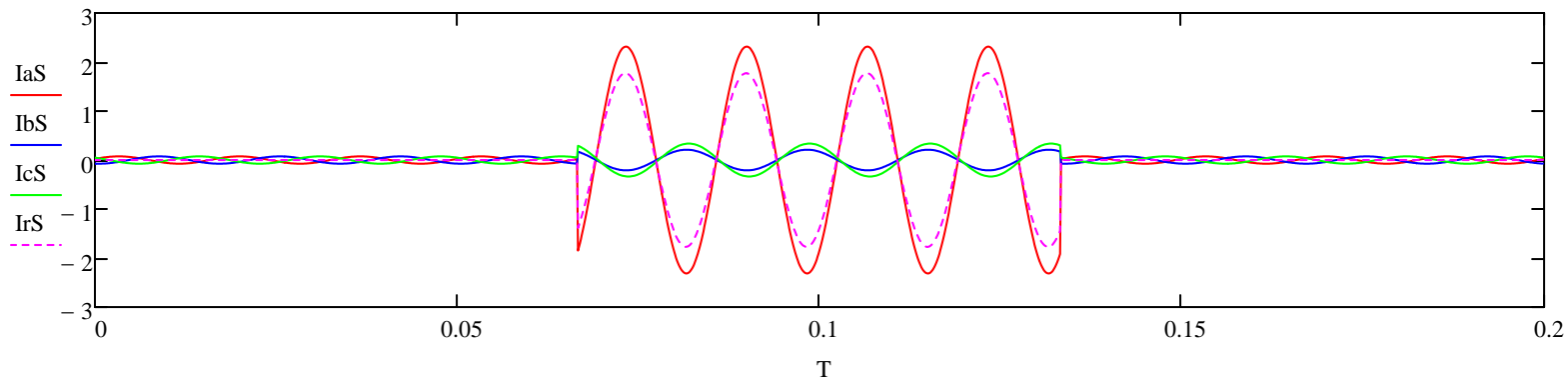

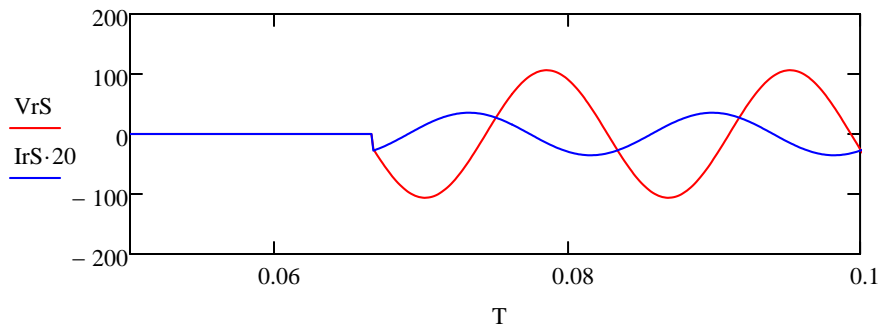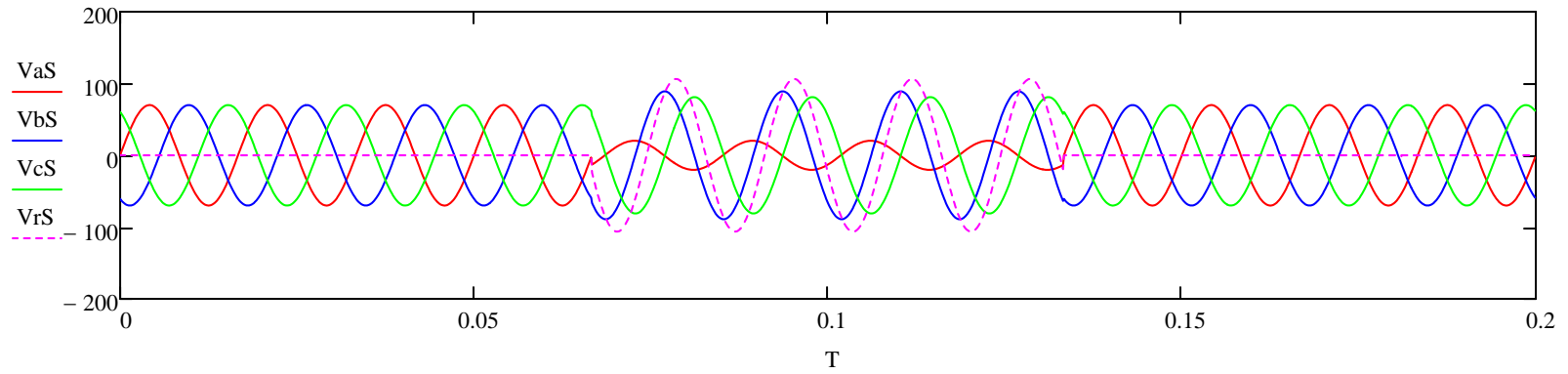

$$VrS_{600} = 104.999$$

$$IrS_{600} = -0.488$$

$$dT := 0.000130208$$

$$\omega := 2 \cdot \pi \cdot 60$$

$$\omega = 376.991$$

$$mm := 1536$$

$$window := 128$$

$$wind := window - 1$$

Now for all the calculations

$$dd := 0 .. \frac{mm}{window} - 1$$

$$kk := 0 .. mm - window$$

$$k := 0 .. \frac{mm - window}{8}$$

$$UrS_k := \text{submatrix}(VrS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$ArS_k := \text{submatrix}(IrS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$UaS_k := \text{submatrix}(VaS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$AaS_k := \text{submatrix}(IaS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$UbS_k := \text{submatrix}(VbS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$AbS_k := \text{submatrix}(IbS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$UcS_k := \text{submatrix}(VcS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$AcS_k := \text{submatrix}(IcS, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$PrS_k := \text{FFT}(UrS_k)$$

$$FrS_k := \text{FFT}(ArS_k)$$

$$\text{CompS}_k := \left(PrS_k \right)_{1,0} \cdot \overline{\left(FrS_k \right)_{1,0}}$$

$$\text{CompS}_{100} = -19.901 - 42.683i$$

$$\text{CompS}_{101} = -19.9 - 42.683i$$

$$\text{WattS}_k := \text{Re}(\text{CompS}_k)$$

$$\text{PaS}_k := \text{FFT}(\text{UaS}_k) \quad \text{PbS}_k := \text{FFT}(\text{UbS}_k) \quad \text{PcS}_k := \text{FFT}(\text{UcS}_k)$$

$$\text{FaS}_k := \text{FFT}(\text{AaS}_k) \quad \text{FbS}_k := \text{FFT}(\text{AbS}_k) \quad \text{FcS}_k := \text{FFT}(\text{AcS}_k)$$

$$\text{CaS}_k := (\text{PaS}_k)_{1,0} \cdot \overline{(\text{FaS}_k)_{1,0}}$$


$$\text{CbS}_k := (\text{PbS}_k)_{1,0} \cdot \overline{(\text{FbS}_k)_{1,0}}$$

$$\text{CcS}_k := (\text{PcS}_k)_{1,0} \cdot \overline{(\text{FcS}_k)_{1,0}}$$

$$\text{RaS}_k := \text{Re}(\text{CaS}_k)$$

$$\text{RbS}_k := \text{Re}(\text{CbS}_k)$$
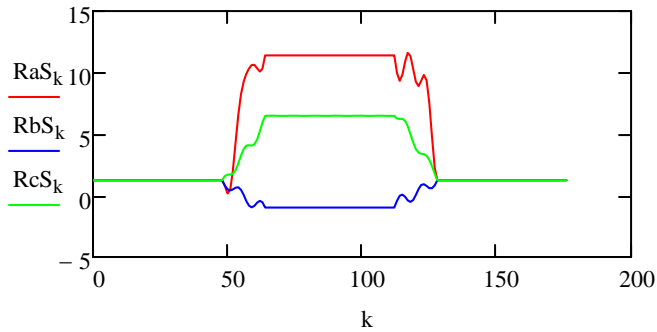
$$\text{RcS}_k := \text{Re}(\text{CcS}_k)$$



Phase a:

$$\text{Ima}_k := \begin{bmatrix} (\text{FaS}_k)_{1,0} \\ (\text{FbS}_k)_{1,0} \\ (\text{FcS}_k)_{1,0} \end{bmatrix}$$

$$\begin{aligned} \text{Z1L} &= 1.035 + 3.864i \\ \text{Z0L} &= 3.105 + 11.592i \end{aligned}$$

$$\alpha a := e^{\frac{2i \cdot \pi}{3}}$$

$$Am_k := \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha a & (\alpha a)^2 \\ 1 & (\alpha a)^2 & \alpha a \end{bmatrix}$$

Phase a:

$$I_{aseq_k} := Am_k \cdot I_{ma_k}$$

$$I_{0a_k} := (I_{aseq_k})_0$$

$$I_{2a_k} := (I_{aseq_k})_2$$

Yang method:

$$K2 := \frac{Z_{0L} - Z_{1L}}{Z_{1L}}$$

Compensated current:

Phase a:

$$I_{a12_k} := FaS_k + K2 \cdot I_{0a_k}$$

$$\alpha a^2_k := \arg(I_{a12_k}) - \arg(I_{2a_k})$$

Resistance and Reactance:

$$X_{11} := \text{Im}(Z_{1L}) \quad X_{11} = 3.864$$

$$R_{11} := \text{Re}(Z_{1L}) \quad R_{11} = 1.035$$

Phase Impedance:

Phase a:

$$Za1_k := \frac{PaS_k}{(Ia12_k)_{1,0}}$$


$$Xa1_k := \text{Im}\left[\left(Za1_k\right)_{1,0}\right]$$

$$Ra1_k := \text{Re}\left[\left(Za1_k\right)_{1,0}\right]$$

Fault Distance:

$$ma_k := \frac{(Xa1_k) + (Ra1_k) \cdot \tan\left[\left(\alpha a2_k\right)_{1,0}\right]}{X11 + R11 \cdot \tan\left[\left(\alpha a2_k\right)_{1,0}\right]}$$

$$m = 0.5$$

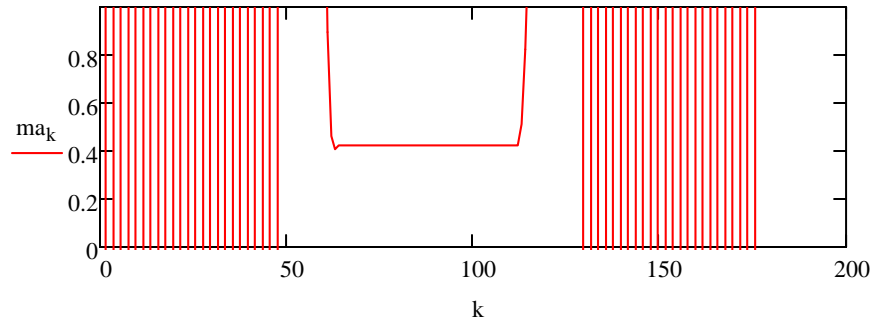

$$\begin{aligned}
 ma_{60} &= 1.905 \\
 ma_{40} &= 69.834 \\
 ma_{70} &= 0.424 \\
 ma_{100} &= 0.423 \\
 ma_{110} &= 0.424
 \end{aligned}$$

Results and Discussion Part1:

When changing the m value (place of the fault) at start of the file ma is changing in same relation. However, ma values seem to come more exact when m is bigger.

| | |
|----------|------------|
| $m=0.25$ | $ma=0.217$ |
| $m=0.45$ | $ma=0.41$ |
| $m=0.5$ | $ma=0.459$ |
| $m=0.75$ | $ma=0.695$ |
| $m=0.9$ | $ma=0.83$ |

Fault resistance ZFG was changed and fault place m was constant ($m=0.5$). If the change of resistance is minor, algorithm works. If value of ZFG increase much, algorithm stops working.

| | |
|--------------|--------------------------|
| $m=0.5$ | |
| ZFG=0.4+j0 | $ma=0.48$ |
| ZFG= 0.85+j0 | $ma=0.458$ |
| ZFG=1.57+j0 | $ma=0.423$ |
| ZFG= 10+j0 | $ma=7.378 \cdot 10^{-3}$ |