

FAULT DETECTION AND LOCATION IN DISTRIBUTION SYSTEMS

Jani Valtari - 11.6.2010

FINAL EXAM

ALL TEXT ADDITIONS TO GIVEN TEMPLATE FILE IN GREEN COLOUR
(Style Normal_Valtari)

INPUT DATA

$$\textcolor{green}{\delta} := 0.001 \quad \text{Voltage Phase Angle}$$

$$\textcolor{green}{es} := 70 \cdot e^{j \cdot \delta \cdot \text{deg}} \quad \text{Source S Voltage} \quad \textcolor{green}{es} = 70 + 1.222i \times 10^{-3}$$

$$\textcolor{green}{er} := 0 \quad \text{Source R Voltage is zero in patent 5}$$

$$Z1S := 4.104 + j \cdot 11.276 \quad \text{Source S Positive Sequence Impedance}$$

$$Z0S := 25.357 + j \cdot 54.378 \quad \text{Source S Zero Sequence Impedance}$$

$$Z1R := 0.518 + j \cdot 1.932 \quad \text{Source R Positive Sequence Impedance}$$

$$Z0R := 3 \cdot Z1R \quad \text{Source S Zero Sequence Impedance}$$

$$Z1L := 1.035 + j \cdot 3.864 \quad \text{Positive Sequence Line Impedance}$$

$$Z0L := 3 \cdot Z1L \quad \text{Zero Sequence Line Impedance}$$

$$\textcolor{green}{Z0L} := 30 + 39i \quad \textcolor{green}{Z1L} := 10 + 13i$$

Corrected values lecture xmcd (creelman)

$$\textcolor{green}{Z0S} := 0 \quad \textcolor{green}{Z1S} := 0$$

ZS was set to zero in the patent 5

Fault Location

$$\textcolor{green}{m} := 0.4$$

$$\text{Fault Impedances (for AG fault case)} \quad \text{INF} := 10^{10}$$

$$ZFA := 0 + j \cdot 0 \quad ZFB := \text{INF} + j \cdot 0 \quad ZFC := \text{INF} + j \cdot 0$$

Fault Resistance

$$Z_{FG} := 0.85 + j \cdot 0$$

CONSTANTS

$$\text{rad} := 1 \quad \text{deg} := \frac{\pi}{180} \cdot \text{rad}$$

Operator

$$a := e^{j \cdot 120 \cdot \text{deg}} \quad a = -0.5 + 0.866i$$

$$\text{BAL} := \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \text{one} := \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{pmatrix} \quad \text{zero} := \begin{pmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{pmatrix}$$

Three phase voltages at S and R


$$ES := es \cdot \text{BAL}$$

$$ES = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

$$ER := er \cdot \text{BAL}$$

$$ER = \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix}$$

CIRCUIT EQUATION

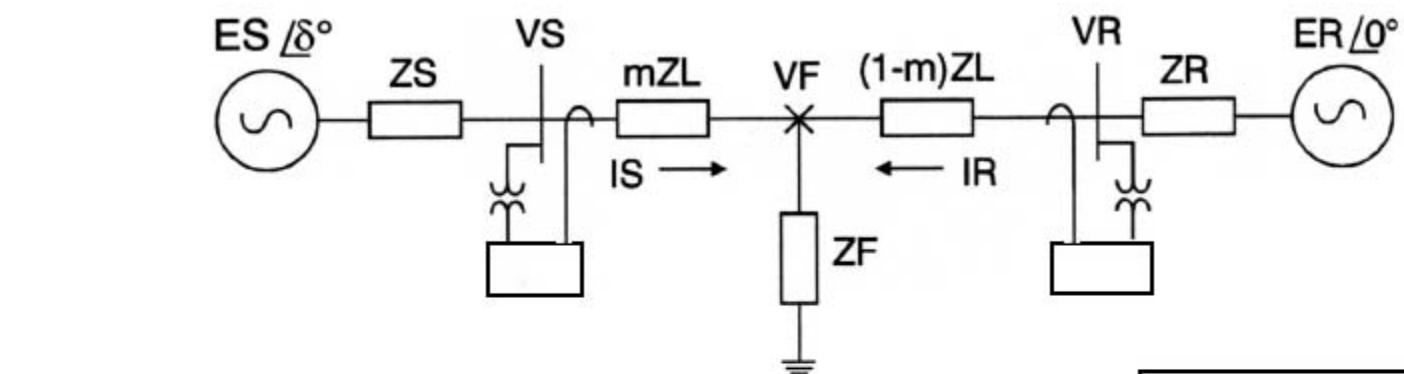

$$\begin{aligned}
 ES &= [ZS + m \cdot ZL] \cdot IS + 0 + VF \\
 ER &= +0 + [ZR + (1-m) \cdot ZL] \cdot IR + VF \\
 0 &= -ZF \cdot IS - ZF \cdot IR + VF
 \end{aligned}$$

$$\begin{aligned}
 ES &= ZSS \cdot IS + 0 + VF \\
 ER &= +0 + ZRR \cdot IR + VF \\
 0 &= -ZF \cdot IS - ZF \cdot IR + VF
 \end{aligned}$$

(
 $ZSS = [ZS + m \cdot ZL]$
 $ZRR = [ZR + (1-m) \cdot ZL]$
)

In 3-phase matrix form, the equation looks like this:

$$\begin{bmatrix} ES \\ ER \\ \text{null} \end{bmatrix} = \begin{bmatrix} ZSS & \text{zero} & \text{one} \\ \text{zero} & ZRR & \text{one} \\ -ZF & -ZF & \text{one} \end{bmatrix} \begin{bmatrix} IS \\ IR \\ VF \end{bmatrix}$$

How do we form the source impedance ZS and ZR ?

Let us consider the link between 3-phase circuit and symmetrical components

Conversion of positive sequence and zero sequence impedances to Self and Mutual impedances

$$zs(z0, z1) := \frac{2 \cdot z1 + z0}{3} \quad zm(z0, z1) := \frac{z0 - z1}{3}$$

Conversion Matrix Format

$$Z(z0, z1) := \begin{pmatrix} zs(z0, z1) & zm(z0, z1) & zm(z0, z1) \\ zm(z0, z1) & zs(z0, z1) & zm(z0, z1) \\ zm(z0, z1) & zm(z0, z1) & zs(z0, z1) \end{pmatrix}$$

Now Conversion

$$ZS := Z(Z0S, Z1S) \quad ZL := Z(Z0L, Z1L) \quad ZR := Z(Z0R, Z1R)$$

$$ZS = \begin{pmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{pmatrix}$$

$$ZR = \mathbf{I}$$

$$ZL = \begin{pmatrix} 16.667 + 21.667i & 6.667 + 8.667i & 6.667 + 8.667i \\ 6.667 + 8.667i & 16.667 + 21.667i & 6.667 + 8.667i \\ 6.667 + 8.667i & 6.667 + 8.667i & 16.667 + 21.667i \end{pmatrix}$$

Source and Line Impedances to the Fault

$$ZSS := ZS + m \cdot ZL$$

$$ZSS = \begin{pmatrix} 6.667 + 8.667i & 2.667 + 3.467i & 2.667 + 3.467i \\ 2.667 + 3.467i & 6.667 + 8.667i & 2.667 + 3.467i \\ 2.667 + 3.467i & 2.667 + 3.467i & 6.667 + 8.667i \end{pmatrix}$$

$$ZRR := ZR + (1 - m) \cdot ZL$$

$$ZRR = \begin{pmatrix} 10.863 + 16.22i & 4.345 + 6.488i & 4.345 + 6.488i \\ 4.345 + 6.488i & 10.863 + 16.22i & 4.345 + 6.488i \\ 4.345 + 6.488i & 4.345 + 6.488i & 10.863 + 16.22i \end{pmatrix}$$

Build System Part of the Impedance Matrix

$$\begin{bmatrix} ES \\ ER \\ null \end{bmatrix} = \begin{bmatrix} ZSS & zero & one \\ zero & ZRR & one \\ -ZF & -ZF & one \end{bmatrix} \begin{bmatrix} IS \\ IR \\ VF \end{bmatrix}$$

$$ES = \begin{bmatrix} ES_a \\ ES_b \\ ES_c \end{bmatrix} \quad ER = \begin{bmatrix} ER_a \\ ER_b \\ ER_c \end{bmatrix} \quad VF = \begin{bmatrix} VF_a \\ VF_b \\ VF_c \end{bmatrix} \quad IS = \begin{bmatrix} IS_a \\ IS_b \\ IS_c \end{bmatrix} \quad IR = \begin{bmatrix} IR_a \\ IR_b \\ IR_c \end{bmatrix}$$

ZTOP := augment(augment(ZSS, zero), one)

$$ZTOP = \begin{pmatrix} 6.667 + 8.667i & 2.667 + 3.467i & 2.667 + 3.467i & 0 & 0 & 0 & 1 & 0 & 0 \\ 2.667 + 3.467i & 6.667 + 8.667i & 2.667 + 3.467i & 0 & 0 & 0 & 0 & 1 & 0 \\ 2.667 + 3.467i & 2.667 + 3.467i & 6.667 + 8.667i & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}$$

ZMID := augment(augment(zero, ZRR), one)

$$ZMID = \begin{pmatrix} 0 & 0 & 0 & 10.863 + 16.22i & 4.345 + 6.488i & 4.345 + 6.488i & 1 & 0 & 0 \\ 0 & 0 & 0 & 4.345 + 6.488i & 10.863 + 16.22i & 4.345 + 6.488i & 0 & 1 & 0 \\ 0 & 0 & 0 & 4.345 + 6.488i & 4.345 + 6.488i & 10.863 + 16.22i & 0 & 0 & 1 \end{pmatrix}$$

ZSYS := stack(ZTOP, ZMID)

$$ZSYS = \begin{pmatrix} 6.667 + 8.667i & 2.667 + 3.467i & 2.667 + 3.467i & 0 & 0 & 0 & 1 & 0 & 0 \\ 2.667 + 3.467i & 6.667 + 8.667i & 2.667 + 3.467i & 0 & 0 & 0 & 0 & 1 & 0 \\ 2.667 + 3.467i & 2.667 + 3.467i & 6.667 + 8.667i & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 10.863 + 16.22i & 4.345 + 6.488i & 4.345 + 6.488i & 1 & 0 & 0 \\ 0 & 0 & 0 & 4.345 + 6.488i & 10.863 + 16.22i & 4.345 + 6.488i & 0 & 1 & 0 \\ 0 & 0 & 0 & 4.345 + 6.488i & 4.345 + 6.488i & 10.863 + 16.22i & 0 & 0 & 1 \end{pmatrix}$$

Pre-fault conditions:

ZPRE := ZS + ZL + ZR

$$ZPRE = \begin{pmatrix} 17.53 + 24.887i & 7.012 + 9.955i & 7.012 + 9.955i \\ 7.012 + 9.955i & 17.53 + 24.887i & 7.012 + 9.955i \\ 7.012 + 9.955i & 7.012 + 9.955i & 17.53 + 24.887i \end{pmatrix}$$

IPRE := $ZPRE^{-1} \cdot (ES - ER)$

$$IPRE = \begin{pmatrix} 2.207 - 3.133i \\ -3.817 - 0.345i \\ 1.61 + 3.478i \end{pmatrix}$$

Pre-fault voltage at S end

VSP := ES - ZS·IPRE

$$VSP = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

$$ES = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

Build the voltage Vector

```

null := (0 0 0)
E := stack(stack(ES,ER),nullT)
TS := augment(augment(one,zero),zero)
TR := augment(augment(zero,one),zero)

```

$$E = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$TS = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix}$$

$$TR = \begin{pmatrix} 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \end{pmatrix}$$

Building Fault Part of the Impedance Matrix:

- the fault impedance ZF
- voltage drop due to each phase current flowing individually in the phase-fault impedances (ZFA, ZFB, or ZFC) and mutually in the ground-fault impedance ZFG.

$$ZF = \begin{bmatrix} ZFAG & ZFG & ZFG \\ ZFG & ZFBG & ZFG \\ ZFG & ZFG & ZFCG \end{bmatrix}$$

where: $\left\{ \begin{array}{l} ZFAG = ZFA + ZFG \\ ZFBG = ZFB + ZFG \\ ZFCG = ZFC + ZFG \end{array} \right.$


ZFAG := ZFA + ZFG

ZFBG := ZFB + ZFG

ZFCG := ZFC + ZFG

$$ZFAG = 0.85$$

$$ZFBG = 1 \times 10^{10}$$

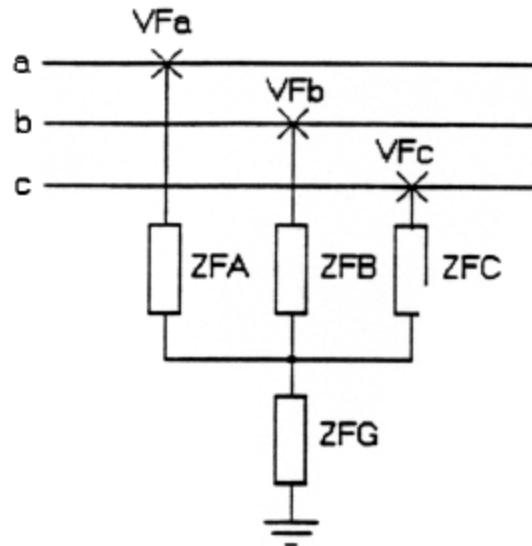

$$ZF := \begin{pmatrix} ZFAG & ZFG & ZFG \\ ZFG & ZFBG & ZFG \\ ZFG & ZFG & ZFCG \end{pmatrix}$$

$$ZF = \begin{pmatrix} 0.85 & 0.85 & 0.85 \\ 0.85 & 1 \times 10^{10} & 0.85 \\ 0.85 & 0.85 & 1 \times 10^{10} \end{pmatrix}$$

$$\begin{bmatrix} ES \\ ER \\ null \end{bmatrix} = \begin{bmatrix} ZSS & zero & one \\ zero & ZRR & one \\ -ZF & -ZF & one \end{bmatrix} \begin{bmatrix} IS \\ IR \\ VF \end{bmatrix}$$

FABCG := augment(augment(-ZF, -ZF), one)

$$FABCG = \begin{pmatrix} -0.85 & -0.85 & -0.85 & -0.85 & -0.85 & -0.85 & 1 & 0 & 0 \\ -0.85 & -1 \times 10^{10} & -0.85 & -0.85 & -1 \times 10^{10} & -0.85 & 0 & 1 & 0 \\ -0.85 & -0.85 & -1 \times 10^{10} & -0.85 & -0.85 & -1 \times 10^{10} & 0 & 0 & 1 \end{pmatrix}$$

FINAL Z MATRIX

ZABCG := stack(ZSYS, FABCG)

$$ZABCG = \begin{pmatrix} 6.667 + 8.667i & 2.667 + 3.467i & 2.667 + 3.467i & 0 & 0 & 0 & 1 & 0 & 0 \\ 2.667 + 3.467i & 6.667 + 8.667i & 2.667 + 3.467i & 0 & 0 & 0 & 0 & 1 & 0 \\ 2.667 + 3.467i & 2.667 + 3.467i & 6.667 + 8.667i & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 10.863 + 16.22i & 4.345 + 6.488i & 4.345 + 6.488i & 1 & 0 & 0 \\ 0 & 0 & 0 & 4.345 + 6.488i & 10.863 + 16.22i & 4.345 + 6.488i & 0 & 1 & 0 \\ 0 & 0 & 0 & 4.345 + 6.488i & 4.345 + 6.488i & 10.863 + 16.22i & 0 & 0 & 1 \\ -0.85 & -0.85 & -0.85 & -0.85 & -0.85 & -0.85 & 1 & 0 & 0 \\ -0.85 & -1 \times 10^{10} & -0.85 & -0.85 & -1 \times 10^{10} & -0.85 & 0 & 1 & 0 \\ -0.85 & -0.85 & -1 \times 10^{10} & -0.85 & -0.85 & -1 \times 10^{10} & 0 & 0 & 1 \end{pmatrix}$$

YABCG := ZABCG⁻¹

Fault Currents:

IABCG := YABCG · E

$$E = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad IABCG = \begin{pmatrix} 4.864 - 5.872i \\ -3.817 - 0.345i \\ 1.61 + 3.478i \\ -0.823 + 1.505i \\ 3.817 + 0.345i \\ -1.61 - 3.478i \\ 3.435 - 3.711i \\ -38.101 - 41.302i \\ -39.932 + 36.43i \end{pmatrix}$$

S - End Fault Currents:

$$IS := TS \cdot IABC_G$$

$$IS = \begin{pmatrix} 4.864 - 5.872i \\ -3.817 - 0.345i \\ 1.61 + 3.478i \end{pmatrix}$$

R - End Fault Currents:

$$IR := TR \cdot IABC_G$$

$$IR = \begin{pmatrix} -0.823 + 1.505i \\ 3.817 + 0.345i \\ -1.61 - 3.478i \end{pmatrix}$$

S - End Voltages

$$VS := ES - ZS \cdot IS$$

$$VS = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

Line Prefault Load Currents from S Bus

$$I_a := IPRE_0 \quad |I_a| = 3.833$$

$$\frac{\arg(I_a)}{\deg} = -54.838 \quad 0.32 \cdot \frac{180}{3.14} = 18.344$$

$$I_b := IPRE_1 \quad |I_b| = 3.833$$

$$\frac{\arg(I_b)}{\deg} = -174.838$$

$$I_c := IPRE_2 \quad |I_c| = 3.833$$

$$\frac{\arg(I_c)}{\deg} = 65.162$$

$$IPRE = \begin{pmatrix} 2.207 - 3.133i \\ -3.817 - 0.345i \\ 1.61 + 3.478i \end{pmatrix}$$

Line Prefault Voltages at S Bus

$$V_a := VSP_0 \quad |V_a| = 70$$

$$\frac{\arg(V_a)}{\deg} = 1 \times 10^{-3}$$

$$VSP = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

$$Vb := VSP_1 \quad |Vb| = 70 \quad \frac{\arg(Vb)}{\deg} = -119.999$$

$$Vc := VSP_2 \quad |Vc| = 70 \quad \frac{\arg(Vc)}{\deg} = 120.001$$

Line Fault Currents from S Bus

$$Iasf := IS_0 \quad |Iasf| = 7.624 \quad \frac{\arg(Iasf)}{\deg} = -50.363$$

$$Ibsf := IS_1 \quad |Ibsf| = 3.833 \quad \frac{\arg(Ibsf)}{\deg} = -174.838$$

$$Icsf := IS_2 \quad |Icsf| = 3.833 \quad \frac{\arg(Icsf)}{\deg} = 65.162$$

$$IS = \begin{pmatrix} 4.864 - 5.872i \\ -3.817 - 0.345i \\ 1.61 + 3.478i \end{pmatrix}$$

Line Fault Currents from R Bus

$$Iarf := IR_0 \quad |Iarf| = 1.715 \quad \frac{\arg(Iarf)}{\deg} = 118.661$$

$$Ibrf := IR_1 \quad |Ibrf| = 3.833 \quad \frac{\arg(Ibrf)}{\deg} = 5.162$$

$$Icrf := IR_2 \quad |Icrf| = 3.833 \quad \frac{\arg(Icrf)}{\deg} = -114.838$$

$$IR = \begin{pmatrix} -0.823 + 1.505i \\ 3.817 + 0.345i \\ -1.61 - 3.478i \end{pmatrix}$$

Line Fault Voltages at S Bus

$$Vaf := VS_0 \quad |Vaf| = 70 \quad \frac{\arg(Vaf)}{\deg} = 1 \times 10^{-3}$$

$$VSP = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

$$V_{bf} := VS_1 \quad |V_{bf}| = 70$$

$$\frac{\arg(V_{bf})}{\text{deg}} = -119.999$$

$$VS = \begin{pmatrix} 70 + 1.222i \times 10^{-3} \\ -34.999 - 60.622i \\ -35.001 + 60.621i \end{pmatrix}$$

$$V_{cf} := VS_2 \quad |V_{cf}| = 70$$

$$\frac{\arg(V_{cf})}{\text{deg}} = 120.001$$

Residual Current Ir

$$Ir := \sum_{j=0}^2 IS_j \quad Ir = 2.657 - 2.738i$$

$$IS = \begin{pmatrix} 4.864 - 5.872i \\ -3.817 - 0.345i \\ 1.61 + 3.478i \end{pmatrix}$$

$$Ir_{PRE} := \sum_{j=0}^2 IPRE_j = 1.776i \times 10^{-15}$$

Phase A SLG Fault

$$Va = m \cdot Z1L \cdot (Ia + k_0 \cdot Ir) + R_F \cdot I_F$$

$$m = \frac{Va - R_F \cdot I_F}{Z1L \cdot (Ia + k_0 \cdot Ir)}$$

$$Vaf = 70 + 1.222i \times 10^{-3} \quad Z1L = 10 + 13i$$

$$Iasf = 4.864 - 5.872i \quad R_f := \text{Re}(ZFAG)$$

$$k_0 := \frac{Z0L - Z1L}{3 \cdot Z1L} \quad R_f = 0.85$$

$$Ir = 2.657 - 2.738i$$

$$If := Iasf + Iarf = 4.041 - 4.366i$$

Fault Current

Impedance to the Fault

$$m_{Calc} := \frac{(Vaf - R_f \cdot If)}{(Iasf + k_0 \cdot Ir) \cdot Z1L} = 0.4$$

Fault Distance

$$m = 0.4$$

$$|m_{Calc}| = 0.4$$

$$|Z1L| = 16.401$$

Line Length

$$Ds := \frac{Iasf}{If} \quad \text{Distribution Factor}$$

$$Ns := \frac{I_{asf}}{I_{asf} - IPRE_0} = 1.992 - 0.157i$$

Loading Factor

$$m = 0.4$$

$$m_{Calc2} := \frac{1}{Z_{1L}} \cdot \left(\frac{V_{af}}{I_{asf} + k_0 \cdot I_r} - \frac{R_f}{D_s \cdot N_s} \right) = 0.405 - 9.125i \times 10^{-3}$$

Fault Distance

$$|m_{Calc2}| = 0.405$$

Zero Sequence Current Distribution Factor, Dn

$$d_s = \frac{Z_H + (1-m)Z_L}{Z_G + Z_H + Z_U}$$

$$\arg(D_s) = -0.055$$

$$D_s := \frac{Z_{0R} + (1 - m) \cdot Z_{0L}}{Z_{0S} + Z_{0R} + Z_{0L}} = 0.641 + 0.015i$$

$$\beta := \arg(D_s) = 0.024$$

$$\theta := -\beta = -0.024$$

distance L (which is supposed to be same as m) by [modified] Takagi Method

$$L_w := \frac{\text{Im} \left[Vaf \left(I_r \cdot e^{j \cdot \theta} \right) \right]}{\text{Im} \left[Z1L \cdot (I_{asf} + k_0 \cdot I_r) \cdot \overline{\left(I_r \cdot e^{j \cdot \theta} \right)} \right]}$$

$$L = 0.4$$

So How do we generate digital signals of Voltage and Current of the Simulation 4 Cycles with 7680 samples per second (128 samples per cycle in 60HZ system)?

$$k := 0 .. 511$$

$$\text{deltT} := 0.0001302$$

$$V_{an_k} := |VSP_0| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(VSP_0))$$

$$T1_k := k \cdot \text{deltT}$$

$$T2_k := 512 \cdot \text{deltT} + k \cdot \text{deltT}$$

$$T3_k := 1024 \cdot \text{deltT} + k \cdot \text{deltT}$$

$$V_{bn_k} := |VSP_1| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(VSP_1))$$

$$\frac{1}{\text{deltT}} = 7.68 \times 10^3$$

$$\frac{7680}{60} = 128$$

$$V_{cn_k} := |VSP_2| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(VSP_2))$$

$$V_{af_k} := |VS_0| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(VS_0))$$

$$V_{bf_k} := |VS_1| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(VS_1))$$

$$T1_k =$$

0
$1.302 \cdot 10^{-4}$
$2.604 \cdot 10^{-4}$
$3.906 \cdot 10^{-4}$
$5.208 \cdot 10^{-4}$
$6.51 \cdot 10^{-4}$
$7.812 \cdot 10^{-4}$
$9.114 \cdot 10^{-4}$
$1.042 \cdot 10^{-3}$
$1.172 \cdot 10^{-3}$
$1.302 \cdot 10^{-3}$

$$V_{cf_k} := |VS_2| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(VS_2))$$

$$I_{an_k} := |IPRE_0| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(IPRE_0))$$

$$I_{bn_k} := |IPRE_1| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(IPRE_1))$$



$$I_{cn_k} := |IPRE_2| \cdot \sin(2 \cdot \pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(IPRE_2))$$

$$I_{af_k} := |IS_0| \cdot \sin(2\pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(IS_0))$$

$$I_{bf_k} := |IS_1| \cdot \sin(2\pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(IS_1))$$

$$I_{cf_k} := |IS_2| \cdot \sin(2\pi \cdot 60 \cdot k \cdot \text{deltT} + \arg(IS_2))$$

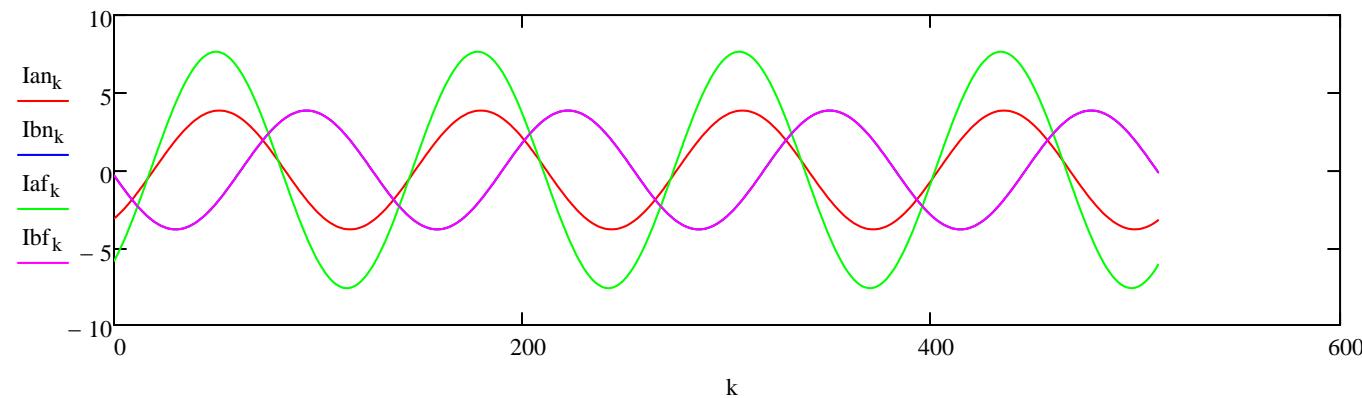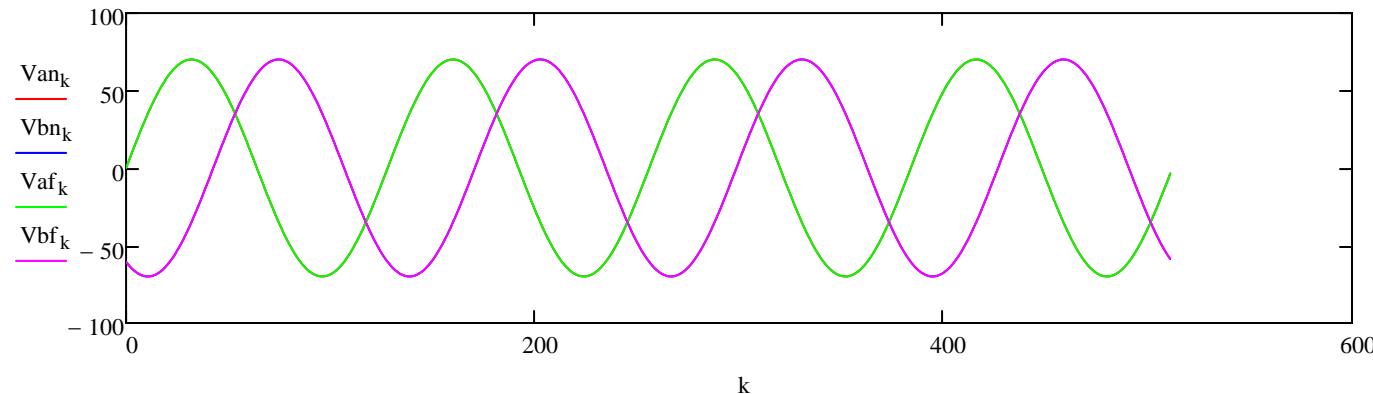1.432 · 10 ⁻³
1.562 · 10 ⁻³
1.693 · 10 ⁻³
1.823 · 10 ⁻³
...



Let us make Normal (4 cycle)+ Fault (4 cycle) +Normal (4 cycle)

Seg1 := augment(T1, Ian, Ibn, Icn, Van, Vbn, Vcn)

Seg2 := augment(T2, Iaf, Ibf, Icf, Vaf, Vbf, Vcf)

```
Seg3 := augment(T3, Ian, Ibn, Icn, Van, Vbn, Vcn)
```

```
Final := stack(Seg1, Seg2, Seg3)
```

$\text{Ir} := \text{Final}^{\langle 0 \rangle}$

$\text{Ia} := \text{Final}^{\langle 1 \rangle}$

$\text{Ib} := \text{Final}^{\langle 2 \rangle}$

$\text{Ic} := \text{Final}^{\langle 3 \rangle}$

$\text{Va} := \text{Final}^{\langle 4 \rangle}$



$\text{Vb} := \text{Final}^{\langle 5 \rangle}$

$\text{Vc} := \text{Final}^{\langle 6 \rangle}$

$\text{Ir} := \text{Ia} + \text{Ib} + \text{Ic}$

$\text{Vr} := \text{Va} + \text{Vb} + \text{Vc}$

Acquired currents and voltages.

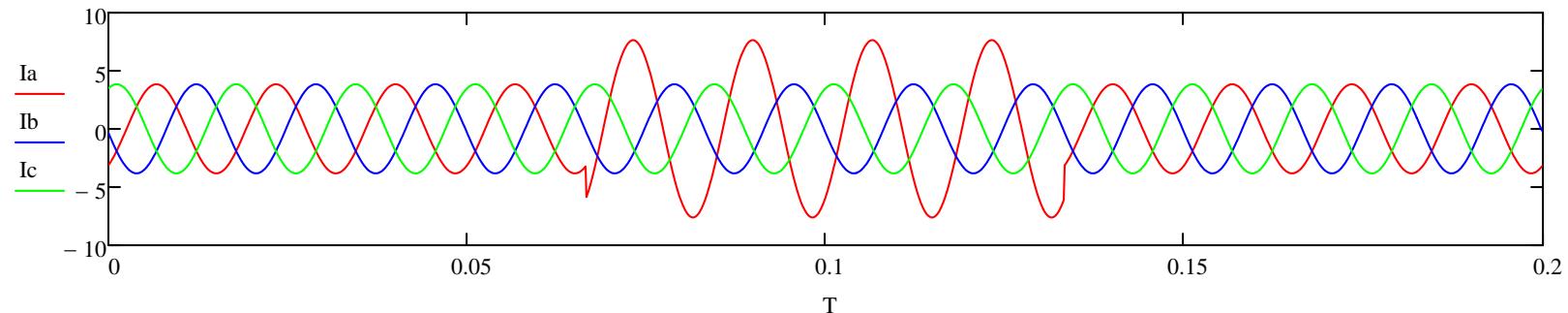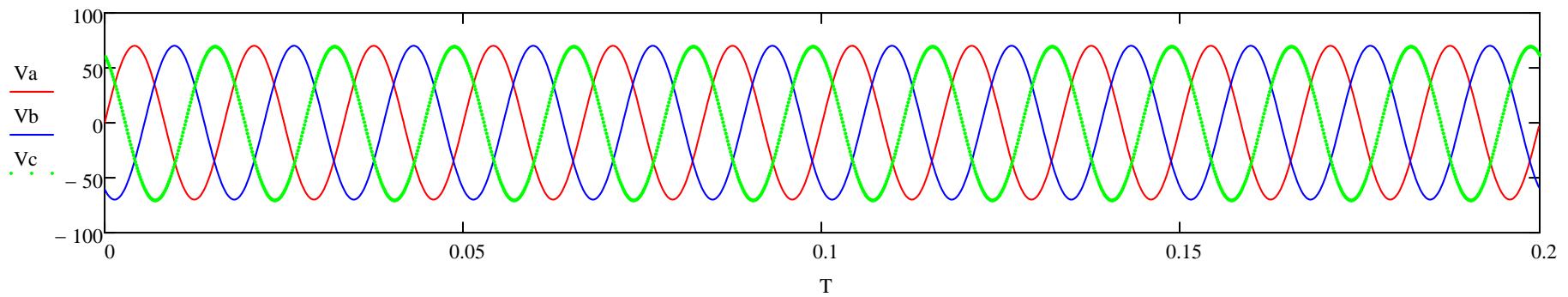

FFT calculation:

$\text{m} := \text{length}(\text{Va})$

$$m = 1.536 \times 10^3$$

window := 128

wind := window - 1

$$\text{Isa} := \text{Ia} + k0 \cdot \text{Ir}$$

$$\text{Isb} := \text{Ib} + k0 \cdot \text{Ir}$$

$$\text{Isc} := \text{Ic} + k0 \cdot \text{Ir}$$

$$k0 = 0.667$$

$$\text{dd} := 0 .. \frac{m}{\text{window}} - 1$$

$$\frac{(m - \text{window})}{8} = 176$$

$$\text{kk} := 0 .. m - \text{window}$$

$$k := 0 .. \frac{m - \text{window}}{8}$$

$$\text{Ua}_k := \text{submatrix}(\text{Va}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Ub}_k := \text{submatrix}(\text{Vb}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Uc}_k := \text{submatrix}(\text{Vc}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Ao}_k := \text{submatrix}(\text{Ir}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Aa}_k := \text{submatrix}(\text{Isa}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Ab}_k := \text{submatrix}(\text{Isb}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Ac}_k := \text{submatrix}(\text{Isc}, k \cdot 8, k \cdot 8 + \text{wind}, 0, 0)$$

$$\text{Pa}_k := \text{FFT}(\text{Ua}_k)$$

$$\text{Pb}_k := \text{FFT}(\text{Ub}_k)$$

$$\text{Pc}_k := \text{FFT}(\text{Uc}_k)$$

$$\text{Fa}_k := \text{FFT}(\text{Aa}_k)$$

$$\text{Fb}_k := \text{FFT}(\text{Ab}_k)$$

$$\text{Fc}_k := \text{FFT}(\text{Ac}_k)$$

$$\text{Pa}_k := \text{FFT}(\text{Ua}_k)$$

$$\text{Pb}_k := \text{FFT}(\text{Ub}_k)$$

$$\text{Pc}_k := \text{FFT}(\text{Uc}_k)$$

$$\text{Fo}_k := \text{FFT}(\text{Ao}_k)$$

Novosel Algorithm

(Left to exam only for comparison, so that results can be compared with patent 5)



$$\text{IaN} := 0$$

$$k1a_k := \frac{\binom{Pa_k}{1,0}}{\binom{Fa_k}{1,0} \cdot Z1L} + \frac{Z1R}{Z1L} + 1 \quad k2a_k := \frac{\binom{Pa_k}{1,0}}{\binom{Fa_k}{1,0} \cdot Z1L} \cdot \left(\frac{Z1R}{Z1L} + 1 \right) \quad k3a_k := \frac{\left[\binom{Fa_k}{1,0} - IaN \right]}{\binom{Fa_k}{1,0} \cdot Z1L} \cdot \left(\frac{Z1S + Z1R}{Z1L} + 1 \right)$$

$$a1_k := 1 \quad ab1_k := \left(\operatorname{Re}(k1a_k) - \frac{\operatorname{Im}(k1a_k) \cdot \operatorname{Re}(k3a_k)}{\operatorname{Im}(k3a_k)} \right) \quad ac1_k := \operatorname{Re}(k2a_k) - \frac{\operatorname{Im}(k2a_k) \cdot \operatorname{Re}(k3a_k)}{\operatorname{Im}(k3a_k)}$$

$$ma_k := \frac{-ab1_k - \sqrt{(ab1_k)^2 - 4 \cdot ac1_k \cdot a1_k}}{2 \cdot a1_k}$$
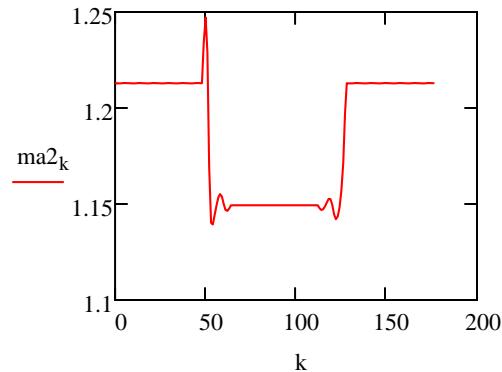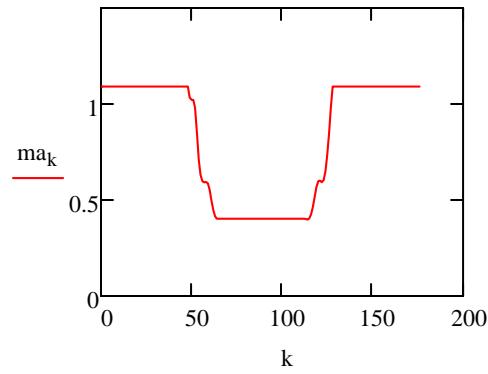
$$ma2_k := \frac{-ab1_k + \sqrt{(ab1_k)^2 - 4 \cdot ac1_k \cdot a1_k}}{2 \cdot a1_k}$$



Result from Novosel algorithm: $ma_{100} = 0.402$

Patent 5 - actual EXAM algorithm:

C1 and C2 parameters

$$C1_k := ZL_{(0,0)} \left(Fa_k \right)_{1,0} + ZL_{(0,1)} \cdot \left(Fb_k \right)_{1,0} + ZL_{(0,2)} \cdot \left(Fc_k \right)_{1,0} \quad C2_k := ZR_{(0,0)} \left(Fa_k \right)_{1,0} + ZR_{(0,1)} \cdot \left(Fb_k \right)_{1,0} + ZR_{(0,2)} \cdot \left(Fc_k \right)_{1,0}$$

Parts of the polynomial

$$ar_k := \operatorname{Re} [C1_k \cdot ZL_{(0,0)}]$$

$$ai_k := \operatorname{Im} [C1_k \cdot ZL_{(0,0)}]$$

$$br_k := \operatorname{Re} \left[\left(Pa_k \right)_{1,0} \cdot ZL_{(0,0)} - C1_k \cdot ZL_{(0,0)} + C1_k \cdot ZR_{(0,0)} \right]$$

$$bi_k := \operatorname{Im} \left[\left(Pa_k \right)_{1,0} \cdot ZL_{(0,0)} - C1_k \cdot ZL_{(0,0)} + C1_k \cdot ZR_{(0,0)} \right]$$

$$cr_k := \operatorname{Re} \left[ZR_{(0,0)} \cdot \left[\left(Pa_k \right)_{1,0} - C1_k \right] \right]$$

$$ci_k := \operatorname{Im} \left[ZR_{(0,0)} \cdot \left[\left(Pa_k \right)_{1,0} - C1_k \right] \right]$$



$$dr_k := \operatorname{Re} \left[\left(Pa_k \right)_{1,0} - C1_k - C2_k \right]$$



$$di_k := \operatorname{Im} \left[\left(Pa_k \right)_{1,0} - C1_k - C2_k \right]$$

$$polya_k := ar_k - \frac{dr_k \cdot ai_k}{di_k}$$

$$polyb_k := br_k - \frac{dr_k \cdot bi_k}{di_k}$$
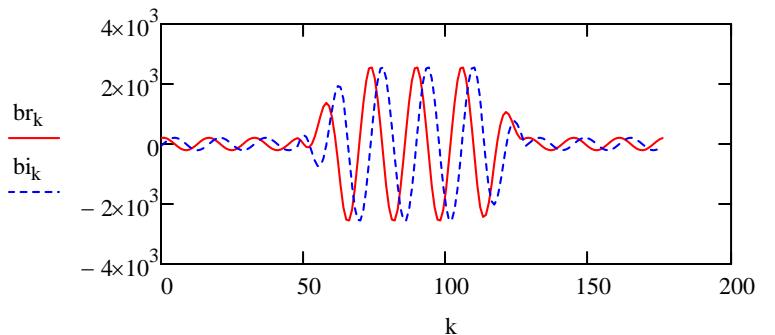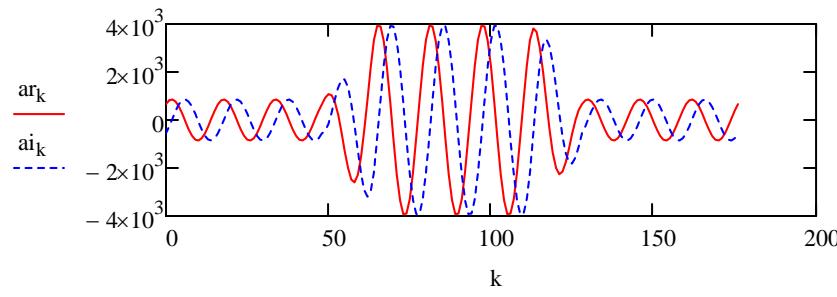
$$polyc_k := cr_k - \frac{dr_k \cdot ci_k}{di_k}$$




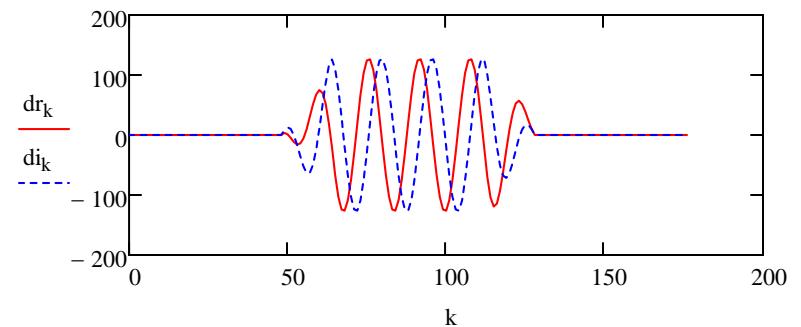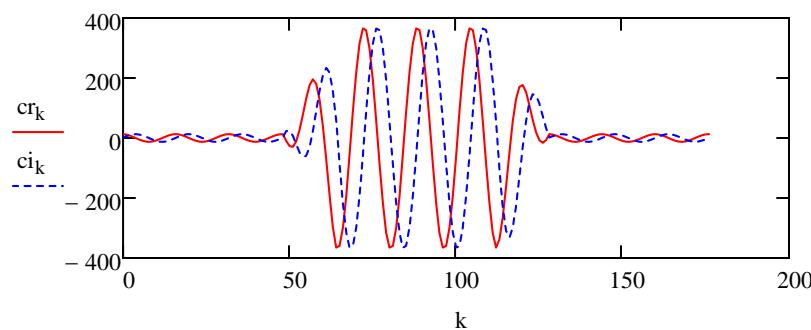


Solving the polynomial

$$ma_k := \frac{-polyb_k + \sqrt{(polyb_k)^2 - 4 \cdot polya_k \cdot polyc_k}}{2 \cdot polya_k}$$
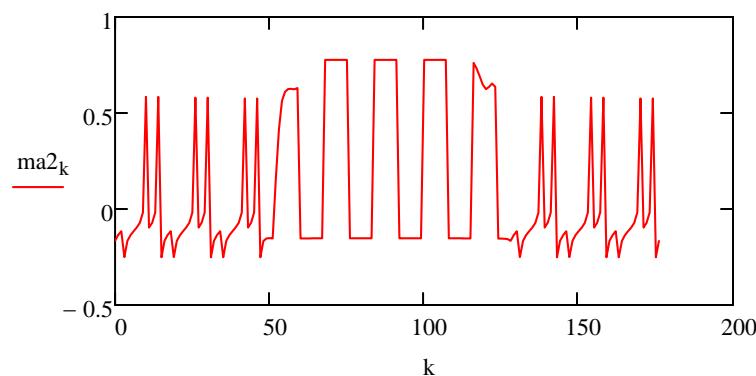
$$ma2_k := \frac{-polyb_k - \sqrt{(polyb_k)^2 - 4 \cdot polya_k \cdot polyc_k}}{2 \cdot polya_k}$$



$$ma_{110} = 0.776$$

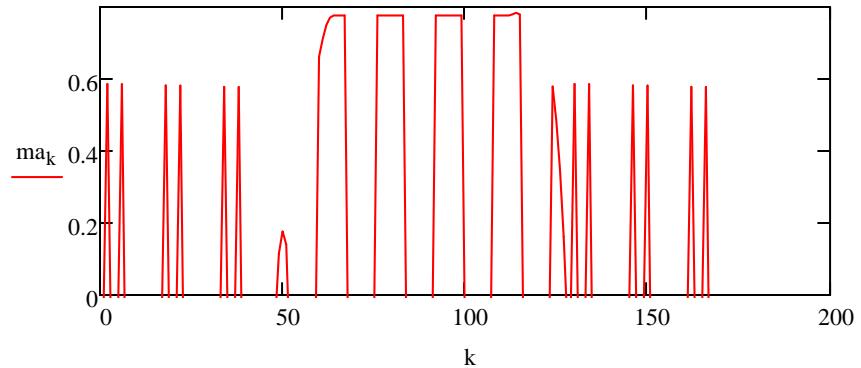

$$ma2_{100} = 0.776$$


$$\text{result} := 2 \cdot (1 - ma_{110})$$

Result from Patent 5:

result = 0.447

Issue in Patent 5 is that there is oscillation in the result, because of changing real and imaginary parts.
 Improvement to the algorithm is to use norm instead:
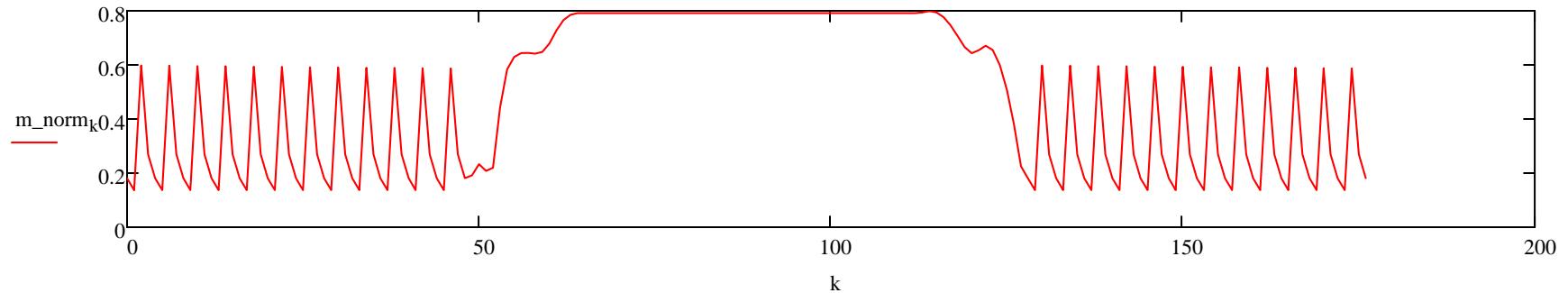
$$m_{\text{norm}}_k := \sqrt{(ma_k \cdot ma_k + ma2_k \cdot ma2_k)}$$



$$m_{\text{norm}}_{100} = 0.791$$

$$\text{result} := 2 \cdot (1 - m_{\text{norm}}_{110})$$

Result from Patent 5:

$$\text{result} = 0.417$$

The improvement makes the signal more stable, and it is easier to determine the fault distance.
 But the algorithm is not very accurate, with different fault distances following results were acquired:

Distance	Patent 5	Improvement
0.1	0.09	0.07
0.2	0.2	0.17
0.3	0.32	0.29
0.4	0.45	0.42
0.5	0.6	0.56
0.6	0.76	0.72
0.7	0.94	0.9
0.8	1.2	1.1
0.9	1.4	1.3
1.0	1.6	1.45

Initial algorithm is better when fault distance is small and improvement is better when fault distance is long.

More testing with fault data was not done, since I did not find from files what was the actual correct fault distance

